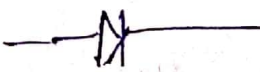



Power Electronics

→ It is defined by control and conversion of high power application, with less switching losses and high efficiency.


→ the device that we see in power electronics are

(1) Power diode 


(2) thyristor

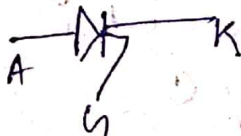(a) SCR 

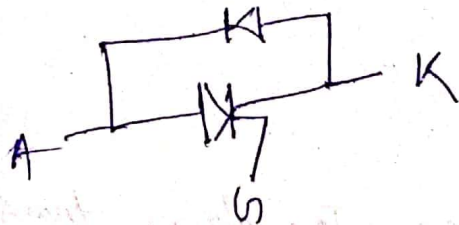(b) A.SCR / RCT → Reverse Control Thyristor
Asymmetric Silicon Control Rectifier.



(c) MTO → Gate turn off thyristor

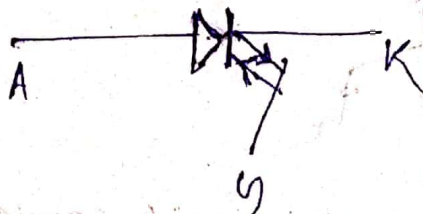

(d) LASCR → Light activated silicon control rectifier.




Pravas Radhiary


③ Diode Alternating Current




④ TRIAC - Triode con Alternating Current

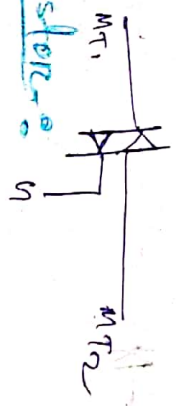

⑤ Insulated gate Bipolar transistor

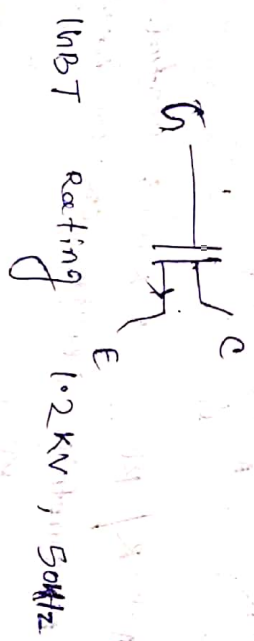


⑥ Transistor -

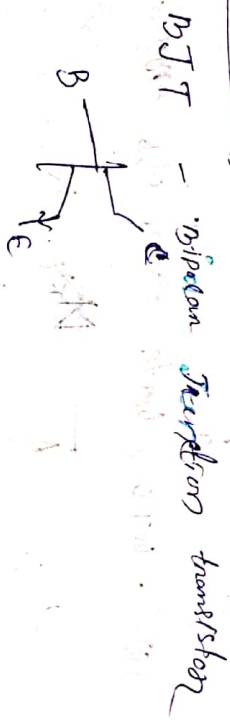


MOSFET - metal oxide semiconductor field effect transistor


enhancement type MOSFET

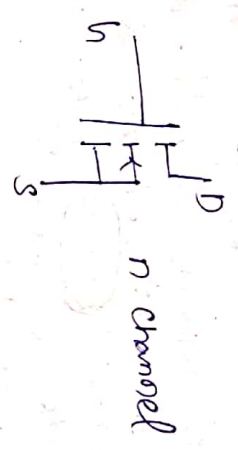

bipolar type MOSFET

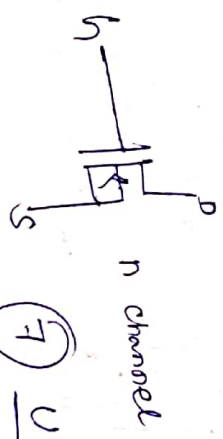

⑦ UJT

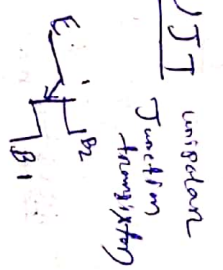


Diode rated in P.I.V

0.7V Silicon


0.3V Germanium

1V Power diode


operating mode of switch:

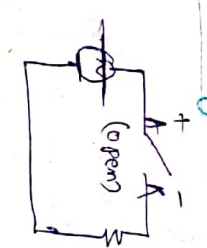

Forward blocking mode

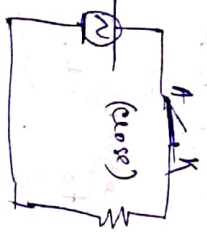

Forward conducting mode

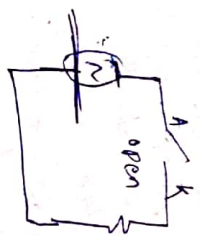


Reverse blocking mode



Reverse conducting mode

VI characteristic of a thyristor :- or SCR

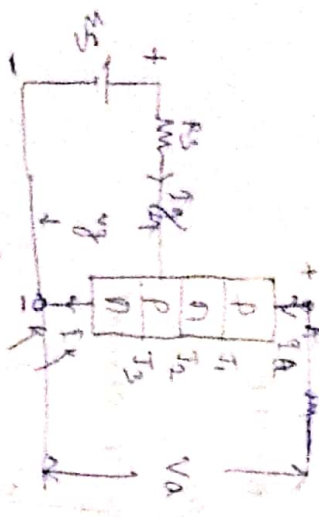→ The anode and cathode are connected to main source through the load. The gate which provides Positive gate current from gate to the cathode.




Here, V_a is the anode voltage across the thyristor terminals A, K and I_a is the anode current. Thyristor has three basic modes of operation.

- Reverse blocking mode.
- Reverse conduction mode.
- Forward conduction mode.
- Forward blocking mode.

Reverse blocking mode

When cathode is made positive, with respect to anode, with switch S open. Thyristor is reverse biased. It behaves like two diodes are connected in series with reverse voltage applied across them. A small leakage current of the order of a few milliamperes flows.

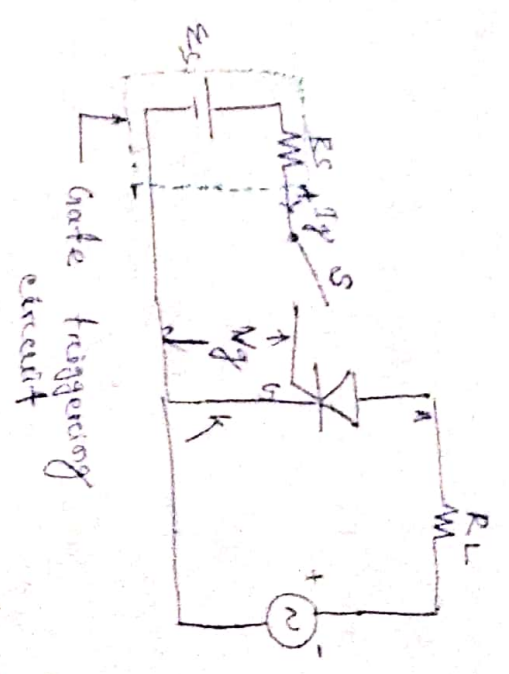This is reverse blocking mode called the off state of the thyristor. Gate I_g & I_g , R.B. and T₂ F.B.




→ If the reverse voltage is increased, very at a critical breakdown level, called reverse breakdown voltage V_{BR} . An avalanche current increase rapidly. A large rise to more loss associated with V_{BR} gives rise to thyristor damage as the junction temperature may exceed. Its permissible temperature rise.

- It should be ensured that maximum working reverse voltage across a thyristor does not exceed V_{BR} .
- When reverse voltage applied across thyristor is less than V_{BR} , the device offers a high impedance in the reverse direction.
- The SCR in the reverse blocking mode treated as an open switch.

→ in the characteristic lines

OP is reverse blocking mode

PQ is reverse avalanche region.

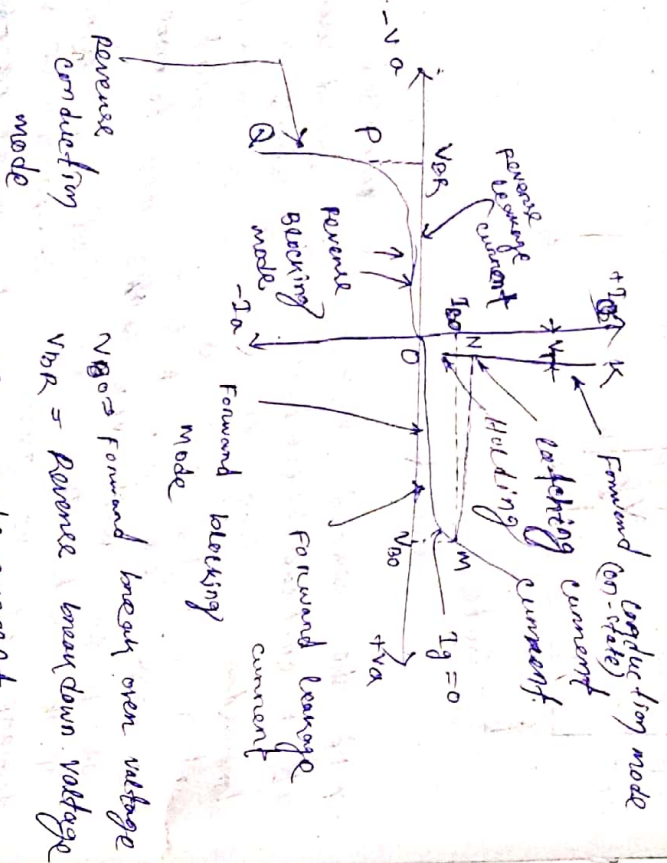

V_{BO} = Forward break over voltage
 V_{BR} = Reverse breakdown voltage
 I_{GR} = gate current

→ NE characteristic after avalanche mode breakdown during reverse blocking mode is applicable only, when the load resistance is zero.

If the load resistance is present, a large anode current associated with avalanche breakdown at V_{BR} would cause substantial voltage drop across load as a result, NE characteristic in 3rd quadrant would bend to right of vertical line drawn at V_{BR} .

Forward blocking mode:

→ when the anode is positive with respect to the cathode, with gate circuit open, thyristor is said to be forward biased.

→ here I_1 & I_2 are forward biased and I_3 reverse biased.

→ In this mode small current, called forward leakage current flows.

→ "ON" shows forward blocking mode of SCR.

→ As the small leakage current of SCR, due to SCR offers a high impedance.

→ Therefore, a thyristor can be treated as an open switch even in the forward blocking mode.

Forward conduction mode:

→ when anode to cathode forward voltage is increased with gate circuit open, reverse bias junction J_2 will cause forward breakdown voltage V_{BO} .

→ After this breakdown, thyristor gets turned ON with point M. At once shifting to N and the point any where N and K, I_1 & I_2 represent the forward conduction mode.

→ A thyristor can be brought from forward blocking mode to forward conduction mode by turning it on by applying...

- (i) a positive gate pulse between gate and cathode.
- (ii) a forward breakover voltage across anode and cathode.

→ Here N.K shows the voltage across the thyristor ^{drop} is of the order of 1 to 2 V depending upon the SCR.

→ N.K across voltage drop increases with increasing slightly with increasing in anode current.

→ Anode current is limited by load impedance alone the voltage across SCR quite small. (N.T).

→ The small voltage drop V_f across the device is due to ohmic drop in the four layers.

→ In forward conduction mode thyristors treated as closed switch.

Thyristor turn-on methods:-

- (a) forward voltage triggering
- (b) gate triggering
- (c) dv/dt triggering
- (d) temperature triggering
- (e) light triggering

(a) Forward voltage triggering:-

→ when forward voltage is applied between anode and cathode with gate circuit open, Junction J_2 is reverse biased. As a result depletion layer formed Junction J_2 .

→ The width of this layer decrease with an increase in anode cathode voltage.

→ If forward voltage across anode-cathode is gradually increased, a stage comes the depletion layer across J_2 vanishes.

→ At that moment, V_{BO} said to be breakdown and the voltage at which it occurs is called forward break over voltage V_{BO} .

→ At this voltage, the thyristor changes from off-state (high voltage with low leakage current) to on state.

→ But in on-state, low voltage across SCR and high ~~reverse~~ forward current.

→ This Forward large current limit by load impedance.

- The magnitude of the V_{BO} and V_{BR} are nearly same and temperature dependent.
- In practice V_{BR} is slightly more V_{BO} .
- After avalanche breakdown, I_2 loses its reverse blocking capacity.
- If the anode voltage is reduce V_{BO} then continue current condition SCR.
- The SCR can now be turned off only by reducing the anode current below a certain value called holding current.



(b) Gate triggering:


→ Turning on of thyristors by gate triggering is simple, reliable and efficient, it is therefore the most usual method of firing the forward biased SCR.

→ A thyristor with forward break over voltage higher than the normal working voltage is chosen. This means that the thyristor will remaining forward blocking mode with normal working voltage across anode and cathode with gate open.

→ However, when turn on of a thyristor is required, a positive gate voltage between gate and cathode is applied.

- with gate current this established, charges are injected into inner p layer and voltage at which forward breakover occurs is reduced.
- Higher gate current, lower is the forward break over voltage.
- when positive gate current is applied between gate and cathode terminal.
- In practice the magnitude of gate current is more than the minimum gate current required to turn on the SCR. The magnitudes of gate current are 20 to 200mA.

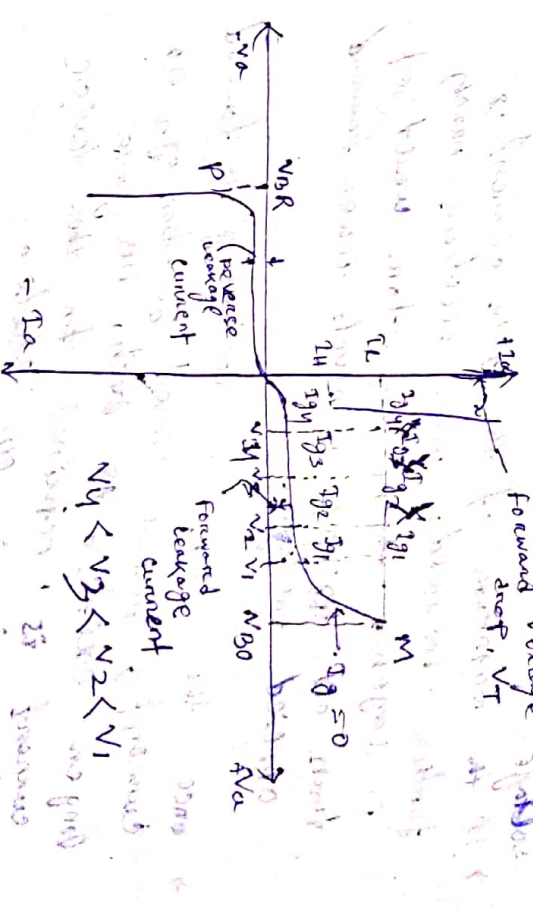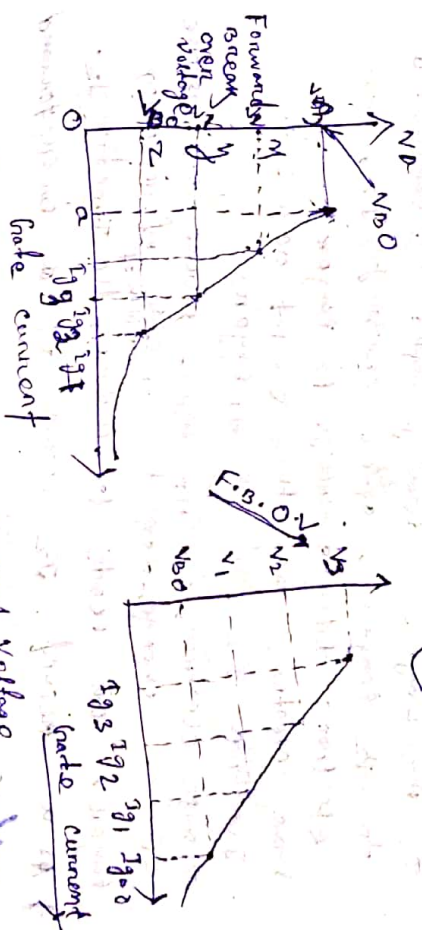

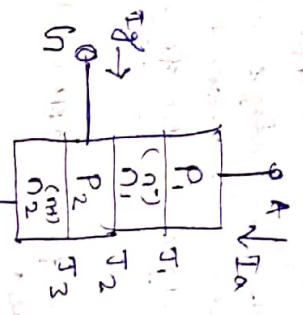

Simple model of thyristor

- When we applied gate current then the electrons from n_2 layer cross junction T_3 .
- n_2 layer is heavily doped as compared to p_2 layer, after crossing T_3 , these electrons diffuse through p_2 layer.
- The electrons one then swept across the junction T_2 into the n_1 layer.
- These electrons in n_1 layer reduce the positive space charge on the n_1 side of depletion layer, this leads to reduce the junction T_2 .
- As a result, T_2 occurs at a lower forward voltage.
- If the magnitude of the gate current is further increased, more electrons reach n_1 layer. then thyristor would get turn on at a much lower forward applied voltage.

→ once the SCR is conducting a forward current, reverse biased junction T_2 no longer exists as reverse bias for the device current is maintained in ON state.

if the gate current is removed, the conduction from anode to cathode remains unaffected.

However, the gate current, the thyristor will turn off again. It is reduce to zero before the rising anode current attains a value called latching current. The thyristor will turn off again.

Latching current: (I_L)

It is defined as the minimum value of anode current which if must attain during turn on process to maintain conduction when gate signal is removed.

Holding current: (I_H)

It is defined as the minimum value of anode current below which it must fall for turning off the thyristor.

$$I_L \approx 3 I_H$$

In industrial applications, holding current is almost taken as zero.

(c) dv/dt triggering :- with forward voltage across

anode and cathode of a thyristor.

→ The two junction T_1 , T_3 are F.B and T_2 is F.B.

→ The reverse biased T_2 has the characteristic of capacitor due to charge exist across the junction.

In other word ^{space} charges exist in the depletion region near Junction J_2 and J_2 Junction behaves like capacitance.

→ If forward ~~to~~ voltage is suddenly applied, a changing current ^{through} Junction capacitance C_j may turn on the SCR.
 → The ^{suddenly} applied voltage V_a reach across Junction J_2 , the changing current I_c given by

$$i_c = \frac{dQ}{dt} = \frac{d(C_j \cdot V_a)}{dt}$$

As the Junction capacitance C_j almost constant, so $\frac{dC_j}{dt} = 0$

So $i_c = C_j \frac{dV_a}{dt}$

If the rate of increase ~~forward~~ voltage dV_a/dt , also the changing current ~~the~~ increase. This changing current play a role of gate current. and turns on the SCR, ~~even~~ gate signal is zero.
 → If V_a is small, it is the rate of change of V_a that plays the role of turning - ON the device.

(d) Temperature triggering or Thermal triggering


During the forward blocking mode most of the applied voltage appears across the Junction J_2 .

→ This voltage across J_2 associated with leakage current & would rise temperature of this Junction, with increase in temperature decrease \downarrow depletion length. This further draws more ^{leakage} current and more Junction temperature.

→ With the cumulative process, at high temperature, near the Junction this temperature vanished. The reverse biased Junction J_2 and the device gets turned ON.

Light triggering

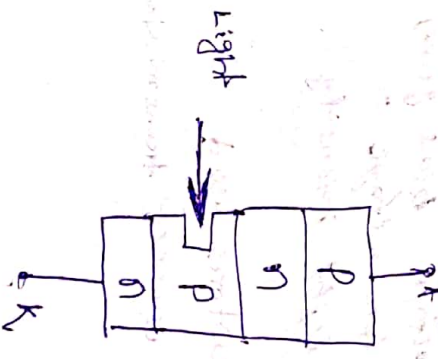In light trigger SCR a recess is made in the inner 'p' layers.



→ when this recess is irradiated, free energy carriers are generated just like when gate signal is applied between gate and cathode.

→ The pulse of light of appropriate wavelength is guided by optical fibres for irradiation.

→ If the intensity of this light thrown on the recess exceeds a certain value, forward-biased SCR is turned ON. Such thyristors are known as light activated SCR (LASER).

→ LASER may be triggered with a light source or a gate signal. Some times both cases used for triggering purpose.

→ The gate is biased with voltage or current slightly less than that required to turn it ON, now a beam of light directed at the inner p-n junction turns on the SCR.


→ The light intensity required to turn on the SCR depends upon the voltage bias given to the gate. If the higher voltage or current bias, lower light intensity required.

→ Light triggered thyristors used high voltage direct current transmission systems.

Systems.

→ SCRs are connected in series-parallel combination and light triggering has the advantage of electrical isolation between power and control circuits.

R.M.S. value of half wave rectifiers:

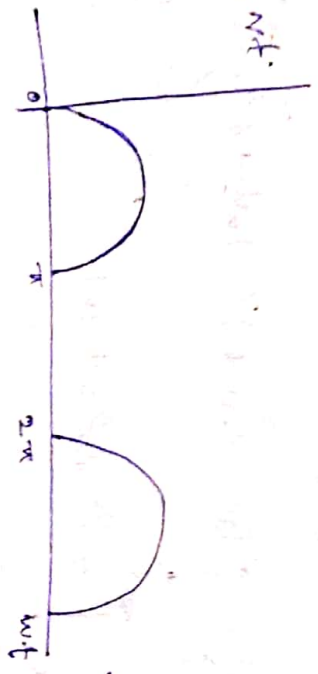

$$T = 2\pi \text{ (sec)}$$

$$f = \frac{1}{2\pi} \text{ (Hz)}$$

$$\omega = 2\pi f$$

$$= \frac{2\pi}{2\pi}$$

$$= 1 \text{ (rad/sec)}$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V^2 dt}$$

$$= \begin{cases} \sqrt{V_m^2 \int_0^\pi \sin^2 \omega t d\omega t} & ; 0 < \omega t < \pi \\ 0 & ; (\pi < \omega t < 2\pi) \end{cases}$$

$$V_{rms} = \frac{1}{T} \int_0^T V(t)^2 dt$$

$$= \frac{1}{2\pi} \int_0^{2\pi} V(t)^2 dt$$

$$= \frac{1}{2\pi} \left[\int_0^{\pi} V(t)^2 dt + \int_{\pi}^{2\pi} V(t)^2 dt \right]$$

$$= \frac{1}{2\pi} \int_0^{\pi} (V_m \sin \omega t)^2 dt + \int_{\pi}^{2\pi} (V_m \sin \omega t)^2 dt$$

$$\left[\because \sin 2\pi = 0 \right]$$

$$= \frac{1}{2\pi} \int_0^{2\pi} V_m^2 \sin^2 \omega t dt$$

$$= \frac{V_m^2}{2\pi} \int_0^{2\pi} \frac{1 - \cos 2\omega t}{2} dt$$


$$= \frac{V_m^2}{2\pi} \left[\frac{1}{2} \omega t \right]_0^{2\pi} - \frac{1}{2} \left[\frac{\sin 2\omega t}{2} \right]_0^{2\pi}$$

$$= \frac{V_m^2}{2\pi} \left(\frac{1}{2} (2\pi - 0) - \frac{1}{2} (\sin 0) \right)$$


$$= \frac{V_m^2}{2\pi} \left(\frac{\pi}{2} \right) \quad \left[\because \sin 2\pi = \sin 0 = 0 \right]$$

$$V_{rms} = \sqrt{\frac{V_m^2}{4}} \quad \left[\because \sin 2\pi = 0 \right]$$

$$V_{rms} = \frac{V_m}{2}$$

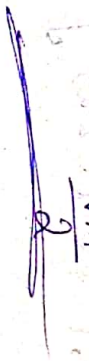

R.M.S Value of full wave rectifier

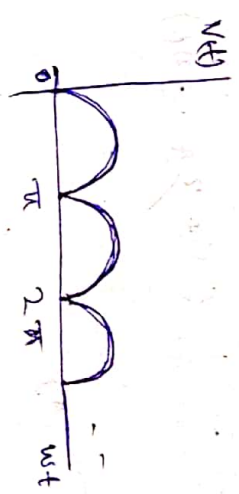

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V(t)^2 dt}$$

$$T = \pi$$

$$f = \frac{1}{T} \text{ cycle/sec}$$

$$\omega = 2\pi f = \frac{1}{\pi} = 2$$

$$V(t) = V_m \sin \omega t, \quad 0 < \omega t < \pi$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V(t)^2 dt}$$

$$= \sqrt{\frac{1}{T} \int_0^{\pi} V_m^2 (\sin \omega t)^2 dt}$$

$$= \sqrt{\frac{1}{T} \int_0^{\pi} V_m^2 \sin^2 \omega t dt}$$


$$= \sqrt{\frac{V_m^2}{T} \int_0^{\pi} \sin^2 \omega t dt}$$

$$= \sqrt{\frac{V_m^2}{T} \int_0^{\pi} \frac{1 - \cos 2\omega t}{2} dt}$$

$$= \sqrt{\frac{V_m^2}{2T} \int_0^{\pi} (1 - \cos 2\omega t) dt}$$

$$= \sqrt{\frac{V_m^2}{2T} \left[\omega t \right]_0^{\pi} - \left[\frac{\sin 2\omega t}{2} \right]_0^{\pi}}$$
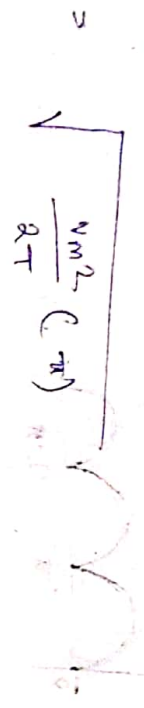
$$= \sqrt{\frac{V_m^2}{2T} \left[(\pi-0) - \frac{1}{2} (\sin 2\pi - \sin 0) \right]}$$




$$= \sqrt{\frac{V_m^2}{2T} \times \pi}$$

$$V_{r.m.s} = \frac{V_m}{\sqrt{2}}$$

Average value for half wave rectification:
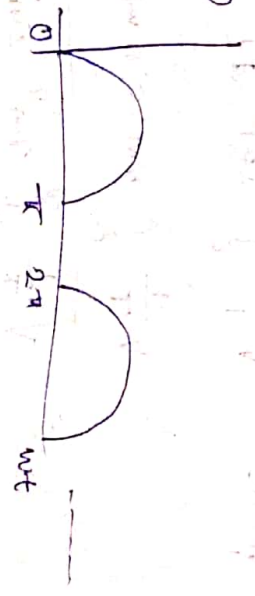
$$V_{avg} = \frac{1}{T} \int_{\pi}^{2\pi} V(t) dt$$



$$T = 2\pi \text{ (sec)}$$

$$f = \frac{1}{2\pi} \text{ Hz}$$

$$\omega = 2\pi \times \frac{1}{2\pi} = 1 \text{ (rad/sec)}$$

$$V(t) = \begin{cases} V_m \sin(\omega t) & ; 0 < \omega t < \pi \\ 0 & ; \pi < \omega t < 2\pi \end{cases}$$

$$V(t) = \begin{cases} V_m \sin(\omega t) & ; 0 < \omega t < \pi \\ 0 & ; \pi < \omega t < 2\pi \end{cases}$$

$$V_{r.m.s} = \frac{1}{T} \int_0^T V(t) dt$$

$$= \frac{1}{T} \int_0^{\pi} V_m \sin \omega t dt + \int_0^{2\pi} 0 dt$$

$$= \frac{1}{T} \int_0^{\pi} V_m \sin \omega t dt$$

$$= \frac{1}{T} \int_0^{\pi} V_m \sin \omega t dt$$

$$= \frac{V_m}{T} (-\cos \omega t) \Big|_0^{\pi}$$

$$= \frac{V_m}{T} [-(\cos \pi - \cos 0)]$$

$$= \frac{V_m}{2\pi} (-\cos \pi + \cos 0)$$


$$= \frac{V_m}{2\pi} [-(-1) + 1]$$

$$= \frac{V_m}{\pi}$$

$$V_{avg} = \frac{V_m}{\pi}$$

Average value of full wave rectifier
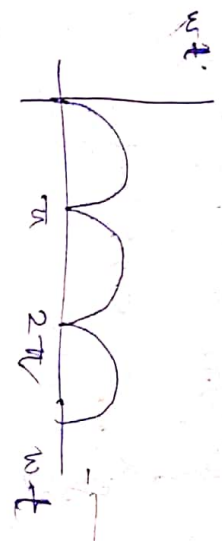
$$V_{avg} = \frac{1}{T} \int_0^T V(t) dt$$



$$T = \pi$$

$$f = \frac{1}{T}$$

$$\omega = 2\pi f = \frac{1}{\pi} = 2$$

$V(t) = V_m \sin(\omega t)$; $0 < \omega t < \pi$

$$V_{avg} = \frac{1}{T} \int_0^T V_m \sin \omega t dt$$

$$= \frac{V_m}{T} \int_0^{\pi} \sin \omega t dt$$

$$= \frac{V_m}{\pi} \int_0^{\pi} \sin \omega t dt$$

$$= \frac{V_m}{\pi} (-\cos \omega t) \Big|_0^{\pi}$$

$$= \frac{V_m}{\pi} [-\cos \pi - (-\cos 0)]$$


$$= \frac{V_m}{\pi} [-(-1) + \cos 0]$$

$$= \frac{V_m}{\pi} (1+1)$$

$$= \frac{2V_m}{\pi}$$

$$V_{avg} = \frac{2V_m}{\pi}$$

Gate characteristic of thyristor:

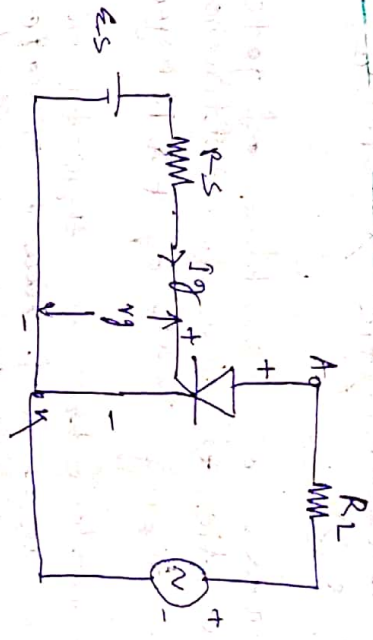


$$E_S = V_g + I_g R_S$$

$$V_g = E_S - I_g R_S$$

$$I_g = mI_a + c$$

$$I_g = V_g, m = \frac{R_S}{R_S + R_{gk}}$$

$$c = I_g, c = E_S$$

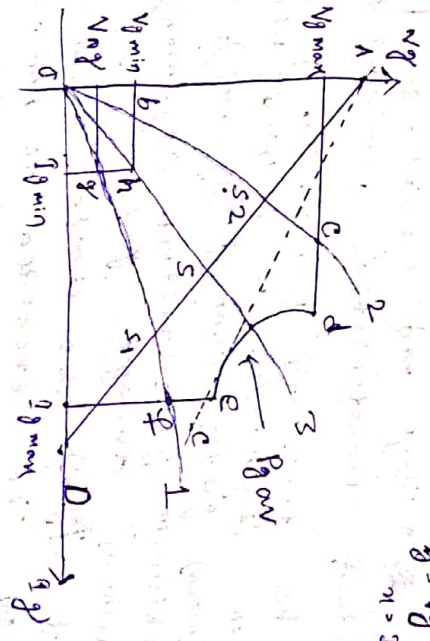

→ Here, positive gate to cathode voltage V_g and positive gate to cathode I_g represent DC values as gate cathode circuit of a thyristor is a PN Junction. Gate characteristics of the device are similar to that of a diode.

→ For a particular types of SCR the $V_g \cdot I_g$ characteristic is spread between ① & ②.

→ This spread or scatter of gate characteristic is due to difference in the doping levels of P & N layers.

→ Gate characteristic of thyristor or SCR gives us a brief idea to operate it within a safe region of applied gate voltage and current. So it is important characteristics regarding thyristor.

→ At the time of manufacturing each SCR or thyristor, it is specified with the maximum gate current (I_{g-max}) and maximum gate voltage (V_{g-max}) and maximum average gate power dissipation limit (P_{avg}). These limits should not be exceeded to protect the SCR from damage and there is also specified minimum voltage (V_{g-min}) and minimum current (I_{g-min}) for proper operation of thyristor.

→ A gate non triggering voltage (V_{ng}) is also mentioned at the time of manufacturing of the device. All noises and unwanted signals should lie under this voltage (V_{ng}) to avoid the turn on of the thyristor.

→ Curve 1 represents the lowest voltage values that must be applied to turn on the SCR and curve 2 represents the highest values of voltage that can safely applied. So from operated area we can see the safety margin of SCR is between 1 & 2.

→ Now from the triggering circuit, we get

$$E_s = V_g + I_g R_s$$

where, $E_s =$ gate source voltage
 $V_g =$ gate cathode voltage
 $I_g =$ gate current
 $R_s =$ gate source resistance

→ A load line of gate source voltage is drawn as AD where OA = E_s and OD = E_s/R_s which is trigger circuit short circuit current.


→ Now, let a NI-characteristic of gate circuit is given by curve 3. The intersection point of load line (AD) and curve 3 is called operating point "B".

→ It is must evident that S_{max} lie between S_1 and S_2 on the load line.
 → ~~open decrease~~ the turn ON of the device, operating point should be as close to P_{max} as possible.


→ For decreasing the turn ON time and to avoid unwanted ^{signal to} turn ON of the device, operating point should be as close to P_{max} as possible.
 Slope of A_D = source resistance R_s .
 minimum amount of R_s can be determined by drawing tangent to the P_{av} curve from the point A.

Two transistor model of SCR or thyristor:

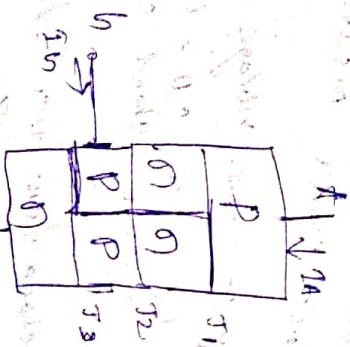
Basic working principle of SCR, can easily be understood by the two transistor model of P and N layers.



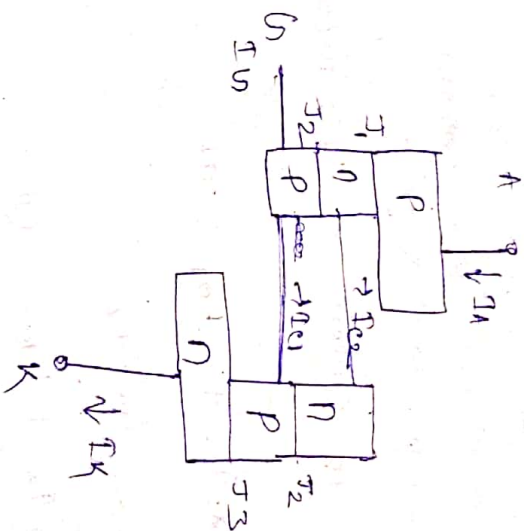→ It is a PNP thyristor. If we bisect two transistor we get **ONE PNP** transistor with J_1 and J_2 junctions and another **NPN** with J_2 and J_3 junctions.
 Figure below:



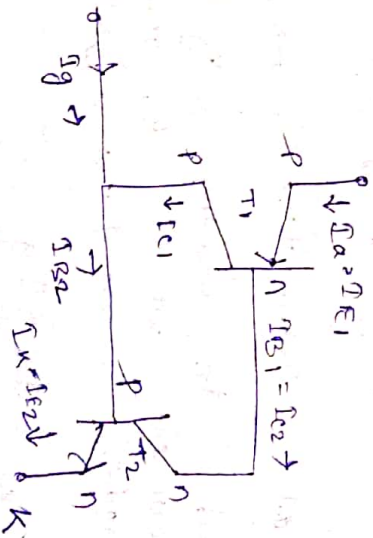the relation between collector current and emitter current given below:



Hence, I_c is collector current, I_e is emitter current, I_{EBO1} is the forward leakage current, α is the common base forward current gain and relationship between I_c and I_B is

$$I_c = \beta I_B$$

where, I_B = base current and β is common emitter forward current gain.

Let's for transistor T_1 this relation holds

$$I_{C1} = \alpha_1 I_{A1} + I_{EBO1} \quad (i)$$

And transistor T_2

$$I_{C2} = \alpha_2 I_{K1} + I_{EBO2} \quad (ii)$$

Now, by the analysis of two transistors model we can get anode current,

$$I_{A1} = I_{C1} + I_{E2} \quad (\text{assuming KCL})$$

$$I_{A1} = \alpha_1 I_{A1} + I_{EBO1} + \alpha_2 I_{K1} + I_{EBO2} - I_{C2}$$

If applied gate current I_g then cathode current will be the summation of anode current and gate current:

$$I_{K1} = I_{A1} + I_g$$

By substituting this value of I_{K1} in (iii)

$$I_{A1} = \alpha_1 I_{A1} + I_{EBO1} + \alpha_2 (I_{A1} + I_g) + I_{EBO2}$$

$$I_{A1} = \alpha_1 I_{A1} + I_{EBO1} + \alpha_2 I_{A1} + \alpha_2 I_g + I_{EBO2}$$

$$I_{A1} = (\alpha_1 + \alpha_2) I_{A1} + \alpha_2 I_g + I_{EBO1} + I_{EBO2}$$


$$[I_{A1} - (\alpha_1 + \alpha_2) I_{A1}] = \alpha_2 I_g + I_{EBO1} + I_{EBO2}$$

$$I_{A1} (1 - (\alpha_1 + \alpha_2)) = \alpha_2 I_g + I_{EBO1} + I_{EBO2}$$


$$I_{A1} = \frac{\alpha_2 I_g + I_{EBO1} + I_{EBO2}}{1 - (\alpha_1 + \alpha_2)}$$

When $I_g > 0$, no gate source opening
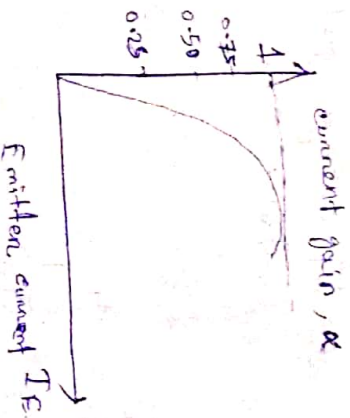
$$I_{A1} = \frac{I_{EBO1} + I_{EBO2}}{1 - (\alpha_1 + \alpha_2)}$$



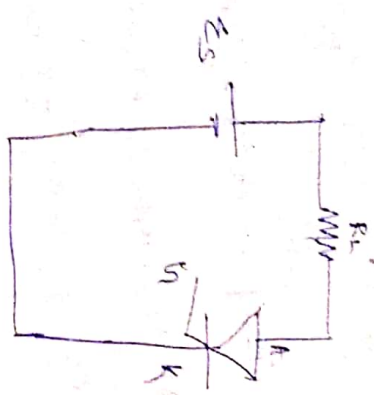* when we apply gate source is
 a. device then its I_E or I_K increase
 then its R value it increase then its also
 increase I_K increase which exceed I_L
 value then device turns ON.
 Thus I_A can be decrease by using
 Load ~~resistance~~ resistance.



Q-1 A trigger cut of a thyristor as
 a. source voltage of 15V and load line
 as slope -120 (V/A). the minimum gate
 current to turn on the SCR is 25mA
 compute source resistance voltage and
 circuit. the trigger current of an average gate
 power dissipation of 0.4W.

Ans:-
 $V_g = -I_g R_s + E_s$
 $V_g I_g = 0.4$
 $V_g = \frac{0.4}{I_g}$

$$0.4 = -I_g R_s + E_s$$

$$0.4 = -I_g^2 120 + 15 I_g$$

$$1.2 I_g^2 - 15 I_g + 0.4 = 0$$

$$I_g = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

a = 120, b = -15, c = 0.4

$$\Rightarrow \frac{15 \pm \sqrt{(15)^2 - 4 \cdot 120 \cdot 0.4}}{2 \cdot 120}$$

$$\Rightarrow \frac{15 \pm \sqrt{225 - 192}}{240}$$

$$\Rightarrow \frac{15 \pm \sqrt{33}}{240}$$

$$\Rightarrow \frac{15 + 5.744}{240}$$

$$\Rightarrow \frac{15 + 5.744}{240}$$

$$\Rightarrow \frac{20.744}{240}$$

$$\Rightarrow 0.08643 \text{ or } 0.08644 \text{ A}$$

$$I_g = 86.43 \text{ mA or } 86.43 \text{ mA}$$

$$V_g I_g = 0.4$$

$$\Rightarrow V_g \cdot I_g = 0.4$$

$$V_g = \frac{0.4}{I_g} = \frac{0.4}{0.08644}$$

$$V_g = \frac{0.4}{0.08644} = 4.629 \text{ V}$$

$$V_g = 8.43 \text{ V}$$

Q2) ~~At the~~ circuit of a thyristor as a source for an SCR the gate cathode characteristic has a straight line slope of 150, for trigger source voltage of 15V. and Anomalous gate Power dissipation of 0.5W. compute the gate source resistance.

$$m = 150$$

$$\leq 5 > 15V$$

$$P_g = 0.5W$$

$$V = mX + C$$

$$V_g = -I_g R_S + \leq 5$$

$$V_g = 150 I_g$$

$$V_g^2 = 150 \times 0.5$$

$$V_g = \sqrt{65}$$

$$V_g = 8.06V$$

$$I_g = \frac{0.5}{8.06} \text{ A} \quad (\because P_g = V_g \cdot I_g)$$

$$I_g \leq 0.062 \text{ A}$$

$$= 62 \text{ mA}$$

$$V_g = -I_g R_S + \leq 5$$

$$8.06 = -8.06 R_S + 15$$

$$R_S = 111.93 \Omega$$

Switching characteristics of SCR:

It is the time variation of voltage across its anode and cathode terminals and the current through during the turn on and turn off process. There are two types of characteristics

- ① During turn on process
- ② During turn off process

It is also known as dynamic characteristics of SCR.

Switching characteristics of SCR during Turn on:

A forward biased thyristor is usually turn on by applying a the gate voltage. Time is however a transition time forward off state to forward ON state. This transition time is called as turn on time. Thyristor is defined as the time during which it changes from forward blocking state to forward ON state or conduction state.

→ The turn on time of SCR comprises 3 different time intervals -

- (i) Delay time
- (ii) Rise time
- (iii) Spread time

Delay time (t_d)

The delay time is measured from the instant at which gate current reaches to 0.01 I_g to the instant at which anode current reaches 0.1 I_a. The final values of anode and cathode current respectively. There were the I_g and I_a are the final values of anode and cathode current respectively.

→ Other ways to define delay time is also defined as the time during which anode voltage falls from V_a to 0.9 V_a. Here V_a is the initial value of anode to cathode voltage when SCR was in forward blocking mode.

→ Another way to define it is the time in which anode current reaches to 0.1 Ia from forward leakage current.

→ The initiation of turn on process basically starts at gate to cathode junction. As soon as we apply gate current, charges are injected into the gate to cathode junction. This charge flows in a narrow path due to non-uniform charge distribution. Hence here the current density near the gate is more and decreases as the distance from gate junction increases. This means during the delay time the anode current flows in narrow region near gate where gate current density is highest.


(ii) RISE TIME: (tr)

→ It is defined as the time taken by the anode current to rise from 0.1 Ia to 0.9 Ia. At this time, the anode to cathode voltage drops from 0.9 Va to 0.1 Va.

→ Rise time is inversely proportional to the magnitude of gate current and its rate of rise. The more gate current, the lesser will be the rise time.


→ During rise time, the current starts to spread from a narrow ~~cathode~~ conducting region in the gate to cathode junction. Just as the rise time is small, the anodes current do not get a change to spread over the entire cross section of cathode.

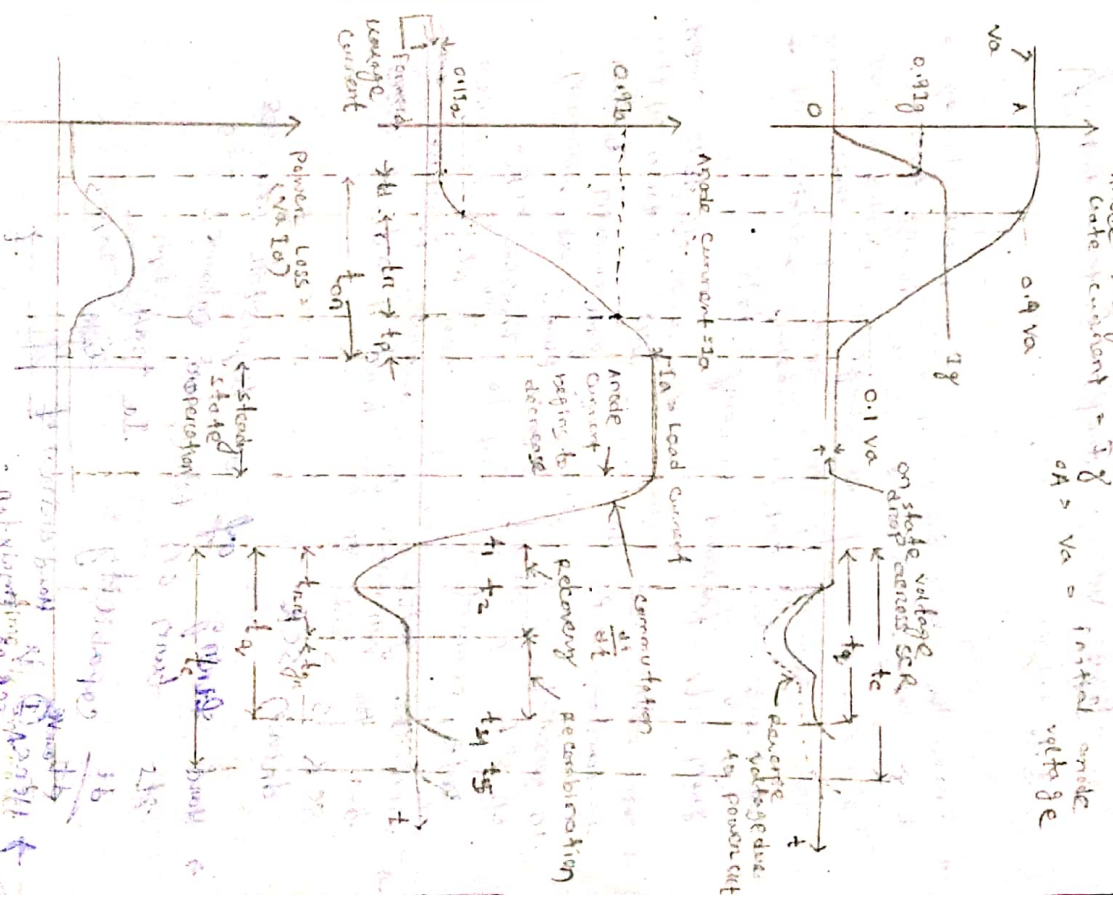The rise time also flows in a narrow region. The area of rise time narrow region is more than in case of delay time, since the voltage and current are more during rise time. The turn on losses is more during rise time.



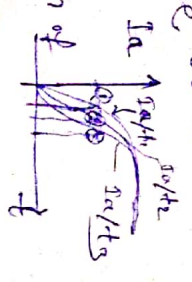1) Spread time (t_p)

- It is the time taken by anode current to reach 0.9I_a to I_a. During this time period, the anode current spread over the entire cross section of cathode.
- After the spread time, the anode current attains a steady state value and the voltage drop across the SCR terminals becomes equal to an stage voltage drop of the order of 1 to 1.5V.
- From the above discussion, we observe that an SCR is a charge controlled device. It is inserted by the A certain amount of charge is injected by the gate current in the forward conduction mode to bring the SCR in forward blocking state.
- This means the higher the value of gate current, the less the time will be taken to turn on SCR.
- In general, the magnitude of gate current to turn on SCR is about 3 to 5 times the minimum gate current required to trigger SCR.
- When the gate current is several times higher than the minimum gate current fixed on over SCR is said to be hard driven SCR.
- Hard driving of a thyristor reduces its turn on time and enhances its dI/dt capability.
- Hence, it is hand driven of SCR or thyristor.



2) Switching characteristics of SCR during Turn off :

- * Switching characteristics of SCR during turn off is the transition of SCR from forward conduction state to forward blocking state.
- * This transition process involves bringing the anode current below holding current, sweeping out of charges from anode p and n junction and recombination of holes and electrons at the junction, try to bring a dynamic process. This dynamic process of bringing SCR to off state is called commutation turn off process.
- * As we know that, once SCR is turned on, gate has no control over it, this means the SCR will continue to be in conduction state even if gate current is removed or kept zero. Now we want to turn off SCR.
- * We need to bring the anode current below holding current. But merely bringing current won't turn off SCR. The change in forward voltage is necessary. This is because holes and electrons are in equilibrium and if we apply forward voltage across anode and cathode, SCR will begin to conduct.
- * This means we need to apply a reverse voltage for some finite time. This time is called turn off time. This time is needed to sweep away carriers from anode p and n junction due to reverse voltage.

therefore these trapped charges must decay due to recombination.

This recombination is only possible if a reverse voltage is maintained across SCR for some finite time, through the magnitude of this reverse voltage is not important. This is because; the rate of recombination only depends on junction temperature. It is independent of external parameters.

The time for recombination of charge is called gate recovery time, t_{gr} . Here the gate recovery time is $(t_4 - t_3)$ At instant t_4 , as there is no excess charge, the SCR can withstand the forward voltage.

Hence we say that the thyristor turn off time is in the range of $3 - 100 \mu s$.

The SCR turn off time depends on the magnitude of anode current prior to starting of commutation.

process, di/dt and Junction temperature. As process, di/dt and Junction temperature increases, the thyristor turn off time.


However turn off time decreases with increase in magnitude of reverse voltage. This is because, high reverse voltage quickly sweeps out holes from p region and electrons from n-region. Thus turn off time of SCR is not a constant parameter. It is depends on the external circuit.

SCR forms a part of the external circuit. The external circuit becomes SCR turn off time. t_{gr} must be greater than t_{gr} for SCR to turn off.

Time t_{gr} defined as the time between the instant anode current crosses SCR terminals becomes greater than t_{gr} must be greater than t_{gr} for SCR to turn off.


Process of a thyristor: commutation is defined as the process of turning off a thyristor. To turning off a thyristor means bringing the device from forward conduction mode to forward blocking mode. Such time interval is called turn off time.

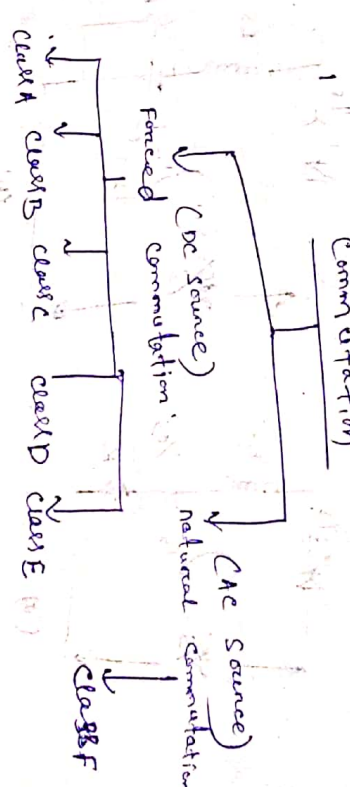There are two type of commutation process.




Class A commutation: load commutation or self commutation.

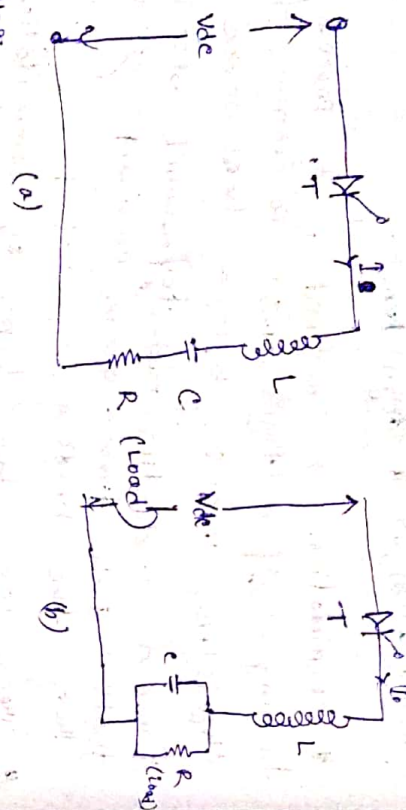It is also called as load commutation or self commutation. It is the A in which R, L, & C are arranged in a closed loop. Where $\omega L > R$ and $\omega C > 1/R$. Here the load commutating for low value of R, L and C resistance in series. For high value of R, L and C connected parallel across the capacitor 'C'.



According to Laplace transformation:

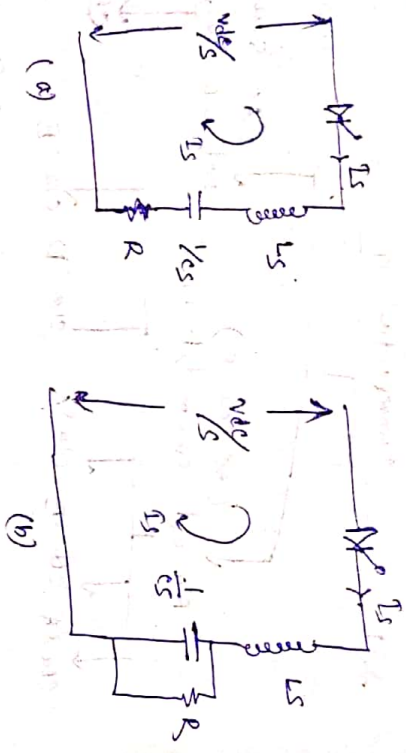

Applying KVL on fig. (a)...

$$\frac{V_{dc}}{s} - I_s L s - \frac{I_s}{C s} - I_s R = 0$$

$$\frac{V_{dc}}{s} = I_s \left(L s + \frac{1}{C s} + R \right)$$

$$I_s = \frac{\frac{V_{dc}}{s}}{L s + \frac{1}{C s} + R}$$

$$I_s = \frac{V_{dc}}{L \left(s^2 + \frac{1}{L C} + \frac{R s}{L} \right)}$$

$$I_s = \frac{V_{dc}}{L \left(s^2 + \frac{1}{L C} + \frac{R s}{L} \right)}$$

Current in time domain,

$$I(s) = \frac{V_{dc}}{L} \frac{1}{s^2 + \frac{1}{L C} + \frac{R s}{L}}$$

current in frequency domain,

$$I(s) = \frac{V_{dc}}{L} \frac{1}{s^2 + \frac{1}{L C} + \frac{R s}{L}}$$


we = damping frequency

To satisfy load commutation in a series R-L-C circuit.

$$\omega_n = \frac{1}{\sqrt{L C}}$$

$$\zeta = \frac{R}{2} \sqrt{\frac{C}{L}}$$

For parallel R-L-C circuit,
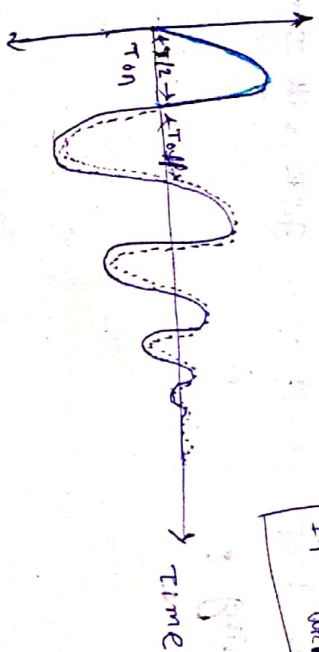
$$\zeta = \frac{1}{2R} \sqrt{\frac{L}{C}}$$


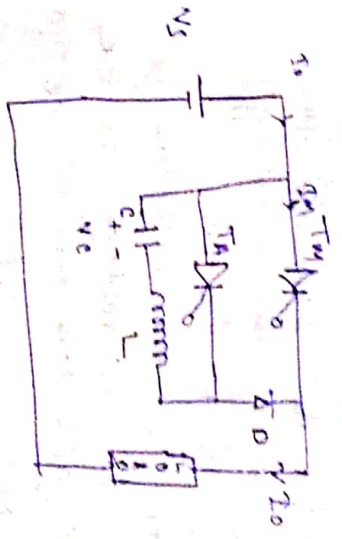
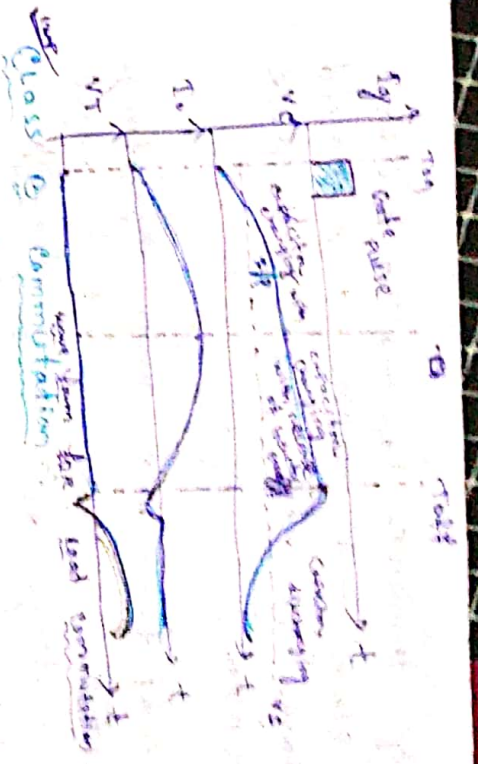
When we applied a dc supply to the SCR, the SCR will turn off. When we applied a gate pulse to the thyristor, then the thyristor will be turned on. Such time the current is greater than the latching current.

When thyristor starts to conducting the voltage across the thyristor is zero and current is I_0 . If the current rises to maximum value and then begins to fall.

In such state of SCR, the capacitor will charge and voltage across the capacitor reaches peak of supply input. Such time the inductive reactance stores energy and opposes the further flow of current.

A time will reach when the current becomes zero then SCR automatically turn off.

At this instant, now the capacitor starts to discharge and as the SCR gets turned off, so the drop across the SCR will start increasing.



It is also called resonant-pulse commutation or current commutation.

Assumption: load current is assumed to remain constant.

I_0 (i.e. load is highly inductive).

Capacitor is initially charged with V_s volts as shown in above figure.

At $t = 0$ sec, T_H is in ON state and $I_M = I_0$.


In the above circ.

T_M = main thyristor
 T_H = auxiliary thyristor
 D = diode

Step-1 Initially thyristor T_M and T_A are in off state and capacitor C is charged to voltage V_S with left hand plate positive as shown in fig.

Now, at $t=0$ the main thyristor is turned on. Load current is equal to I_0 steady to flowing through the main thyristor T_M and load.

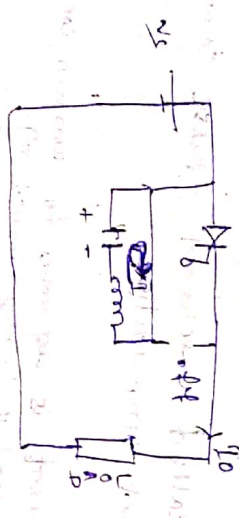Now we want to turn off the thyristor, we fire the auxiliary thyristor T_A at $t=t_{\text{thy}}$. Till the $t=t_m$, the capacitor is charged with source voltage V_S i.e. $V_C = V_S$. Capacitor current $i_C = 0$.



Now the capacitor discharges in the manner shown in above fig. The discharge current of capacitor

$$i_C = -I_0 \sin \omega t$$

I_0 is instantaneous value of discharge current

$I_{p.s}$ peak current
 $i_C = -I_0 \sin \omega t$
 when thyristor thyristor change a capacitor discharge, capacitor and polarity change


When discharge current decays to zero, the capacitor voltage reverses its polarity. Capacitor voltage is cosine wave when

$$i_C = I_0 \cos \omega t$$

At end of step 1, capacitor polarity, reverse and T_A turns off.

Step-2 In step-2, T_A turns off and Diode D turns on.

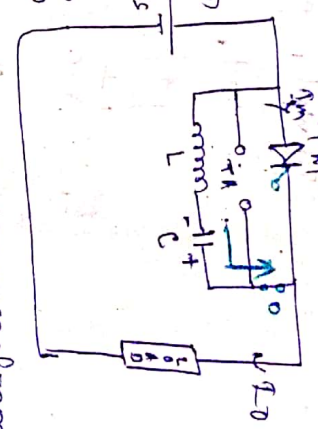Capacitor polarity has reversed. So when T_A turns off, capacitor voltage applied a forward bias across the diode. So the diode turns on.



Now the capacitor current increases from zero to I_0 .

Applying KCL

$$I_M + I_C = I_0$$

Here the load current I_0 is constant and capacitor current increase slowly.

Sum of capacitor current is constant. Main thyristor current increases continuously.

So as capacitor current increases, I_M decreases. Hence the capacitor current increases by the presence of inductor.

→ when the capacitor current reaches I_0 , then I_m becomes zero and main thyristor is turned off.

calculate the total time taken by I_m to turn off :-

Let time taken by capacitor current to reach I_0 after to time be t_1 .

T_m is off when $I_c = I_0$

Q. p. sign w.t. $= I_0$ $\left(\because I_c = I_p \sin \omega t \right)$
 $\left(I_p = \sqrt{V_c} \right)$
 $\left(\omega = \frac{1}{\sqrt{LC}} \right)$
 $\left(\omega = 2\pi f \right)$
 $\left(\text{resonant frequency} \right)$

sign w.t. $= \frac{I_0}{I_p}$

w.t. $= \sin^{-1} \left(\frac{I_0}{I_p} \right)$

$t_1 = \frac{1}{\omega} \cdot \sin^{-1} \left(\frac{I_0}{I_p} \right)$

$t_1 = \frac{1}{\sqrt{LC}} \cdot \sin^{-1} \left(\frac{I_0}{I_p} \right)$


$t_1 = \sqrt{LC} \cdot \sin^{-1} \left(\frac{I_0}{I_p} \right)$

t_1 is the time taken by T_m to switch off after to see.

So, total time taken by T_m turn off from instant T_A is turns on at f_{SO}
 $= t_0 + t_1 = \pi \sqrt{LC} + \sqrt{LC} \sin^{-1} \left(\frac{I_0}{I_p} \right)$

∴ total time taken by T_m to turn off
 $= \pi \sqrt{LC} + \sqrt{LC} \sin^{-1} \left(\frac{I_0}{I_p} \right)$

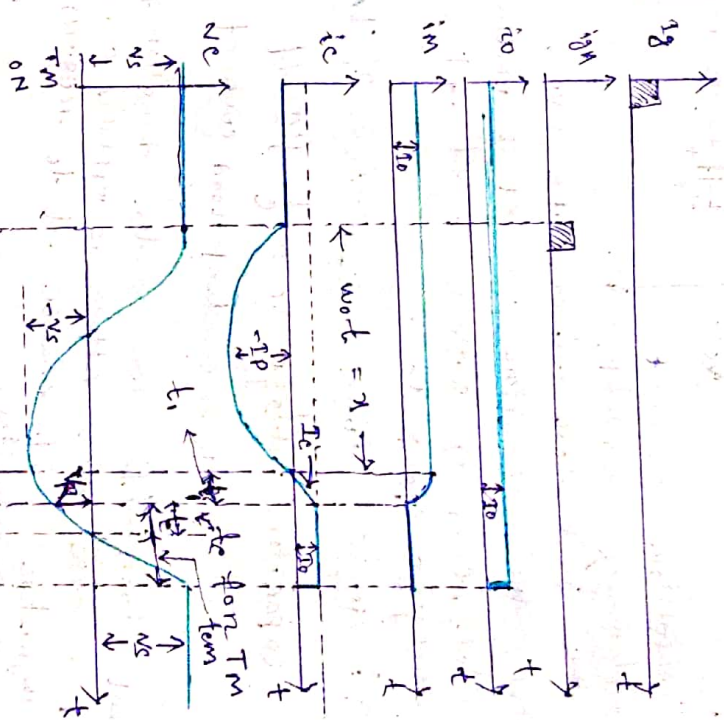
Conduction time of auxiliary thyristor
 $T_A = t_0 = \pi \sqrt{LC}$



step-3

T_m is turned off but we need to maintain reverse voltage across it to enable blocking capability. T_m reverse base voltage is maintained in step 3.

* when $I_c = I_o$, T_m is turned off.

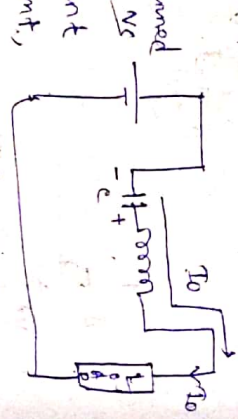

* Now capacitor current I_c remains constant, till the capacitor charges to $+V_s$.

* Now the capacitor current is no longer sinusoidal, read it suppressing it and maintaining constant I_o .

To find circuit turn off time of T_m :

capacitor voltage $V_c = \frac{1}{C} \int I_o dt$

$I_o = \text{constant load current}$

* circuit turn off time is the duration for which reverse bias voltage is applied across the thyristor to enable it to regain blocking capability.

* I_{Tm} the waveform, the term represents the circuit turn off time of main thyristor T_m .

* In the waveform, the value of reverse voltage which appears across the T_m , when it gets turned-off is V_R .

Now putting the value in the expression for capacitor voltage.

$V_c = V_R = \frac{1}{C} \int I_o dt$

$V_R = \frac{I_o \cdot C}{C} \cdot t_{em}$

$t_{em} = \frac{V_R \cdot C}{I_o}$

→ finding the value of V_{av}

→ capacitor voltage is a cosine function at time t_1

$V_R = V_C$

$= V_s \cos \omega t_1$

$V_R = V_s \cos \left\{ \sin^{-1} \left(\frac{I_o}{I_P} \right) \right\}$

$\therefore \omega t_1 = \sin^{-1} \left(\frac{I_o}{I_P} \right)$
 $I_P = V_s \sqrt{\frac{C}{L}}$


$t_{em} > V_R \frac{C}{I_o}$

$V_R = V_s \cos \left(\sin^{-1} \frac{I_o}{I_P} \right)$

$I_P = V_s \sqrt{\frac{C}{L}}$


$\omega t_1 = \sin^{-1} \frac{I_o}{I_P}$

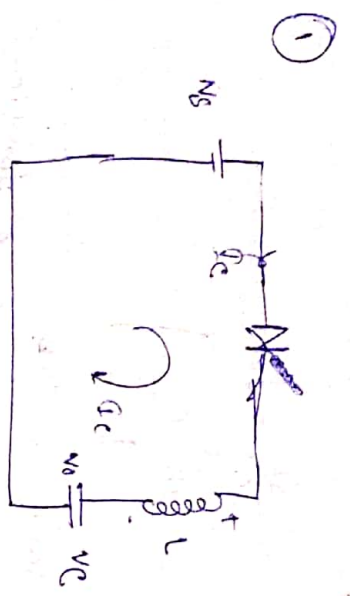* Another part
How to find i_c and v_c in RL
with Diode ckt.



V_0 = initial voltage of capacitor

Laplace form:

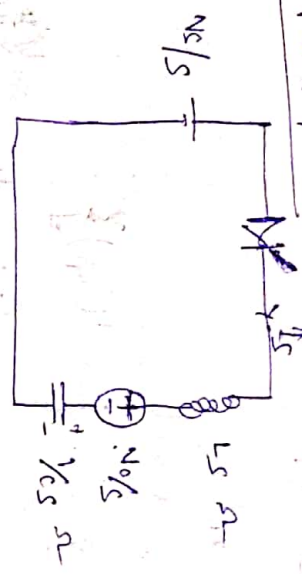

$$\frac{V_s}{s} - I_s Ls - V_0/s - I_s / cs = 0$$

$$\int_0^{\infty} i(t) \cdot e^{-st} dt$$

$$\frac{V_s}{s} - \frac{V_0}{s} = I_s Ls + I_s \frac{1}{cs}$$

$$\frac{V_s - V_0}{s} = I_s \left(Ls + \frac{1}{cs} \right)$$

$$I_s = \frac{V_s - V_0}{s} \times \frac{cs}{Ls \cdot cs + 1}$$

$$F(s) = \frac{c(V_s - V_0)}{Ls^2 + 1}$$

$$f(s) = \frac{c(V_s - V_0)}{L(s^2 + \frac{1}{Lc})}$$

$$f(s) = \frac{V_s - V_0}{L(s^2 + \frac{1}{Lc})}$$

$$\frac{V_s - V_0}{L} \cdot \left(\frac{1}{s^2 + \frac{1}{Lc}} \right) = I_s$$

$$\frac{V_s - V_0}{L} \left(\frac{1}{s^2 + \left(\frac{1}{\sqrt{Lc}}\right)^2} \right) = I_s$$

$$\Rightarrow \frac{V_s - V_0}{L} \left[\frac{\frac{1}{\sqrt{Lc}}}{s^2 + \left(\frac{1}{\sqrt{Lc}}\right)^2} \right] = I_s$$


$$\Rightarrow \frac{V_s - V_0}{L} \left[\frac{\sqrt{Lc} \times \frac{1}{\sqrt{Lc}}}{s^2 + \left(\frac{1}{\sqrt{Lc}}\right)^2} \right] = I_s$$

$$\Rightarrow \frac{V_s - V_0 \times \sqrt{\frac{c}{L}}}{L} (\sin \omega t) = I_s$$

$$L(\sin \omega t) = \frac{V_0}{s^2 + \omega^2}$$

$$\omega = \frac{1}{\sqrt{Lc}}$$
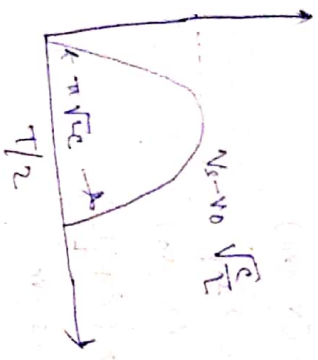
$$I_s = I_e \sin \omega t \quad \left(\sqrt{\frac{V_c}{L}} \times \sin \omega t \right)$$



$$T = \frac{2\pi}{\omega}$$

$$T/2 = \pi \sqrt{LC}$$

$$V_c = \frac{1}{C} \int I(t) dt$$

$$= \frac{1}{C} \int (I_p \sin(\frac{t}{\sqrt{LC}})) dt$$

$$\left[I_p = (V_s - V_0) \sqrt{\frac{C}{L}} \right]$$

$$= \frac{I_p}{C} (-\sqrt{LC} \cos \frac{t}{\sqrt{LC}})$$

$$= \frac{I_p}{C} (-\sqrt{LC}) \cos \frac{t}{\sqrt{LC}}$$

$$= \frac{V_s - V_0}{\sqrt{LC}} \sqrt{LC} (-\sqrt{LC}) \cos \frac{t}{\sqrt{LC}}$$



$$= -(V_s - V_0) \cos \frac{t}{\sqrt{LC}}$$

$$= V_s - V_0 \left(-\cos \frac{t}{\sqrt{LC}} \right) + C$$

$$V_c = -(V_s - V_0) \cos \omega t$$

$$I_c = (V_s - V_0) \left(\sqrt{\frac{V_c}{L}} \times \sin \omega t \right)$$

2

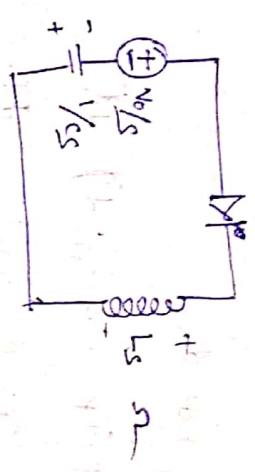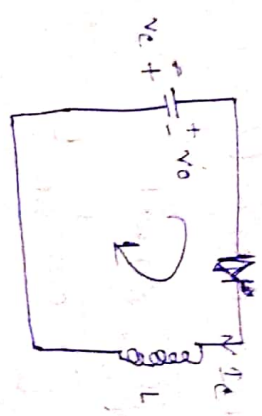

$$V_0/s - I_s R_s - I_s / cs = 0$$

$$\frac{V_0}{s} = I_s \left(R_s + \frac{1}{cs} \right)$$

$$\Rightarrow I_s$$

$$\frac{V_0}{s} \times \frac{cs}{Lcs^2 + 1}$$

$$I_s = \frac{V_0 c}{Lcs^2 + 1}$$

$$I_s = \frac{V_0 c}{L(c^2 + \frac{1}{Lc})}$$

$$I_s = \frac{V_0}{L} \left(\frac{1}{c^2 + \frac{1}{Lc}} \right)$$

$$V_0 \left(\frac{\frac{1}{\sqrt{L}} \times \sqrt{L}}{s^2 + \left(\frac{1}{\sqrt{L}}\right)^2} \right)$$

$$\frac{V_0}{L} \sqrt{L} (\sin \omega t)$$

$$= \frac{V_0 \sqrt{L}}{L} \sin \omega t$$

$$I_s = \frac{V_0 \sqrt{L}}{L} \sin \frac{1}{\sqrt{L}} t$$

$$V_c = \frac{1}{C} \int I dt$$

$$= \frac{1}{C} \int \left[\frac{V_0}{L} \sin \left(\frac{1}{\sqrt{L}} t \right) \right] dt$$

$$= \frac{1}{C} \frac{V_0}{L} \int \sin \frac{1}{\sqrt{L}} t dt$$

$$= \frac{V_0}{C} - \sqrt{L} \cos \frac{1}{\sqrt{L}} t$$

$$= \frac{V_0}{C} - \sqrt{L} \cos \frac{1}{\sqrt{L}} t$$

$$= -\frac{V_0}{C} \sqrt{L} \times \sqrt{L} \cos \frac{1}{\sqrt{L}} t$$

$$V_c = -V_0 \cos \frac{1}{\sqrt{L}} t$$

$$V_e = I_s = \frac{V_0 \sqrt{L}}{L} \sin \omega t$$

$$V_c = -V_0 \cos \omega t$$

Class E commutation:


It is also known as natural commutation or line commutation. because the SCR is turned off automatically during negative cycle of alternating supply.

There are no commutating components used in this method therefore it is not called as forced commutation.

The time duration for the negative half cycle must be greater than the SCR specified turned off time.

This method is applicable only for alternating supply.

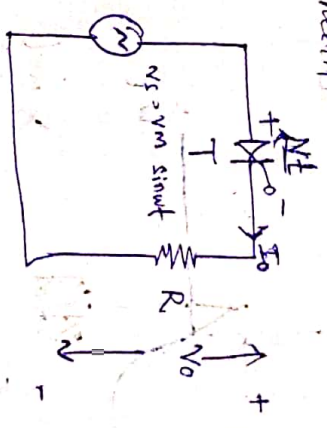Applications: This method is used in the line commutator inverters, and cyclo-converters.




When supply is AC, then anode current through the thyristor automatically pass through zero at the end of every positive half cycle i.e. at $\omega t = \pi$. Such time of conduction and the voltage thyristor will be thyristor $\omega t = 0$.

When it is -ve half cycle $V_s = -V_f$.

So anode current becomes zero after positive half cycle.

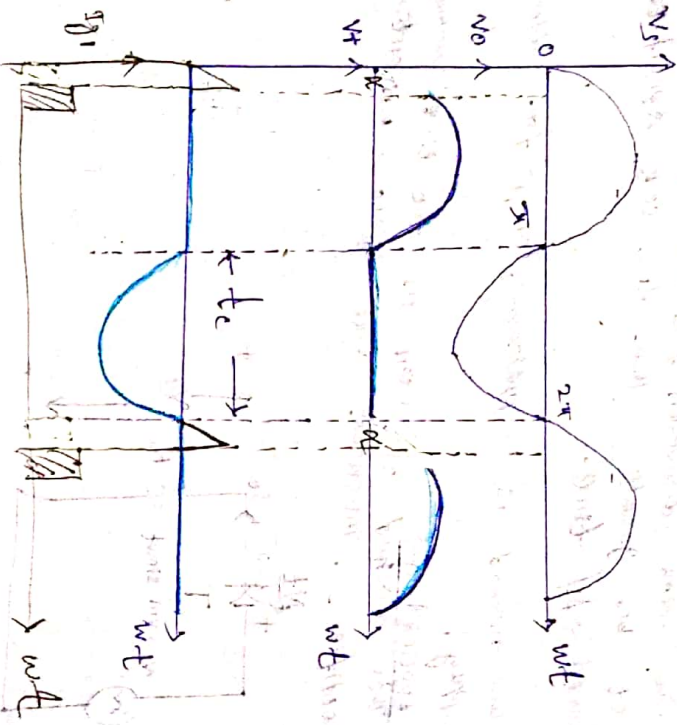If the supply voltage also applies a reverse bias voltage across the SCR, in the negative half cycle. This reverse bias ensures that SCR regains its blocking capability.




See firing circuits

Some of the various triggering methods on the SCR, gate triggering, instant of SCR efficient and reliable with gate triggering turning on is possible with various firing methods. Some of various firing methods of SCR.

- * Resistance firing ckt.
- * R-c firing ckt.
- * UJT pulse trigger ckt. or firing ckt.

Resistance Firing circuit:-

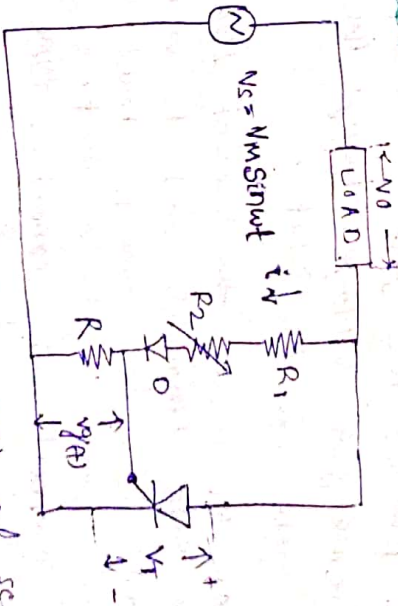

- * The resistance triggering of SCR where it is employed to drive the load from the input AC supply.
- * Resistance and diode combination ckt acts as a gate control ckt. to switch the SCR in the desired condition.
- * As the +ve voltage applied, the SCR is forward biased and does not conduct until its gate current is more than minimum gate current of the SCR.

When the gate current is applied, by varying the resistance R_2 such that the gate current should be more than the minimum value of gate current, the SCR is turned ON. AND the load current starts to flowing through the SCR.

When the gate current is applied


The SCR remains ON until the anode current is equal to the holding current of the SCR. And it will switch off when the voltage applied is zero. So the load current is zero as the SCR acts as open switch,

The diode protects the gate drive CRT from reverse gate voltage during the -ve half cycle of the input.

And resistance R_1 limits the current flowing through the gate terminal and its value is such that the gate current should not exceed the maximum gate current.

It is the simplest and economical type triggering but limited for few application due its disadvantages.

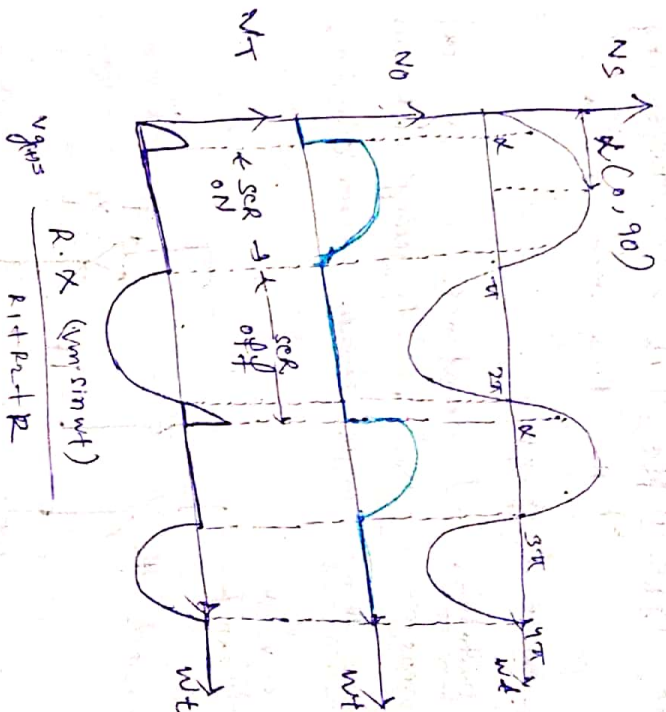In this, the triggering angle is limited to 90° degrees only, because the applied voltage is maximum at 90° degrees. So the gate current has to reach minimum gate current value somewhere between zero to 90° degrees.




$$V_{avg} = \frac{R \times V_m}{R_1 + R_2 + R}$$

If R is more, α is high
 If R is less, α is low
 Range of α (firing angle) is between 0° to 90° .

Re firing circuit:

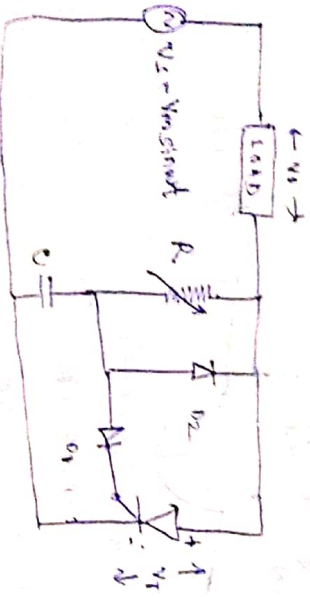- 1. It is two type ① Re. half-wave trigger ckt
- ② Full-wave

① Re half wave firing ckt
 The limitation of resistance firing ckt can be overcome by the re triggering ckt which provides the firing angle control from 0 to 180° .




In re ckt by varying the value of R_f , firing angle can be controlled from 0 to 180° . In the negative half cycle, capacitor charges through D_2 with lower peak voltage v_m of $wt > -90^\circ$. After $wt = -90^\circ$, source voltage v_s decreases from $-V_m$ at $wt = -90^\circ$ to zero at $wt = 0^\circ$. During this period the capacitor voltage v_c may fall from $-V_m$ at $wt = -90^\circ$ to some lower value $-V_c$ at $wt = 0^\circ$.
 $V_c \approx -V_m$


During positive half cycle of the input, the SCR becomes forward biased and now the SCR anode voltage passes through zero and becomes positive. The capacitor starts charging through variable resistance with upper plate positive & lower resistance. When the capacitor charges to positive voltage equal to gate trigger voltage V_{gt} , SCR is turned ON and capacitor holds a small voltage.

When the capacitor voltage is helpful for triggering the SCR even after 90° degrees of the input wave from.

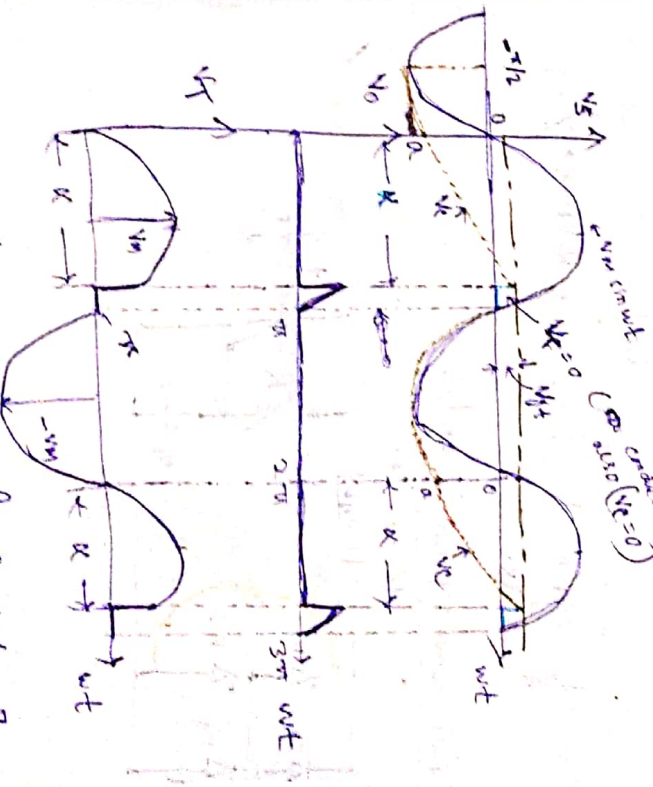In this, diode D_1 prevents the -ve voltage between the gate and cathode, during the -ve input through diode D_2 .



[High value of Resistance]

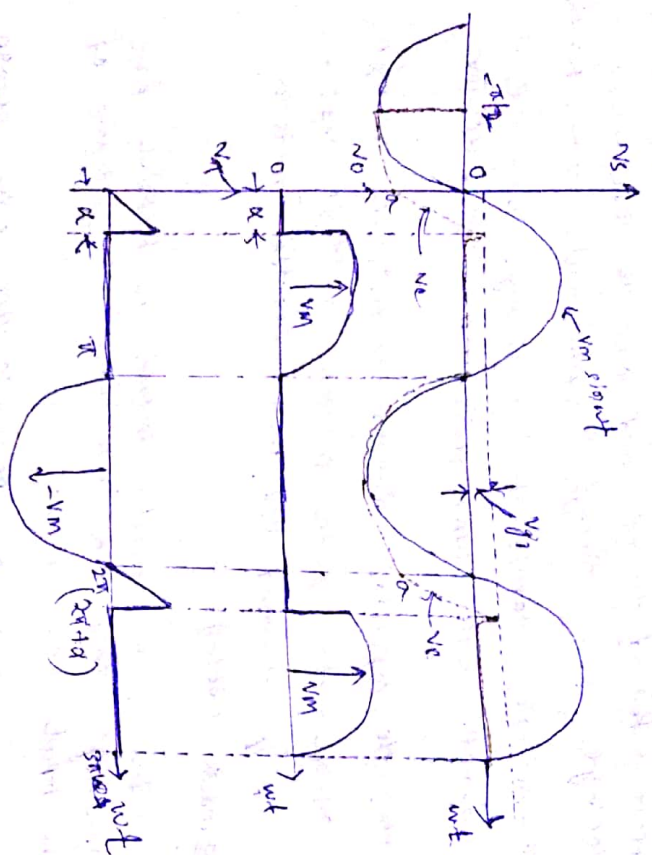


Low value of resistance

$$R \geq \frac{1.3T}{2} \approx \frac{1}{W}$$

$T = \frac{1}{f}$ = period of ac line frequency in seconds.

③ RC full wave firing circ.:

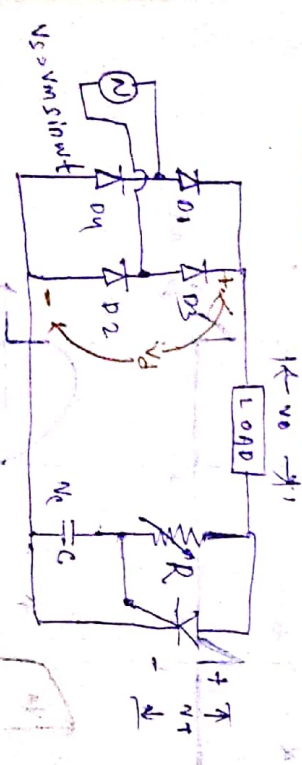

If there the AC voltage is converted into full wave diode bridge.

They allow the SCR to triggered on for both half cycle the line voltage, which doubles the available power to the load.

Hence Diode D1-D4 form a full wave diode bridge. Hence the initial voltage from which capacitor v_c changes is almost zero.

The capacitor v_c is set to this low positive voltage (intra plate positive) by the clamping action of SCR gates.

If when the capacitor charges to v_gt, SCR triggers on and rectified voltage v_d across load as v_o.


If the value of RC calculated from following relation

$$RC \geq 50T = \frac{1.5T}{W}$$

($T = \frac{1}{f}$) Firing angle alpha is more than




90° (high value of R) ~~90°~~
~~alpha < 90°~~ (Low resistance)

Scanned with CamScanner

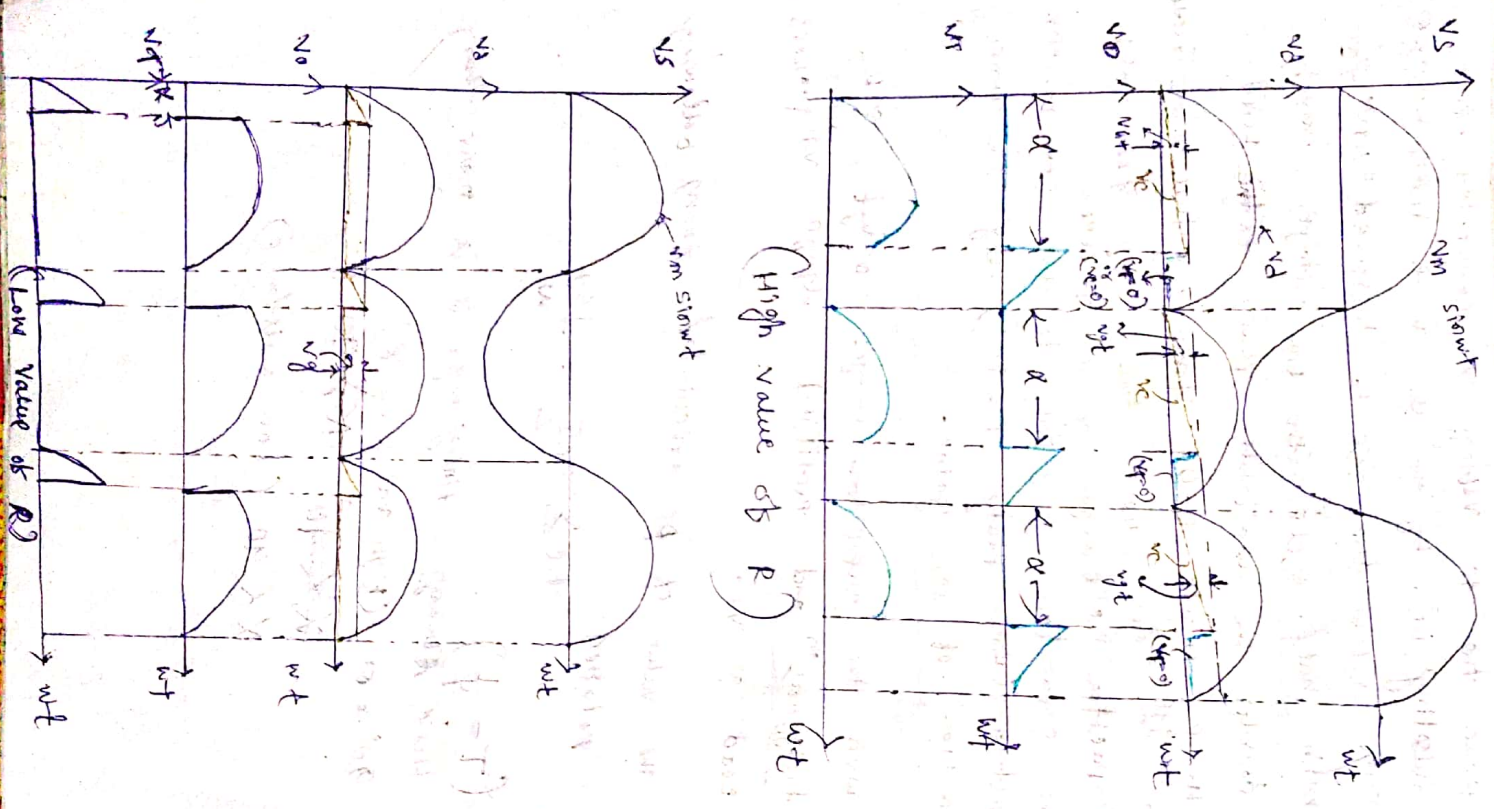

UJT :-

uni Junction transistor

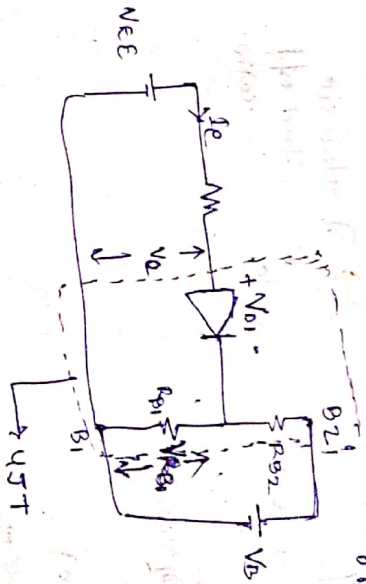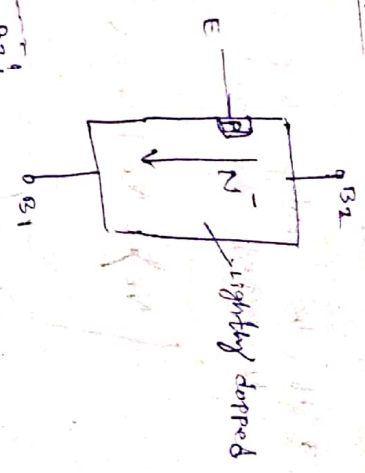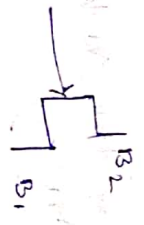

$R_{B1} \rightarrow$ the resistance between E - B₁ Junction

$R_{B2} \rightarrow$ the resistance between E - B₂ Junction



$$V_{E1} = V_{EB} \left(\frac{R_{B1}}{R_{B1} + R_{B2}} \right)$$

$$\left[V_E > V_{EB} \times \frac{R_{B1}}{R_{B1} + R_{B2}} \right] \rightarrow \text{In 'seal' Base is}$$

try it conduct (UJT)

To conduct the diode. N_E should be greater than N_{B1} .

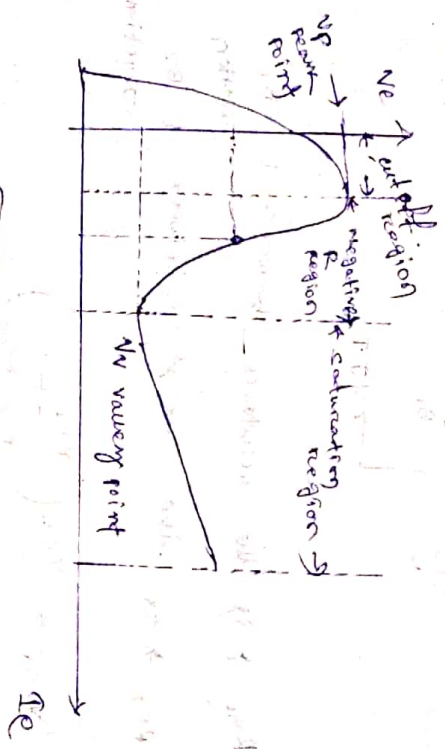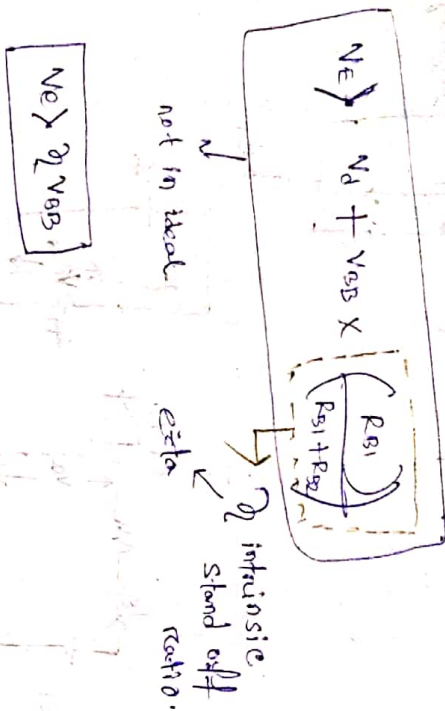If the voltage drop across the diode N_A then to conduct the diode $N_D \gg N_{B1}$.



$$N_P = 2 V_{DS} + V_D$$

If in the cut off zone current through the diode. In $-V_E$ and after $I_E = 0$, current in $+V_E$ and voltage V_E will gradually increase upto the peak point.

$$I_D = \frac{V_{S1}}{R_{S1} + R_{E2}}$$

As the diode gets forward biased, the voltage across it will be 0.7V. So, this is constant and V_{S1} goes on decreasing. It decrease hence V_E goes on decreasing. At least V_E called valley voltage. N_V resistance. as I_E will increase the voltage V_E will reduce because of R_{S1} will decrease.

$$R = R_0 (1 + \alpha I)$$

$$\alpha \uparrow \rightarrow R \downarrow \quad [R \text{ will be } -ve]$$

The voltage V_E will decrease upto valley voltage. V_E after that the UJT will enter into saturation zone, where it behaves like a diode as the current will increase voltage V_E also increase in the saturation zone.

Application of UJT -?


Its application as relaxation oscillator.

$$N_E > V_T + (V_{DS} - V_{DS}) e^{-\frac{t}{\tau}}$$

$N_0 = V_0$ = initial voltage of capacitor

$N_{DS} > V_T >$ Final voltage of the capacitor

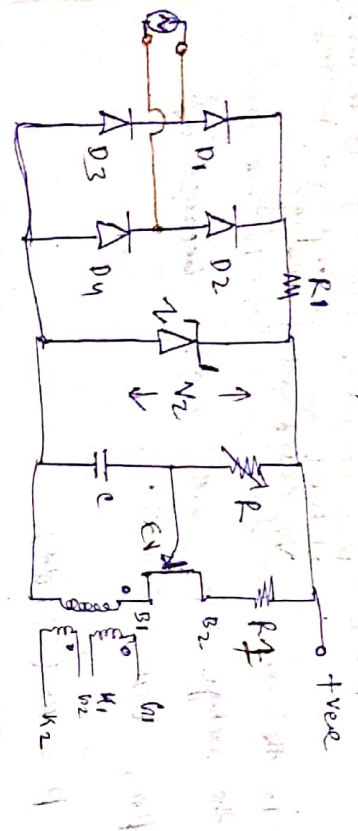UJT Triggering Ckt :- of synchronized UJT triggering ckt



$E B_2$ = Forward biased
 $E B_1$ = Reverse biased

- The unijunction transistor UJT have 3 terminal device i.e. Emitter, base 1 & base 2.
- It consist of lightly doped N-layer as base and P-layer heavily doped P-type inside it.
- The load is wire welded to the 3 layers.
- So, there are 2 junctions.
- $E B_1$ & $E B_2$ junction acts as resistance.
- This 2 junctions are acts as resistance i.e. R_{E1} & R_{E2} .
- The emitter leads is placed nearer to the R_{E2} leads so the $E B_2$ junction is in forward biased as the B_1 leads is away from E so $E B_1$ junction is reverse biased.
- At $E B_1$ junction is break the conduction start through UJT.

The above ckt shows UJT diode (D_1, D_2, D_3, D_4) acts as rectifier which convert A.C to D.C & VDC applied across the UJT.

A zener diode connected across the ckt to maintain the constant voltage and also clip the rectified voltage. To a standard level V_Z & a variable resistance R_1 & a capacitor C acts as P-C charging ckt used for charged the capacitor C .


The variable resistance (R_1) & capacitance (C) acts as R-C charging ckt used for change the capacitor (C).

By variable resistance (R_1) we control the firing angle α i.e. it R value is high they capacitor takes more time to charge hence α increase.

Nice sense.


When the capacitor charge reaches to 'V' which is acts between E & B_1 result the breaking of junction.

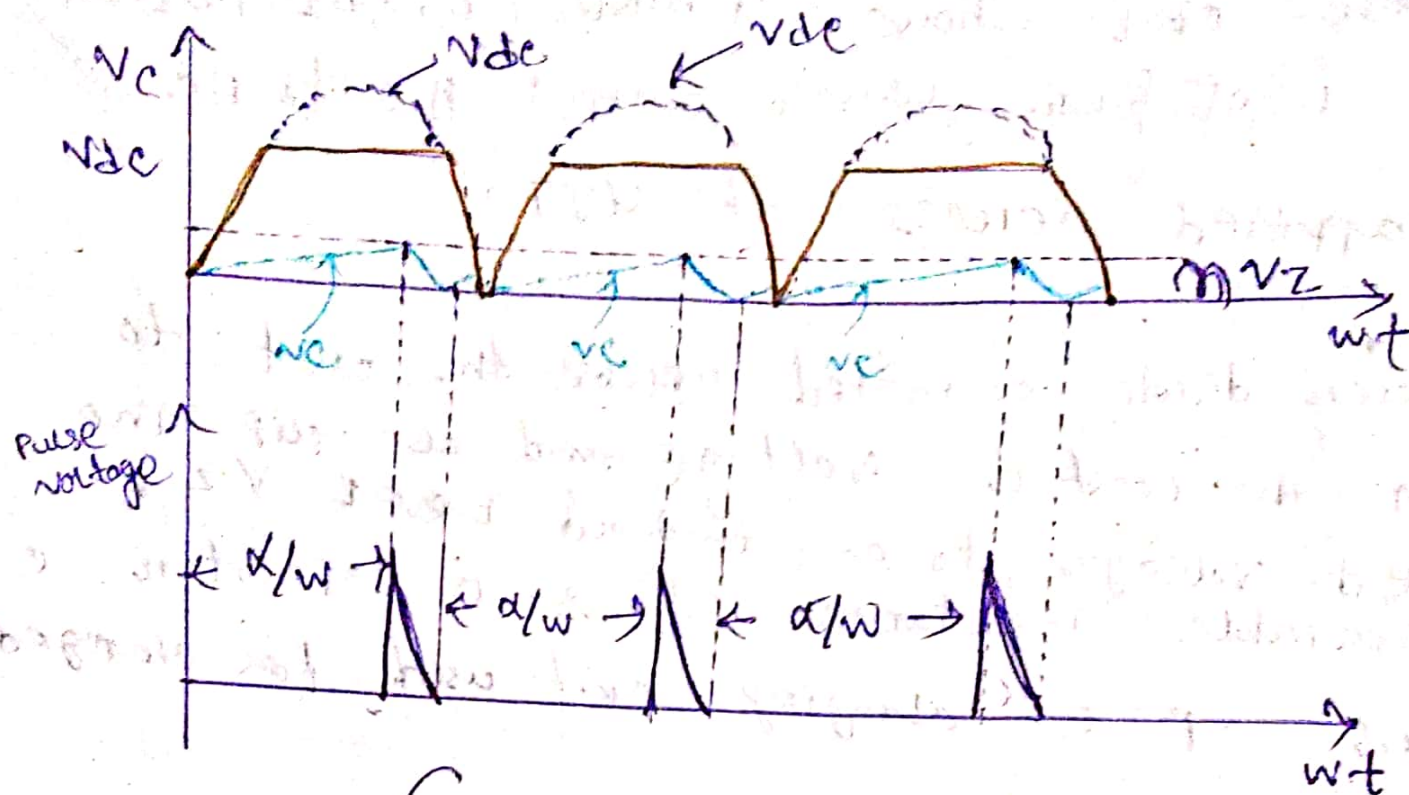As a result current I_2 flowing through R_1 & $R_2 \rightarrow E \rightarrow B_1$ & the pulse transformer. The pulse transformer shows transmission to the secondary and voltage applied to the thyristor circuit.



(High resistance)

Snubber circuits:-

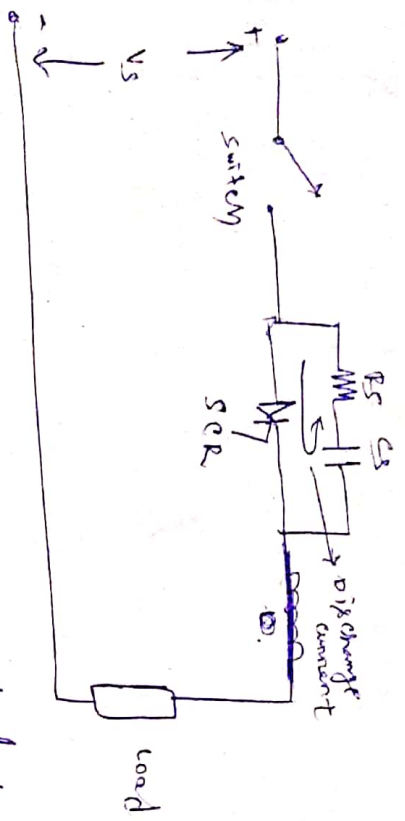

It is circuit which is protect to the ~~SCR~~ circuit.

Snubber ext consist of resistance R_S and capacitance C_S in parallel. with the thyristor.

To prevent the unwanted dv/dt triggering of SCR.

working of snubber ext:-

Role of capacitor C_S :-

When the switch S is closed, a sudden voltage appears across the circuit. capacitor does not allow the sudden change in voltage.

Initially capacitor C_S behaves like a shorted path and hence the voltage across SCR is zero and also capacitor across is zero.

But as time passes, voltage starts building up across capacitor C with a slow rate.

Thus the rate of rise of voltage dv/dt across SCR terminals will also be slow and less than the specified dv/dt rating of SCR.

Role of resistance R_S :-

Before SCR is triggered by gate pulse, the capacitor C_S is fully charged to supply voltage V_S .

When SCR is turned on by gate pulse, this charged capacitor C_S discharges through

SCR.

Hence, a current having magnitude V_S / R_S of loop formed by SCR and capacitor C_S flows in the local path formed by SCR and capacitor C_S .

Since the value of resistance of this local path is quite small.

The magnitude of discharge current will be quite higher.

This will lead to high value of dv/dt which may exceed the specified dv/dt rating of SCR.

In order to limit the magnitude of the discharge current resistance should be connected in series with the capacitor.

Selection of R_s , r_{cs} and Load Parameters

Resistance R_s , capacitance r_{cs} and load parameters are so chosen that the dv/dt during charging capacitor C is less than the specified dv/dt rating of SCR.

The discharge current at the turn on of SCR is less than the specified di/dt rating.

Normally R_s , r_{cs} and load parameters forming an underdamped ext so that dv/dt is limited to acceptable value as provided by the SCR rating.

Protection of SCR:-


Protection of a device is an important aspect for its reliable and efficient operation.

SCR may face different type of fault during over voltage and over current, ^{transient} type of voltage

There are different type of protection given below

- ① over voltage protection
 - ② over current "
 - ③ High dv/dt "
 - ④ High di/dt "
 - ⑤ normal R_{th} "
 - ⑥ gate protection
 - ⑦ over voltage protection:-
- The thyristor subjected to over voltage due to

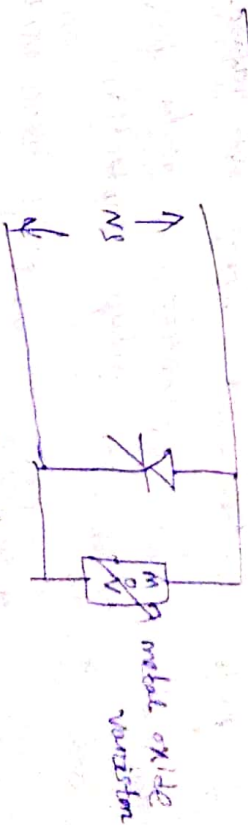- ① bad commutation (turn off)
 - ② short ext condition. clearing by ext breaker.
 - ③ transient due to switching operation
 - ④ lightning strike.
- clearing of over voltage:-



Non-linear resistor R_s working resistance R_{on} low voltage
 Non-linear resistor R_s working resistance R_{off} high voltage
 Low resistance for high voltage

(I) For protection of thyristor from over voltage a non-linear metal oxide varistor connected parallel with thyristor to be protected.

(II) This protective device have falling resistance characteristics with increase in voltage.

(III) At normal operating condition MOV show high resistance, so load current slow through thyristor.

(IV) When over voltage condition arises at that time MOV often low resistance which produce a short cut across thyristor and high voltage surge discharge the MOV & protect the SCR from over voltage.


(V) Generally MOV is selenium thyristor diode one used for over voltage protection.

MOV is made up of ceramic mass of zinc oxide grains & +

② over current protection:-

a. are thyristor subjected to over current due to short cut condition of only two lines, lightning stroke.

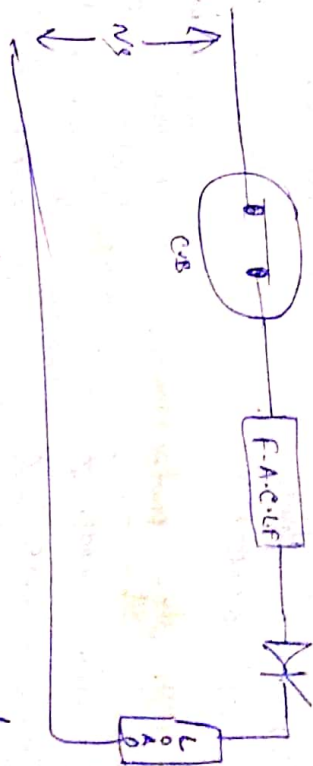b. sudden increasing of loads
 c. line to ground faults.



F.A.C.L.F → First acting current limiting fuse.

During over current a heavy current pass through thyristor have some resistance (0.25Ω) AS the junction across the device due to heat produced in more time.

It produced if it circulate in more time a 22Rt is it standing capacity of

The temperature with standing a high a of SCR is very small it a over current temperature develops due to over current many damage device.


* So to protect the SCR from over current a CRT breaker & FALF are connecting in series with thyristor.

* The circuit breaker is used to protect the thyristor against continuous over load for a long duration.
 * The FALF is used to protect the thyristor from over current for short duration.

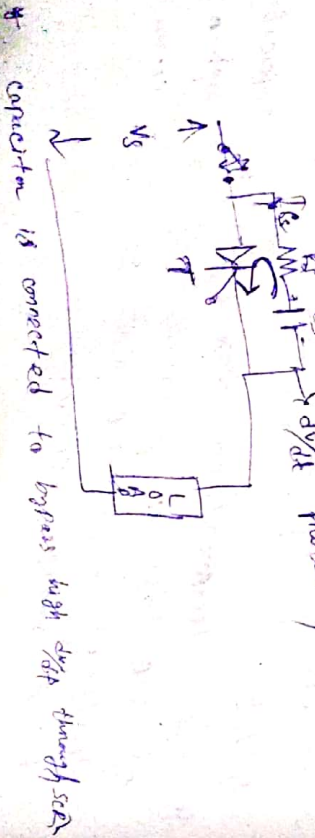(3) High $\frac{dv}{dt}$ protection:- (rate of change of voltage w.r.t time)

* When anode is the w.r.t cathode & no gate pulse is applied in behaves like a capacitor & the total source voltage is appears across V_{T2} junction.

* High $\frac{dv}{dt}$ may result into false turn on of SCR.
 * To provide $\frac{dv}{dt}$ protection we connect snubber CRT.




* Result a changing current start flowing if $\frac{dv}{dt}$ value is high, the I_C value is high which is able to turn on the SCR without giving any gate pulse.

* This is known as false operation of SCR which is called $\frac{dv}{dt}$ turn on.
 * The I_C is parallel with device to prevent unwanted $\frac{dv}{dt}$ triggering, & R_S also connected in series with C_S to limit the changing in current.

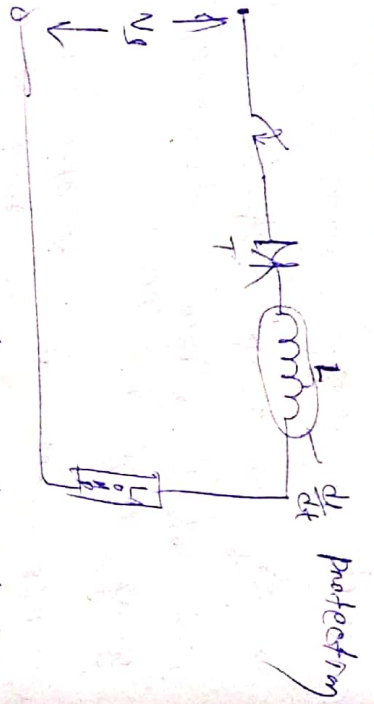(4) High $\frac{di}{dt}$ protection:-


* $\frac{di}{dt}$ is rate of change of current in device.
 * When SCR is in forward bias, and it is on by gate signal, there will be flow of anode current, anode current requires some time to spread inside device.
 * The anode current velocity of change in the I_C that may create hotspot & won't create SCR damage.
 * So, to maintain $\frac{di}{dt}$ through SCR we connected inductor in series to the SCR.




∴ Voltage across inductor can be calculated

by $V_s = L \frac{di}{dt}$

$\Rightarrow L = \frac{V_s}{di/dt}$

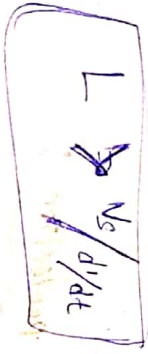


5) Thermal protection -
H.S. (Heat Sink)

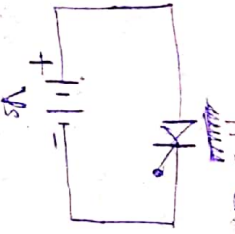


∴ when increase the leakage current near the junction T_2 with the increase in the temperature of the junction. insulation may get failed. So we have to take a proper measure to limit the temperature rise.

∴ this can be achieved by mounting the transistor on heat sink which is made by high thermal conductivity metals like Aluminium (Al), copper (Cu) etc. mainly aluminium is used due to its low cost.

6) Gate protection :-

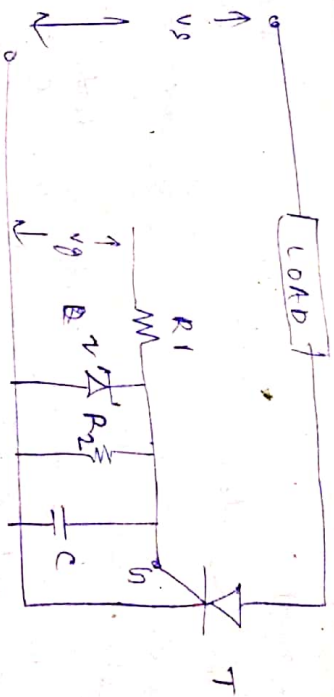

or

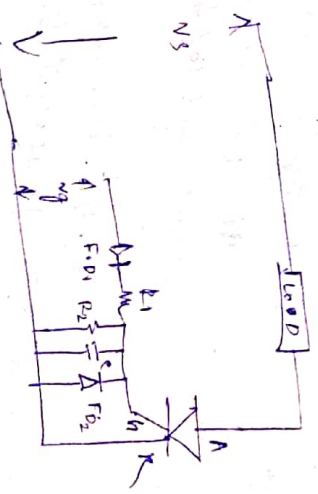

f.o = free wheeling diode.

4. For turn on the SCR by gate ckt method we applied gate pulse between gate & cathode. So the necessity gate pulse is given to gate terminal in a control method.

5. For giving gate pulse in control manner we used different ckt elements which are connected in the above diagram.

6. In the starting of the ckt a free wheeling diode is connected in series with the supply for allow only the pulse.

7. The R_1 connected series the diode which will limiting the current in safe value.

8. Another resistance R_2 connected parallel with gate & cathode.


9. For increasing the capability of the SCR for reducing the holding and latching current.

10. And increasing the high frequency component by connecting parallel inductance.

11. capacitor 'C' removes high frequency component by filter ckt.

12. The diode for avoids the flow of the -ve pulse from cathode to gate.

Total Protection ckt of SCR:

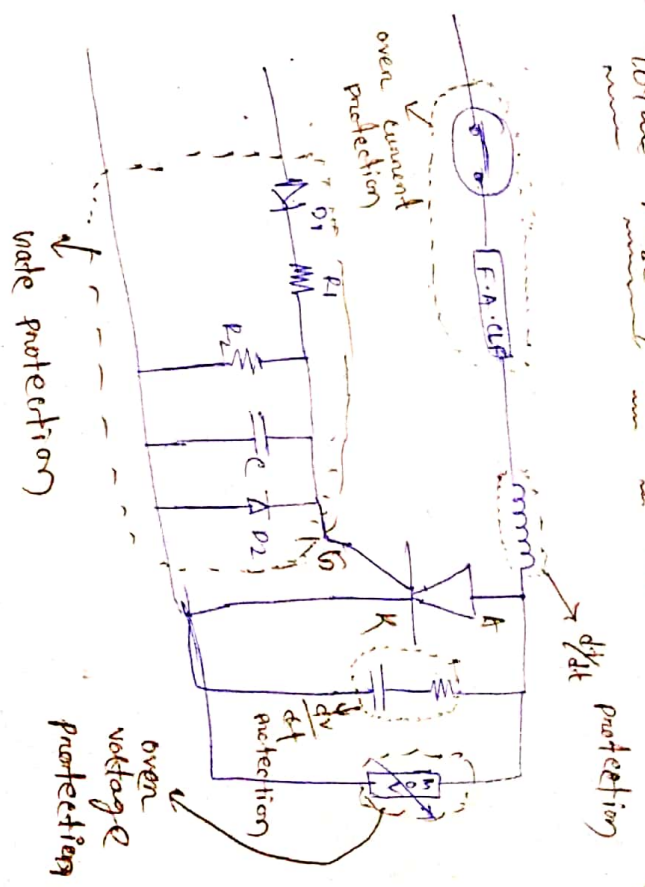

and Phase controlled Rectifier / Rectifier

As the conversion of AC to DC is known as converter.

For power ckt on power conversion ckt is from AC to DC. we use thyristor in place of diode.

There are two types of rectifier

- 1) controlled rectifier
- 2) un-controlled

1) controlled rectifier:- thyristor known as

control rectifier because thyristor is a control device.

we o/p can be vary by varying the firing angle.

hence o/p value of diode also vary. since it is a control device. it is available in high current, high voltage, high power rating.

it may be either 1 ϕ or 3 ϕ ac i/p.

it may be either semi-converter or fully converter having different quadrant operation.

2) un controlled rectifier:-


in case of un controlled rectifier because the value of AC voltage converted into fixed value of DC voltage.

Diode voltage:

it is used increase of some low power device where control of o/p voltage is not required.

it is low cost and simple ckt.

Classification of converter:-

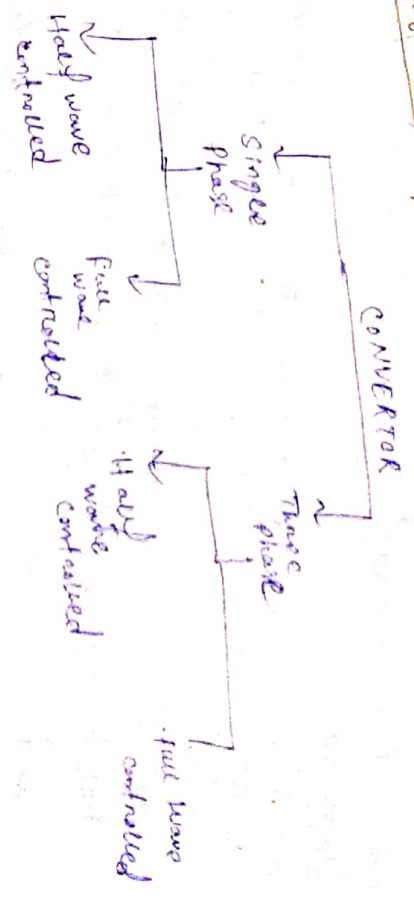



Application of converter

- (i) For high voltage D.C transmission.
- (ii) speed control of DC motor.
- (iii) DC use used for battery charging.
- (iv) magnetic power supply.
- (v) Excitation control of alternator.

Working Principle of converter:

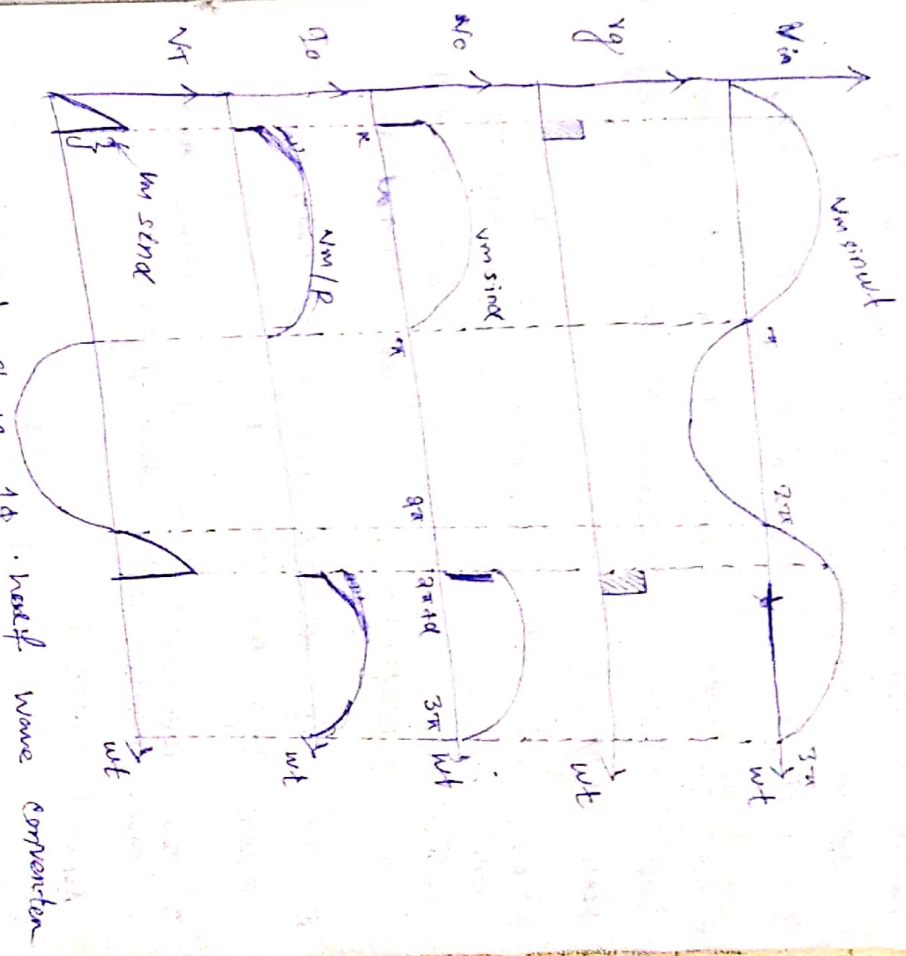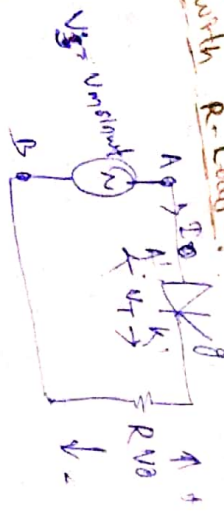- (i) A SCR can only conduct when anode voltage is +ve & cathode is -ve & Gate signal is applied.
- (ii) The load element blocks upto it is not triggered.
- (iii) When we applied gate pulse with some delay angle / firing angle (α). It would start conducting.
- (iv) So a thyristor may conduct during the half cycle i.e. $\alpha - \pi$, $2\pi + \alpha - 3\pi$ and so on.
- (v) If thyristor is replaced by a diode then it conduct $0 - \pi$, $2\pi - 3\pi$ & so on.
- as it is uncontrolled device.
- So by varying the firing angle α of thyristor which a vary rough o/p voltage as per requirement.

AC half wave control rectifier or converter with R-load:



The above circuit shows a half wave conversion with R-load.

The SCR is connected to a load resistance 'R' & the SCR is fed by a.c. supply $V_s = V_m \sin \omega t$ which is forward biased when the +ve half cycle appears across it i.e. $0 - \pi$.

So the SCR is forward biased when the +ve half cycle appears across it i.e. $0 - \pi$ and $2\pi - 3\pi$ and so on.

During the half cycle A-point is +ve, & point is -ve & the thyristor is subjected to forward bias.

As soon as gate pulse is given with firing angle α , it starts conducting and off voltage appears across the load.

So it is conduct upto $\alpha - \pi$ & $2\pi - \alpha + \alpha - \pi$.

When the cycle appears of π and $-\pi$ of SCR subjected to reverse biased conduction and hence it is off.

It and again able to trigger when the cycle seen again. It so by the conduction of SCR eliminate -ve half cycle and off seen in pulsating dc or unidirectional a.c.

The off voltage seen across load is given by the $V_o = I_o R$.
The displacement of current & voltages curve are shown in the above fig.

Average value:-

$$V_o = \frac{1}{2\pi} \left[\int_0^{2\pi} V_m \sin \omega t \cdot d\omega t \right]$$

$$\int_0^{\pi} V_m \sin \omega t \cdot d\omega t + \int_{2\pi}^{\pi} V_m \sin \omega t \cdot d\omega t$$

$$= \frac{1}{2\pi} \int_0^{\pi} V_m \sin \omega t \cdot d\omega t$$

$$= \frac{V_m}{2\pi} (-\cos \omega t) \Big|_0^{\pi}$$

$$= \frac{V_m}{2\pi} (-\cos \pi - \cos 0)$$


$$V_o = \frac{V_m}{2\pi} (1 + \cos \alpha)$$

$$I_o = \frac{V_o}{R} = \frac{V_m}{2\pi R} (1 + \cos \alpha)$$

When $\alpha = 0$, $I_o = \frac{V_m}{2\pi R} (1 + 1) = \frac{V_m}{\pi R}$ (Average value)
When $\alpha = \pi$, $I_o = \frac{V_m}{2\pi R} (1 - 1) = 0$ (Average value)

When load have inductive then the resistance & inductance will be by source.

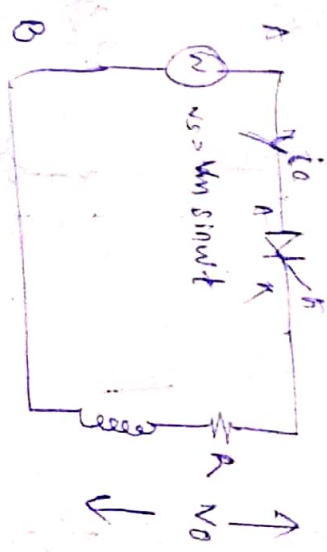
Induction has a property which does not allow sudden change of current i.e. either increasing or decreasing. Induction is according to the current vary across inductor is according to exponential.



operation:-

The above cut diagram show semi-converter or 1 ϕ half wave converter with R-L load, so it conducts only during the cycle.

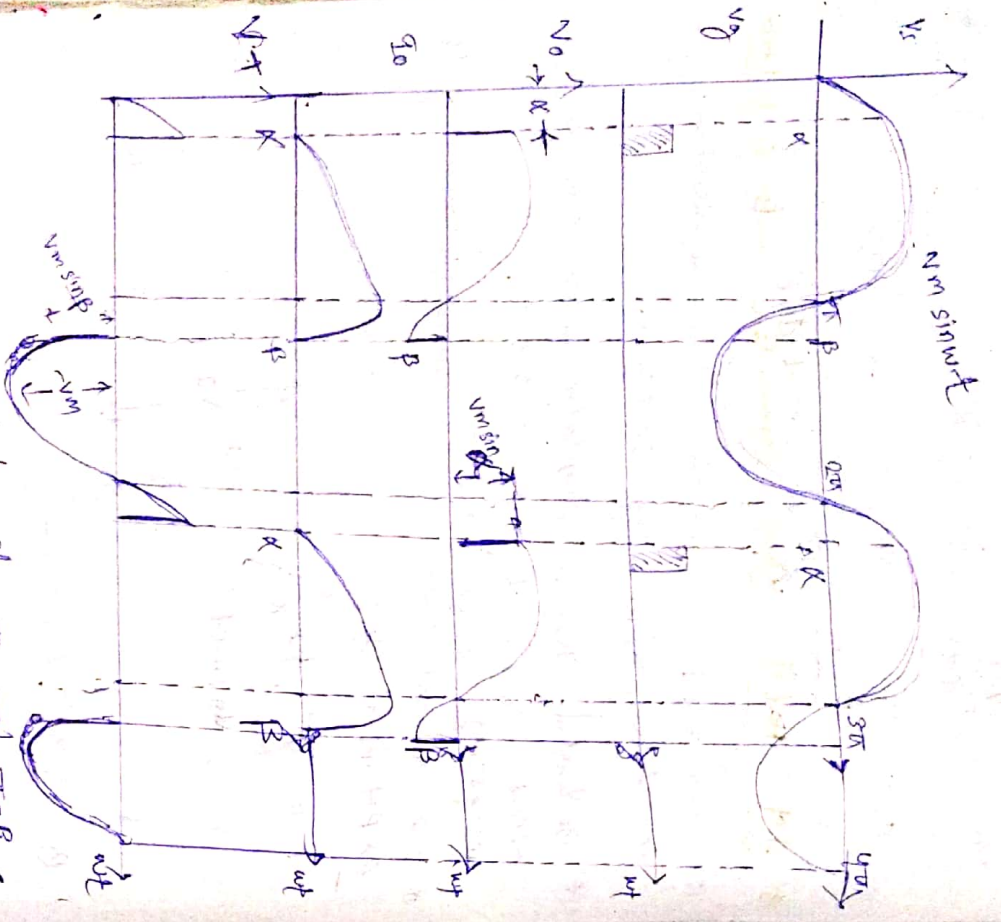At angle α when gate pulse is given to SCR it starts conducting & voltage across the load is same as the source voltage with R-L load.



-ve SCR conducted upto π and $\pi-p$.
 Hence the load inductance L forces the
 the load current to gradually
 reaches maximum and then begins to
 decrease (conductor does not allow the
 sudden change of current), so
 over through the source voltage comes
 to zero and the current reduces to
 slowly to zero.

from π to 2π which is appearing
 and flowing through load from source
 If R is π hence power flow from source
 to load.
 from $\pi-p$, i_0 is +ve but V_0 is -ve
 the power is hence -ve.
 Hence the power is called back to load to
 source this is called regaining.
 The regaining is continuous till the energy in
 the inductor given back to the source due
 the average o/p voltage get reduced due
 the average o/p voltage. \therefore longer the
 -ve signal. \therefore longer the inductance then longer the
 of α . longer the inductance then longer the
 -ve area \therefore hence the average
 o/p voltage & vice-versa.
 \therefore when SCR is triggered due to V_0, I_0
 starts flowing from $\omega t = \alpha$ & gradually
 reaches maximum.
 increases \therefore starts decreasing
 and after π if start decreasing
 upto π known as extinction angle $B - \alpha = \gamma$
 and lines the SCR conducts $B - \alpha = \gamma$
 known as conduction angle.
 $\alpha =$ firing angle
 $B =$ extinction angle

AVG value of voltage :-

$$V_0 = \frac{1}{\pi} \int_{\alpha}^{\beta} v_m \sin \omega t \, d(\omega t)$$



$$= \frac{v_m}{2\pi} \left(-\cos \omega t \right)_{\alpha}^{\beta}$$

$$V_0 = \frac{v_m}{2\pi} (\cos \alpha - \cos \beta)$$

$$I_0 = \frac{V_0}{2\pi R} (\cos \alpha - \cos \beta)$$

$$I_{RMS} = \frac{1}{\pi} \sqrt{\int_{\alpha}^{\beta} v_m^2 \sin^2 \omega t \, d(\omega t)}$$

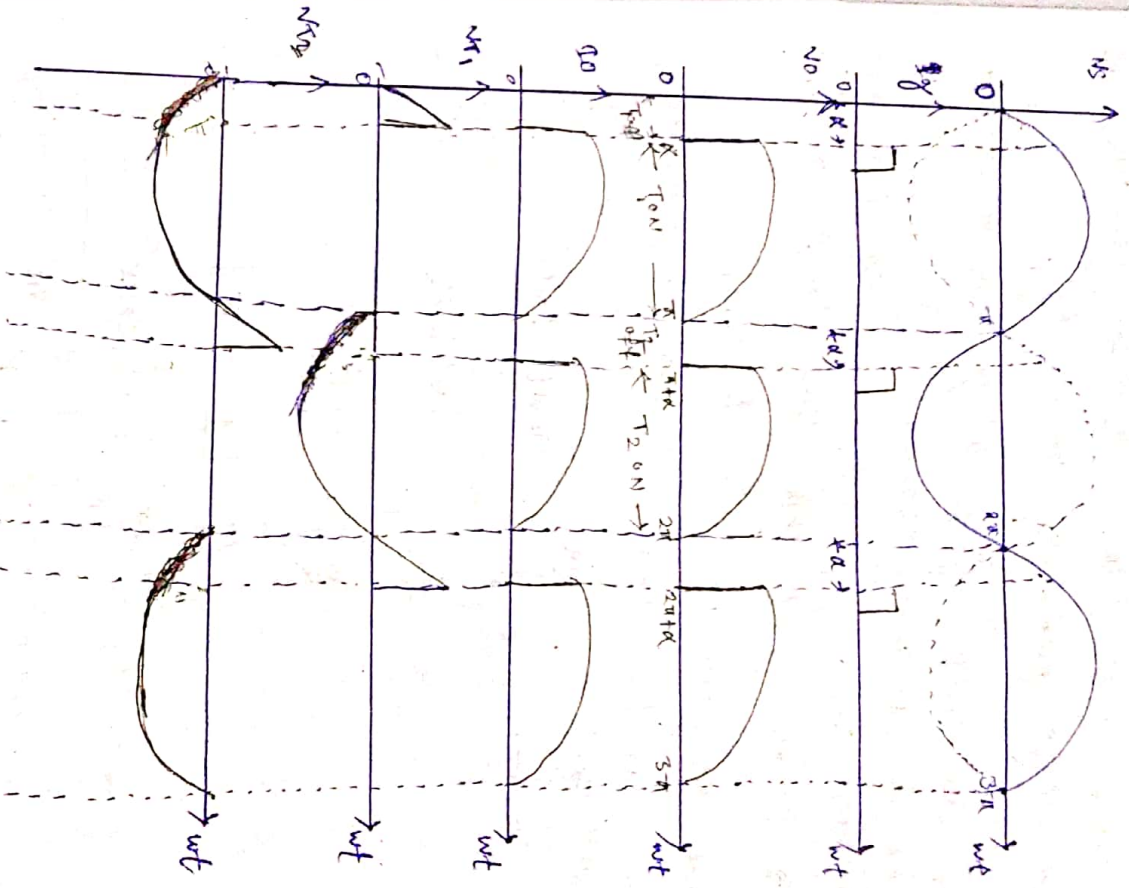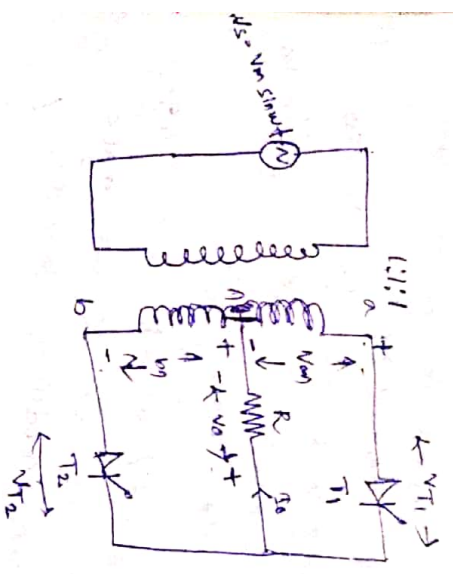Q-4 Full wave mid-converter with R-load :-



→ A centre tapped tfp and two thyristors for one used in this converter.

→ In the half cycle 'a' is the first 'b' and terminal 'a' is the first 'b'.

→ When V_{om} is the first T_1 forward biased and T_1 is on. If this time T_2 is off.

In this case the thyristor is in conduction.

→ In the next cycle 'a' is +ve w.r.t 'O' and 'b' is +ve w.r.t 'O'. F.B and

→ When V_{an} is +ve... T_2 is on. V_{bn} is +ve... T_1 is on.

T_2 is on at this time +, ix off.

→ Here the turn ratio of transformer is 1:1:1

→ For resistive load, current is in phase with V_o .

$$I_{o\text{ avg}} = \frac{1}{R} \int_{\pi}^{2\pi} V_m \sin \omega t \, d(\omega t)$$

$$= \frac{V_m}{R} \int_{\pi}^{2\pi} \sin \omega t \, d(\omega t)$$



$$= \frac{V_m}{R} [-\cos \omega t]_{\pi}^{2\pi}$$

$$= \frac{V_m}{R} [1 + \cos \pi]$$



$$I_{o\text{ avg}} = \frac{V_m}{\pi R} [1 + \cos \pi]$$

$$V_{o\text{ rms}} = \frac{1}{R} \sqrt{\int_{\pi}^{2\pi} V_m^2 \sin^2 \omega t \, d(\omega t)}$$

Bridge converter with R load

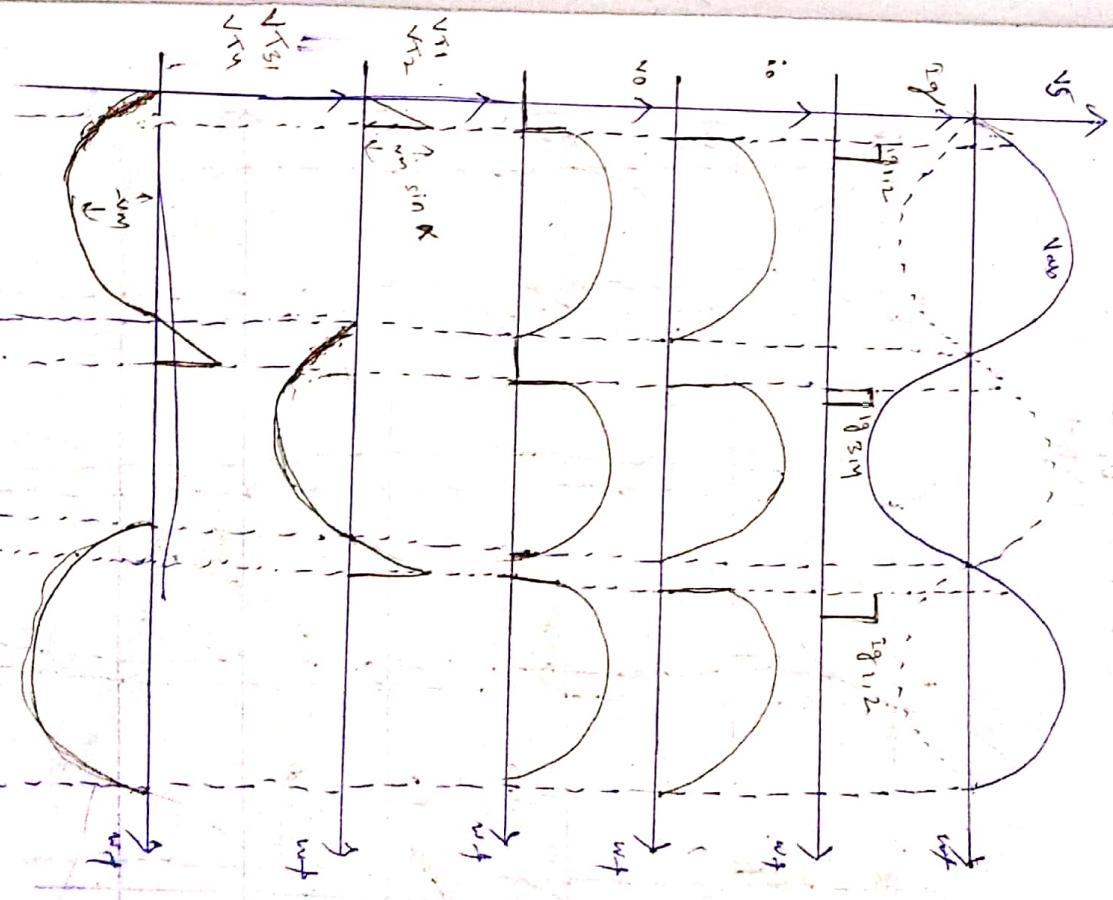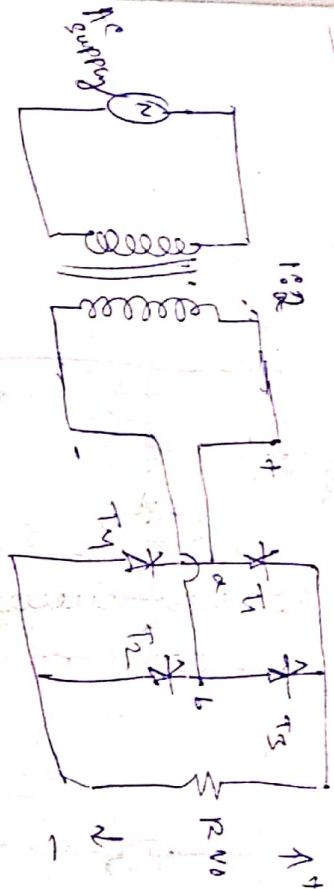

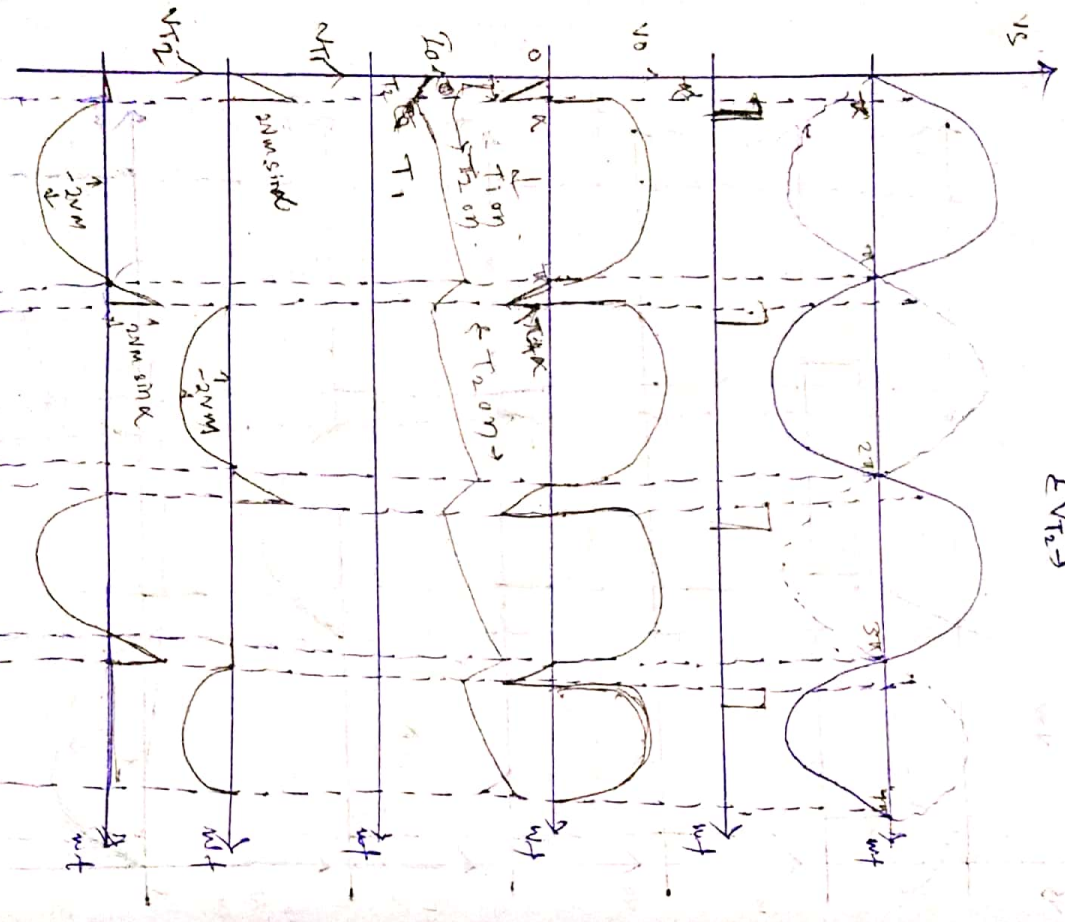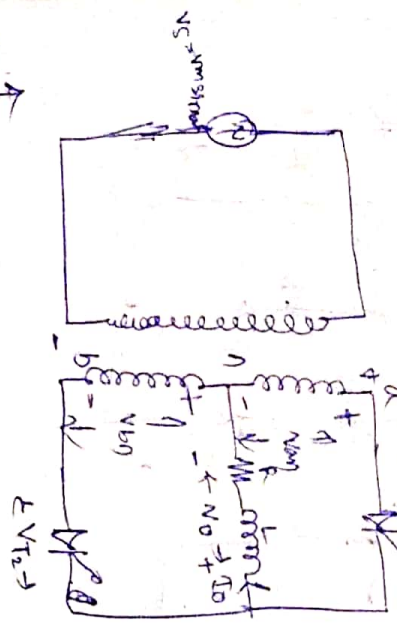1 ϕ full wave mid converter with RL load.



$$V_{avg} = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t \, d\omega t$$

$$V_{avg} = \frac{2V_m}{\pi} \cos \alpha$$


$$V_{o.r.m.s} = \sqrt{\frac{1}{\pi} \int_0^{\pi} V_m^2 \sin^2 \omega t \, d\omega t}$$

$$= \frac{V_m}{\sqrt{2}} \int_0^{\pi} \sin^2 \omega t \, d\omega t$$

$$V_{o.r.m.s} = \frac{V_m}{\sqrt{2}}$$

$$V_{o.r.m.s} = V_s$$

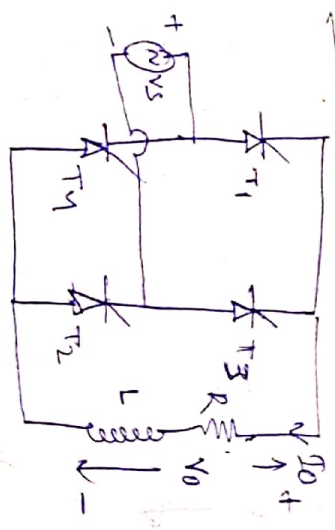1 ϕ full wave bridge converter with RL load. $V_{o.r.m.s} = V_s$





Free wheeling Diode

Answer



* A free wheeling diode placed across the inductive load will provide a path for release of energy stored in the inductor under the load voltage drops to zero.

→ The freewheeling diode prevents the load voltage from becoming negative. whenever load voltage tends to go negative, F.O.D comes to play. It improves the line power factor. It is not capacitor required but general diode.

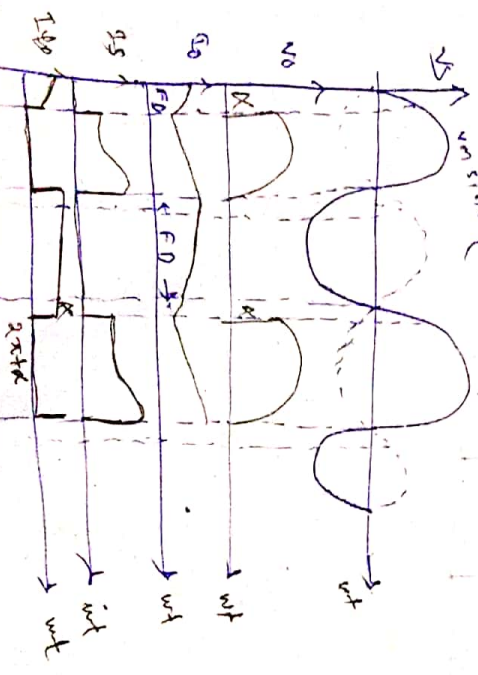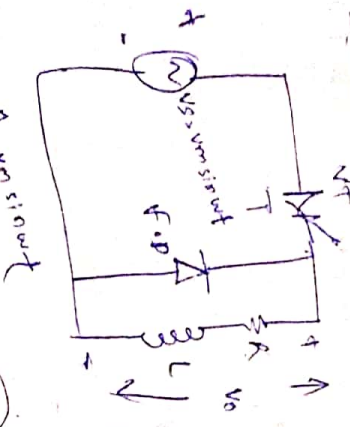Single phase half wave thyristor with RL load and freewheeling diode:



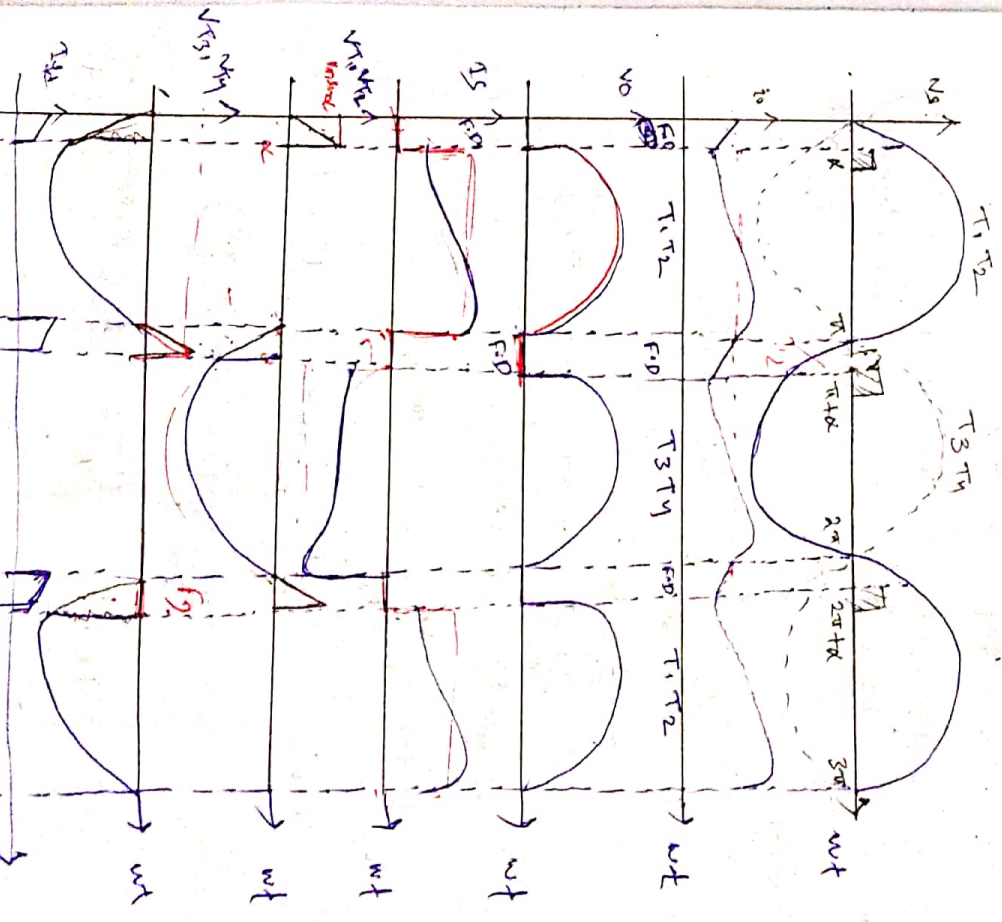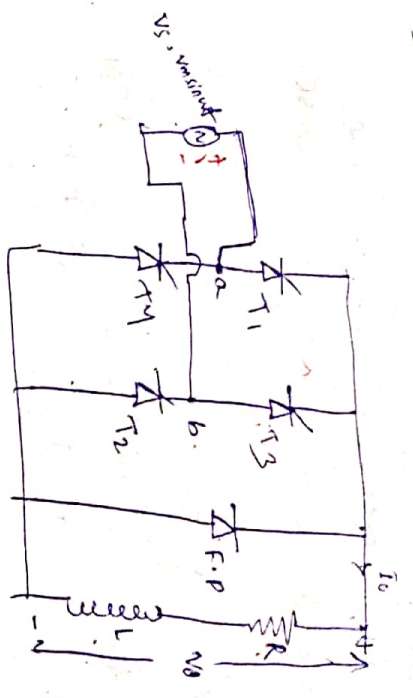① - φ full wave converter with RL load and free wheeling diode



→ The VCT consist of four thyristor T_1, T_2, T_3, T_4 and R_L load and free wheeling diode.

→ During the half cycle, T_1 & T_2 are forward biased & T_3 & T_4 are reverse biased.

→ So T_1 & T_2 are on.

→ During the -ve half cycle, T_3 & T_4 are f.b. & T_1 & T_2 are r.b.

→ So T_3 & T_4 are on.

→ By connecting a free wheeling diode, a continuous load current is maintaining and it prevents the reversal of load voltage.

$$V_{o\text{avg}} = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t \, d(\omega t)$$

$$= \frac{V_m}{\pi} \int_0^{\pi} (-\cos \omega t) \, d(\omega t)$$

$$= \frac{V_m}{\pi} [-\cos \omega t]_0^{\pi} = \frac{V_m}{\pi} (-(-\cos \pi) - (-\cos 0))$$


$$V_{o\text{avg}} = \frac{V_m}{\pi} (1 + \cos \alpha)$$

$$I_{o\text{avg}} = \frac{V_m}{\pi R} (1 + \cos \alpha)$$


$$V_{o\text{R.m.s}} = \sqrt{\frac{1}{\pi} \int_0^{\pi} V_m^2 \sin^2 \omega t \, d(\omega t)}$$

$$= \frac{V_m}{\sqrt{2\pi}} \sqrt{(\pi - \alpha) - \frac{\sin 2\alpha}{2}}$$
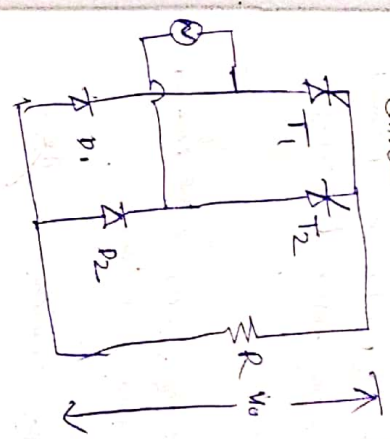
$$I_{o\text{R.m.s}} = \frac{V_{o\text{R.m.s}}}{R} = I_s \text{ (Supply R.m.s current)}$$



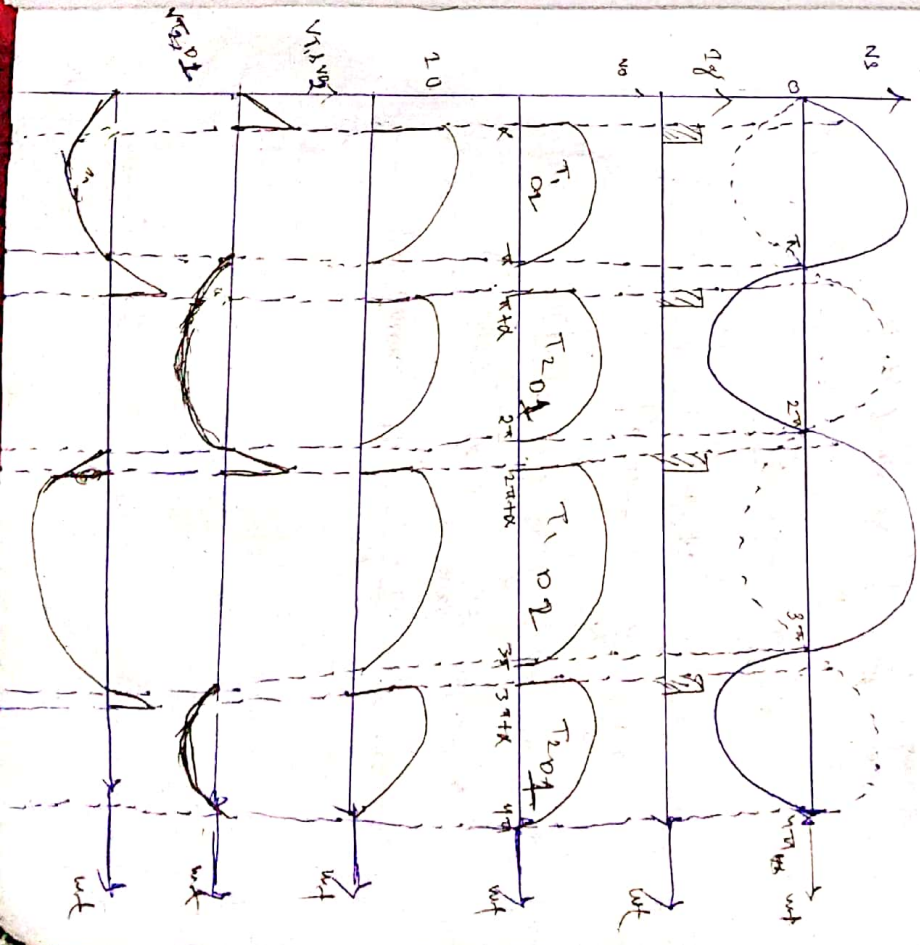1-φ half wave controlled bridge converter for R load of 1-φ full wave semi-converter with R load. (Symmetric)



It consists of two thyristors T_1, T_2 and two diodes D_1, D_2 .

- During the half cycle T_1, D_2 are forward biased and T_2, D_1 are reverse biased.
- So T_1, D_2 are on.
- During the half cycle, T_2, D_1 are forward biased and T_1, D_2 are reverse biased.

As so T_2, D_1 are on, the current to R is in phase with V_o .

$$I_o = \frac{V_m}{R} \int_0^{\pi} \sin \omega t \, d(\omega t)$$

$$= \frac{V_m}{R} [-\cos \omega t]_0^{\pi}$$

$$= \frac{V_m}{R} [1 + \cos \alpha]$$

$$I_o = \frac{V_m}{R} [1 + \cos \alpha]$$



$$I_{o,avg} = \frac{V_m}{R} \left[\frac{1}{\pi} \int_0^{\pi} \sin^2 \omega t \, d(\omega t) \right]$$

$$I_{o,avg} = \frac{V_m}{R} \left[\frac{1}{\pi} \left(\frac{\omega t}{2} - \frac{\sin 2\omega t}{4} \right) \right]_0^{\pi}$$

$$I_{o,avg} = \frac{V_m}{R} \left[\frac{\pi}{2\pi} - \frac{\sin 2\pi}{4\pi} + \frac{\sin 0}{4\pi} \right]$$

$$I_{o,avg} = \frac{V_m}{R} \left[\frac{1}{2} \right]$$

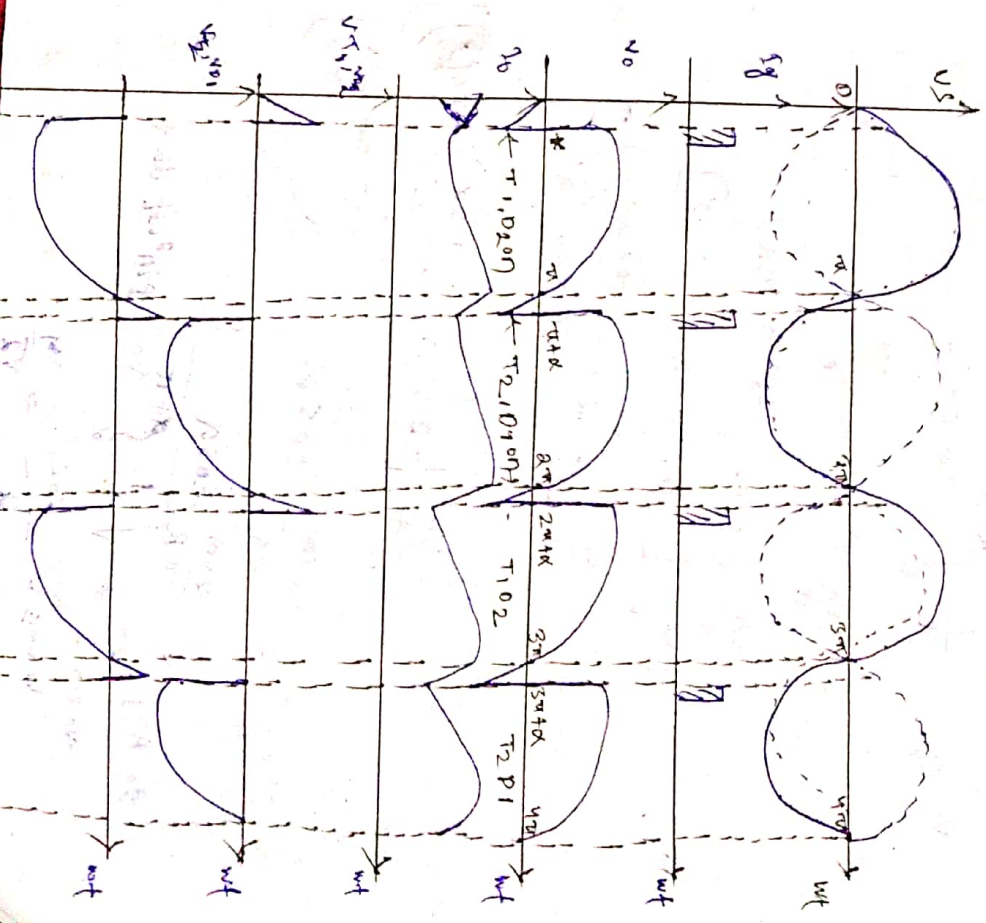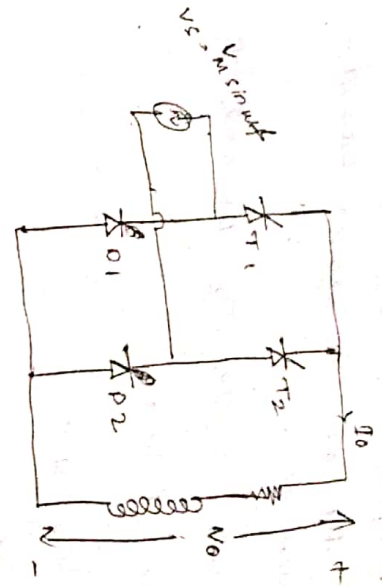1- ϕ half wave controlled bridge converter for R-L load.
 or ϕ full wave semi converter with R-L load.



→ The ckt consist of two thyristor T_1, T_2 and two diode D_1, D_2 .

→ During the half cycle T_1, D_2 are forward biased and T_2, D_1 are reversed.

→ So T_1, D_2 are on.

→ During the half cycle T_2, D_1 are F.B. and T_1, D_2 are R.B.

→ So T_2, D_1 are on.

$$V_o \text{ avg} = \frac{1}{\pi} \int_{\pi+\alpha}^{2\pi} V_m \sin \omega t \, d\omega t$$

$$= \frac{V_m}{\pi} (-\cos \omega t) \Big|_{\pi+\alpha}^{2\pi}$$

$$= \frac{V_m}{\pi} (-\cos(2\pi) + \cos(\alpha))$$

$$= \frac{V_m}{\pi} [\cos(\alpha) - \cos(2\pi)]$$

$$= \frac{V_m}{\pi} \left[-2 \sin\left(\frac{\pi+\alpha}{2}\right) \sin\left(\frac{\pi+\alpha}{2}\right) \right]$$

$$\left(\because \sin\left(\frac{\pi}{2} + \alpha\right) = \cos \alpha \right)$$



$$V_i \text{ avg} = \frac{2V_m}{\pi} \cos \alpha$$

g.o. Avg = $\frac{2V_m}{\pi} \cos \alpha$

No. r.m.s = $\frac{V_m}{\sqrt{2}}$

$V_{i \text{ rms}} = \frac{V_m}{\sqrt{2}} \cos \alpha$

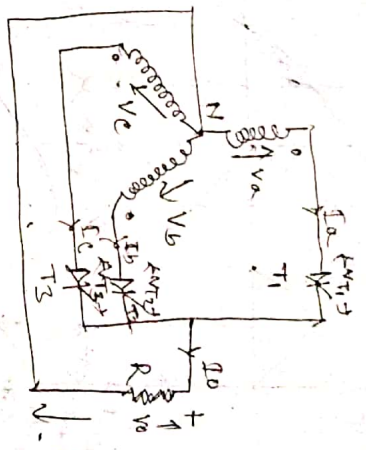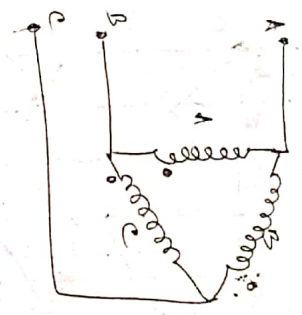3-φ Half wave controlled converter with R Load.



Three phase are displaced by 120° .

Here $V_a = V_m \sin \omega t$

$V_b = V_m \sin(\omega t - 2\pi/3)$

$V_c = V_m \sin(\omega t - 4\pi/3)$


Here during range voltage phase conduct thyristor compare to other phase.

* If firing angle is zero degree, SCR T_1 would begin conducting from $\omega t = 30^\circ$ to 150° , T_2 from $\omega t = 150^\circ$ to 270° and T_3 from measured from $\omega t = 30^\circ$ and 390° and so on.

* In other words, firing angle from this controlled converter would be measured from $\omega t = 30^\circ$ for T_1 , from $\omega t = 150^\circ$ for T_2 and from $\omega t = 270^\circ$ for T_3 .

* For zero degree firing angle delay, thyristor behaves like as diode.

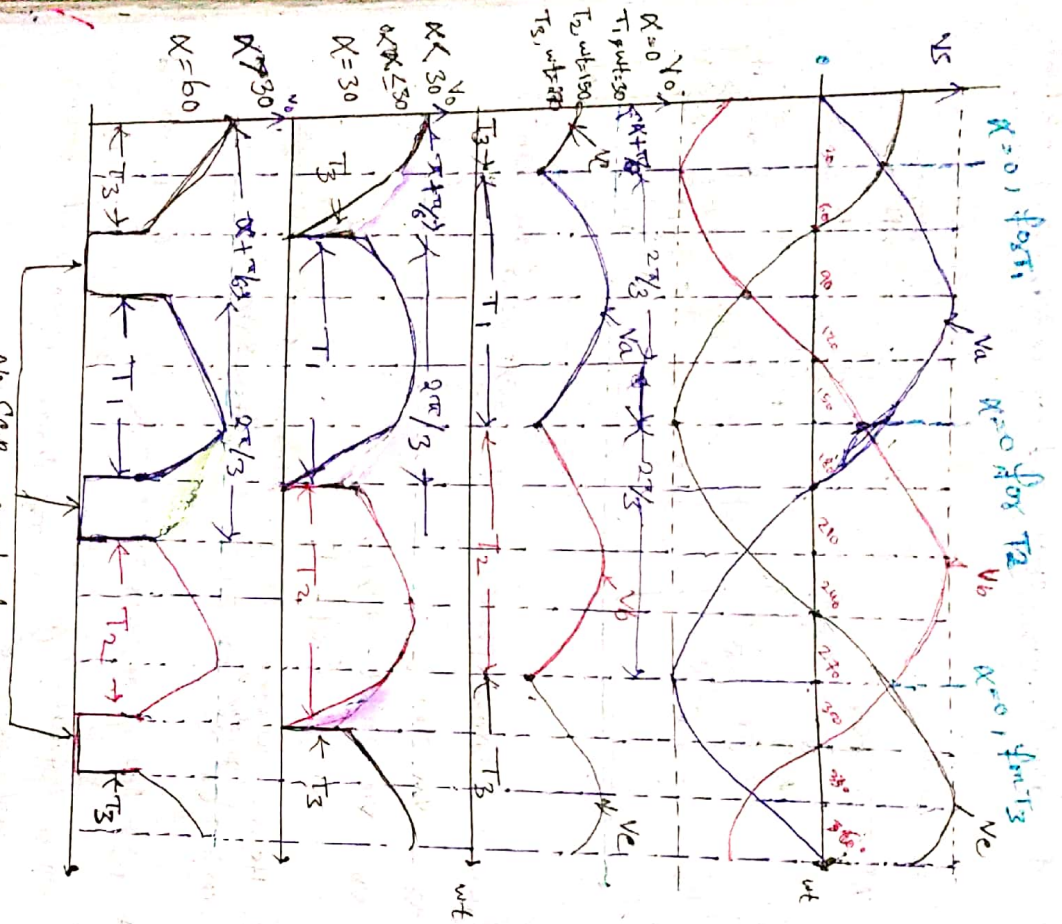* The operation of this converter is now described for $\alpha < 30^\circ$ and for $\alpha > 30^\circ$.



Firing angle $< 30^\circ$
 → The output voltage wave form V_o for firing angle less than 30°
 → where T_1 conduct from $\omega t = 30^\circ + \alpha$ to $\omega t = 150^\circ + \alpha$, T_2 from $150^\circ + \alpha$ to

$270^\circ + \alpha$ and so on.

each SCR conducts for 120° .
 → The wave form of I_o is same as V_o wave form.

$$0 < \alpha < 30$$

$$V_o \text{ avg} = \frac{1}{T} \int_0^T v_o(t) dt$$

$$= \frac{1}{2\pi/3} \int_{\alpha+\pi/6}^{\alpha+\pi/6} V_{m\phi} \sin \omega t \, d\omega t$$

$$= \frac{3}{2\pi} \times V_{m\phi} \int_{\alpha+\pi/6}^{\alpha+\pi/6} \sin \omega t \, d\omega t$$

$$= \frac{3 \times V_{m\phi}}{2\pi} \left[-\cos \omega t \right]_{\alpha+\pi/6}^{\alpha+\pi/6}$$

$$= \frac{3 V_{m\phi}}{2\pi} \left[\cos(\alpha + 5\pi/6) - \cos(\alpha + \pi/6) \right]$$

$$= \frac{3 V_{m\phi}}{2\pi} \left[\cos \alpha \cdot \cos 5\pi/6 - \sin \alpha \cdot \sin 5\pi/6 - \left(\cos \alpha \cdot \cos \pi/6 + \sin \alpha \cdot \sin \pi/6 \right) \right]$$

$$= \frac{3 V_{m\phi}}{2\pi} \left[\cos \alpha (\cos 5\pi/6 - \cos \pi/6) - \sqrt{3} \sin \alpha (\sin 5\pi/6 + \sin \pi/6) \right]$$

$$= \frac{3 V_{m\phi}}{2\pi} \left[-\sqrt{3} \cos \alpha - 2 \sin \alpha \right]$$

$$V_{o \text{ avg}} = \frac{3 V_{m\phi} \cos \alpha}{2\pi}$$

$V_{m\text{ph}}$ = maximum value of phase voltage
 V_m = maximum value of line voltage.

α = firing angle delay

$$V_{o\text{rms}} = \sqrt{\frac{1}{T} \int_0^T V_o^2(t) dt}$$

$$= \frac{3}{2\pi} \int_{\alpha + \pi/6}^{\pi} V_{m\text{ph}}^2 \sin^2 \omega t d(\omega t)$$

(Numerator)² $\frac{3 V_{m\text{ph}}^2}{2\pi} \int_{\alpha + \pi/6}^{\pi} \sin^2 \omega t d(\omega t)$

$$= \frac{3 V_{m\text{ph}}^2}{2\pi} \int_{\alpha + \pi/6}^{\pi} \frac{1 - \cos 2\omega t}{2} d\omega t$$

$$= \frac{3 V_{m\text{ph}}^2}{2\pi} \left[\frac{1}{2} (\omega t) \Big|_{\alpha + \pi/6}^{\pi} - \frac{1}{2} \left(\frac{\sin 2\omega t}{2} \right) \Big|_{\alpha + \pi/6}^{\pi} \right]$$

$$= \frac{3 V_{m\text{ph}}^2}{4\pi} \left[\left(\pi + \frac{5\pi}{6} - \alpha - \frac{\pi}{6} \right) - \left(\frac{\sin 2\omega t}{2} \right) \Big|_{\alpha + \pi/6}^{\pi} \right]$$

$$= \frac{3 V_{m\text{ph}}^2}{4\pi} \left(4\pi/6 \right) - \frac{1}{2} \left[\sin \left(2\alpha + \frac{5\pi}{3} \right) - \sin \left(2\alpha + \pi/3 \right) \right]$$

$$= \frac{3 V_{m\text{ph}}^2}{4\pi} \left[\left(\frac{2\pi}{3} \right) - \frac{1}{2} \left(\sin 2\alpha + \cos 5\pi/3 + \cos 2\alpha - \sin 2\alpha \right) \right]$$

$$= \frac{3 V_{m\text{ph}}^2}{4\pi} \left[\frac{2\pi}{3} - \frac{1}{2} \left(-\cos 2\alpha \sqrt{3} \right) \right]$$

$$= \frac{3 V_{m\text{ph}}^2}{4\pi} \left(\frac{2\pi}{3} + \frac{\sqrt{3}}{2} \cos 2\alpha \right)$$

$$V_{o\text{rms}} = \sqrt{\frac{3 V_{m\text{ph}}^2}{4\pi} \left(\frac{2\pi}{3} + \frac{\sqrt{3}}{2} \cos 2\alpha \right)}$$

$$= V_{m\text{ph}} \sqrt{\left[\frac{\sqrt{3}}{2} + \frac{3\sqrt{3}}{8\pi} \cos 2\alpha \right]}$$

$$= V_{m\text{ph}} \sqrt{\left[\frac{1}{2} + \frac{3\sqrt{3}}{8\pi} \cos 2\alpha \right]}$$

$$= V_{m\text{ph}} \sqrt{3 \left(\frac{1}{2} \times 3 + \frac{\sqrt{3}}{8\pi} \cos 2\alpha \right)}$$

$$= \sqrt{3} V_{m\text{ph}} \sqrt{\frac{1}{6} + \frac{\sqrt{3}}{8\pi} \cos 2\alpha}$$

$$= V_m \sqrt{\frac{1}{6} + \frac{\sqrt{3}}{8\pi} \cos 2\alpha}$$

$$V_{o\text{rms}} = \frac{V_{o\text{rms}}}{R} = \frac{V_m}{R} \sqrt{\frac{1}{6} + \frac{\sqrt{3}}{8\pi} \cos 2\alpha}$$

Firing angle $\gamma > 30^\circ$ is more than 30° , when the firing angle $\alpha + 30^\circ$ or $30^\circ + \alpha$ to T_1 , would conduct ϕ from $\alpha + 30^\circ$ or $30^\circ + \alpha$ to 180° , T_2 from $150^\circ + \alpha$ to 300° and so on.

For R , load, when phase voltage N_a reaches at zero at $\omega t = 180^\circ$, current $i_o = 0$, T_1 is therefore turned off.

Thus, To would conduct from 30° to 180° . Same is true for other sets. This shows that each set, for firing angle α & 30° conducts for $(150^\circ - \alpha)$ only.

→ This implies that for R load, maximum possible value of firing angle is 150° .

$$V_{avg} = \frac{3}{2\pi} \int_{\alpha + \pi/6}^{\pi} V_m \sin \omega t \, d(\omega t)$$

$$= \frac{3}{2\pi} V_m \int_{\alpha + \pi/6}^{\pi} \sin \omega t \, d(\omega t)$$

$$= \frac{3}{2\pi} V_m \left(-\cos \omega t \right)_{\alpha + \pi/6}^{\pi}$$

$$= \frac{3}{2\pi} V_m \left(\cos \alpha + \pi/6 \right)$$

$$= \frac{3}{2\pi} V_m \left(\cos \alpha + \cos \pi/6 + \sin \pi/6 \right)$$

$$= \frac{3}{2\pi} V_m \left[-1 - \cos(\alpha + 30^\circ) \right]$$

$$V_{avg} = \frac{3}{2\pi} V_m \left[1 + \cos(\alpha + 30^\circ) \right]$$

$$V_{avg} = \frac{3}{2\pi} \int_{\alpha + \pi/6}^{\pi} V_m \sin^2 \omega t \, d(\omega t)$$

$$= \frac{3}{2\pi} \frac{1}{2} \int_{\alpha + \pi/6}^{\pi} (1 - \cos 2\omega t) \, d(\omega t)$$

$$= \frac{\sqrt{3}}{2\sqrt{\pi}} V_m \left[\frac{1}{2} (\pi - \alpha - \pi/6) - \frac{1}{2} \left[\sin 2\pi - \sin(2\alpha + \pi/3) \right] \right]$$

$$= \frac{\sqrt{3}}{2\sqrt{\pi}} V_m \left[\frac{5\pi}{6} - \alpha - \frac{1}{2} \left[\sin 2\alpha + \pi/3 \right] \right]$$

$$= \frac{\sqrt{3}}{2\sqrt{\pi}} V_m \left[\left(\frac{5\pi}{6} - \alpha \right) + \frac{1}{2} \sin(2\alpha + \pi/3) \right]$$

$$= \frac{V_L}{2\sqrt{\pi}} \left[\left(\frac{5\pi}{6} - \alpha \right) + \frac{1}{2} \sin(2\alpha + \pi/3) \right]$$

3rd full wave controlled converter with R-load:


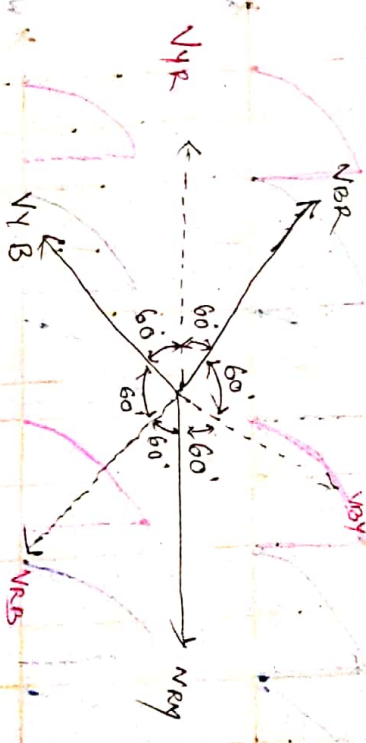
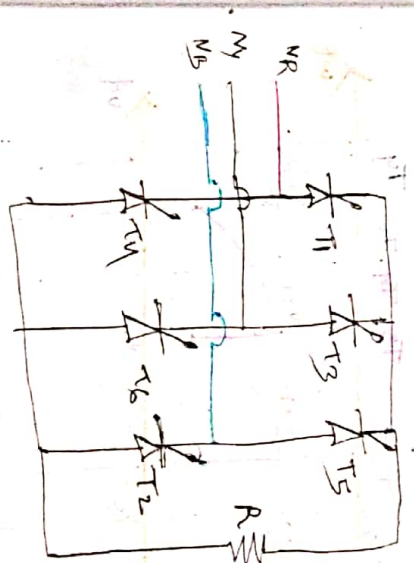


Fig 1.12

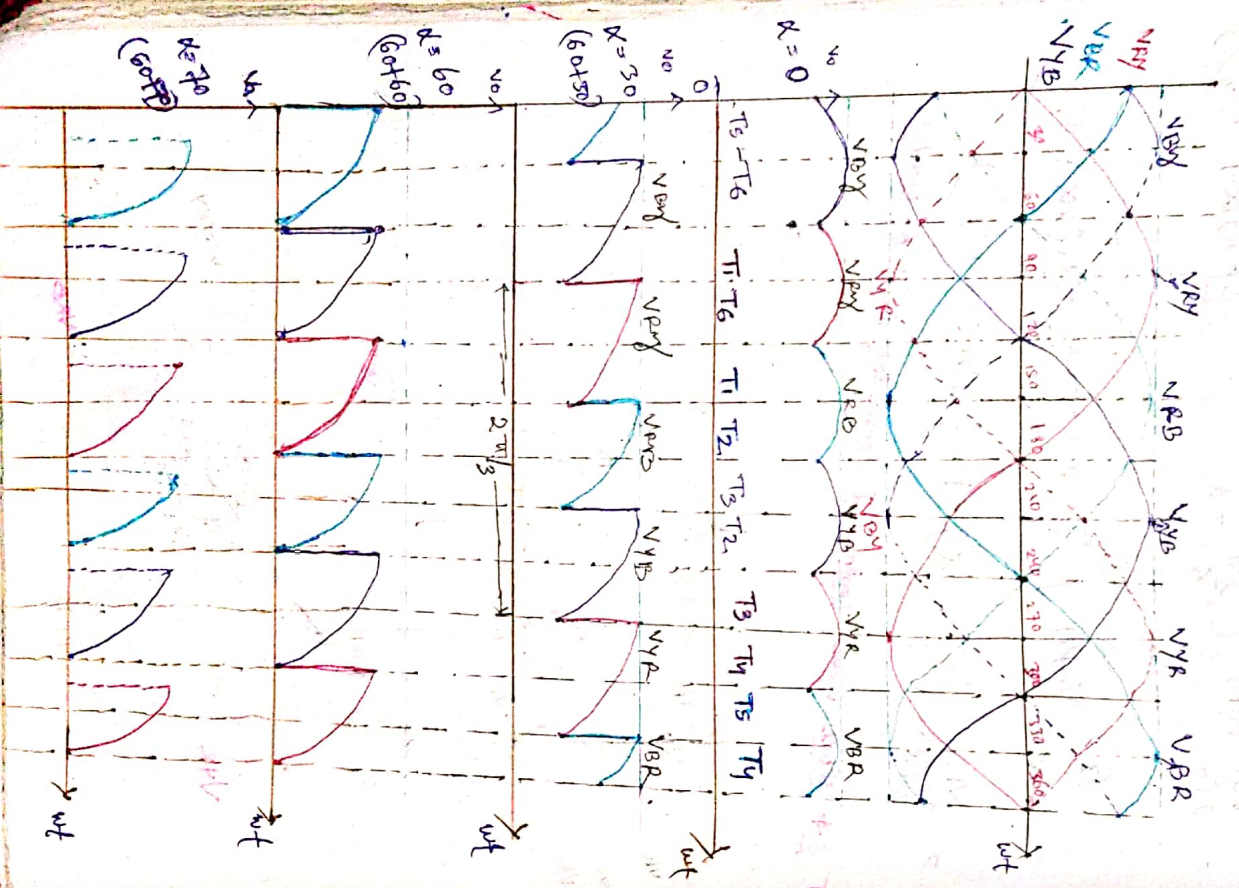At m ix the number of pulse .
 $\frac{2\pi}{6} = \pi/3$ (pulse width)



3-φ supply is given to the terminal A, YB.
 → The ext consists of six thyristors T₁, T₂, T₃, T₄, T₅ & T₆ and a R-load.

→ when $\alpha = 30^\circ$
 T₁, T₂ conduct from (60+30) = 90 to 150

T₃, T₄ conduct from 150 to 210

T₅, T₆ conduct from 210 to 270

T₁, T₄ conduct from 270 to 330

T₃, T₆ conduct from 330 to 390 (Here 30°)

T₅, T₂ conduct from 390 to 450 (Here 90°)

→ At $\alpha = 0$ we will get a continuous conduction.

→ For R load we will get a continuous conduction.

→ Each thyristor is fired after 60°.

→ Each thyristor conducts for 120° but in 60° interval only.

→ Here 60° interval only.

→ As T₁ & T₂ are connected to R and B so they appear at output.

$$0 < \alpha \leq 60^\circ$$

$$V_{avg} = \frac{1}{T} \int_0^T v_o(t) dt$$

$$= \frac{1}{\pi/3} \int_{\pi/3}^{\pi} V_m \sin \omega t dt$$

$$= \frac{V_m}{\pi/3} \left[-\cos \omega t \right]_{\pi/3}^{\pi + 2\pi/3}$$

$$= \frac{3V_m}{\pi} \left(\cos(\pi + 2\pi/3) - \cos(\pi/3) \right)$$

$$= \frac{3V_m}{\pi} \left[\cos \pi \cdot \cos \pi/3 - \sin \pi \cdot \sin \pi/3 - \cos \pi \cdot \cos 2\pi/3 + \sin \pi \cdot \sin 2\pi/3 \right]$$

$$= \frac{3V_m}{\pi} \left[\cos \alpha \right]$$

$$V_{avg} = \frac{3V_m}{\pi} \cos \alpha$$

$$I_{avg} = \frac{3V_m}{\pi R} \cos \alpha$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v_o^2 dt}$$

$$V_{rms}^2 = \frac{3}{\pi} \int_{\pi/3}^{\pi} V_m^2 \sin^2 \omega t dt$$

$$= \frac{3V_m^2}{\pi} \int_{\pi/3}^{\pi} \frac{1 - \cos 2\omega t}{2} dt$$

$$= \frac{3V_m^2}{\pi} \left[\frac{t}{2} - \frac{\sin 2\omega t}{4\omega} \right]_{\pi/3}^{\pi}$$

$$= \frac{3V_m R}{\pi} \frac{1}{2} \left[\cos \omega t \right]_{\pi/3}^{\pi + 2\pi/3} - \left(\frac{\sin 2\omega t}{2} \right)_{\pi/3}^{\pi + 2\pi/3}$$

$$= \frac{3V_m^2}{2\pi} \left[(\pi + 2\pi/3 - \pi - \pi/3) - \frac{1}{2} \left(\sin(2\pi + 4\pi/3) - \sin(2\pi/3) \right) \right]$$

$$= \frac{3V_m^2}{2\pi} \left[(\pi/3) - \frac{1}{2} (\sin 2\pi + \sin 2\pi/3) \right]$$

$$= \frac{3V_m^2}{2\pi} \left(\pi/3 \right) - \frac{1}{2} \left(\sin 2\pi + \sin 2\pi/3 \right)$$

$$= \frac{3V_m^2}{2\pi} \left(\pi/3 \right) - \frac{1}{2} \left(\sin \pi \cdot \cos \pi/3 + \cos \pi \cdot \sin \pi/3 + \cos 2\pi \cdot \cos \pi/3 - \sin 2\pi \cdot \sin \pi/3 \right)$$

$$= \frac{3V_m^2}{2\pi} \left(\pi/3 \right) - \frac{1}{2} \left(\cos \pi \cdot \cos \pi/3 + \cos 2\pi \cdot \cos \pi/3 - \sin \pi \cdot \sin \pi/3 - \sin 2\pi \cdot \sin \pi/3 \right)$$

$$= \frac{3V_m^2}{2\pi} \left(\pi/3 \right) - \frac{1}{2} \left(\cos \pi \left(\sin \pi/3 - \sin 2\pi/3 \right) \right)$$

$$= \frac{3V_m^2}{2\pi} \left(\pi/3 \right) - \frac{1}{2} \cos \pi \left(-\sqrt{3} \right)$$

$$= \frac{3V_m^2}{2\pi} \left[\pi/3 + \frac{\sqrt{3}}{2} \cos \alpha \right]$$

$$V_{rms} = \sqrt{\frac{3V_m^2}{2\pi} \left(\pi/3 + \frac{\sqrt{3}}{2} \cos \alpha \right)}$$

$$= V_m \sqrt{\frac{3}{2\pi} \left[\pi/3 + \frac{\sqrt{3}}{2} \cos \alpha \right]}$$

Working of single phase AC regulator:-

It is a device which converts fixed single phase alternating voltage with direct frequency to a variable alternating voltage without a change in frequency. The 1/P and 0/P of the device is single phase.


There are two types of AC voltage controller:

1. single phase half wave controller.
2. single phase full wave controller.

Working principle of single phase AC voltage controller:-

Half wave AC voltage controller:-

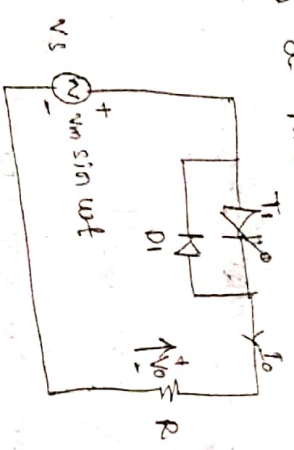A single phase half wave AC voltage controller consists of a thyristor connected in series with a load.



Here the load is taken resistive load. The input source is $v_s = v_m \sin \omega t$.


For the half cycle the thyristor is forward biased. Hence the thyristor starts to conduct when we provide gate pulse.

By adjusting the firing angle α we can provide the thyristor to the thyristor. Such time the resistive load stands to conducting through the thyristor.

It makes load voltage $v_o = v_m \sin \omega t$.

At a time $\omega t = \pi$, the load current is reversed. Such voltage becomes zero and the thyristor T_1 is naturally commutated.

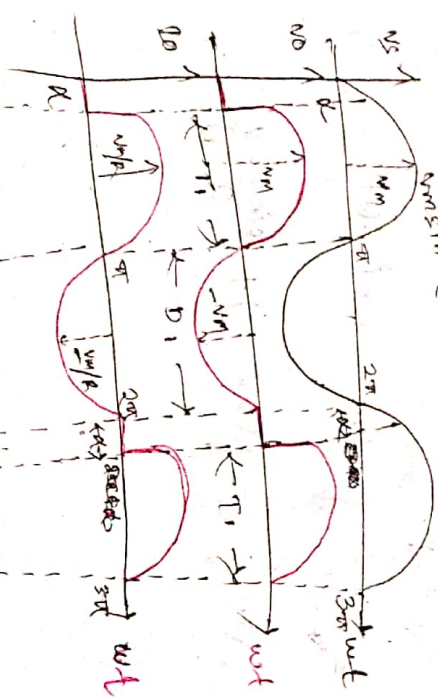After $\omega t = \pi$, diode D_1 becomes forward biased and voltage & current are supplied across load voltage $v_o = v_m \sin \omega t$ resistively for the negative half cycle.



$$V_{avg} = \frac{1}{T} \int_0^T v_o(t) dt$$

$$V_{avg} = \frac{1}{2\pi} \int_0^{2\pi} v_m \sin \omega t d\omega t$$

$$= \frac{1}{2\pi} \int_0^{\pi} v_m \sin \omega t d\omega t + \int_{\pi}^{2\pi} v_m \sin \omega t d\omega t$$

$$= \frac{1}{2\pi} [v_m (-\cos \omega t)]_0^{\pi} - v_m [\cos \omega t]_{\pi}^{2\pi}$$

$$= \frac{v_m}{2\pi} ((\cos \pi - \cos 0) - v_m (\cos 2\pi - \cos \pi))$$

$$= \frac{v_m}{2\pi} [1 + \cos \alpha] + (\frac{-1-1}{2\pi})$$

$$= \frac{v_m}{2\pi} (1 + \cos \alpha - 2)$$

$$V_{avg} = \frac{v_m}{2\pi} (\cos \alpha - 1)$$


$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v_o^2 dt}$$

$$= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (v_m \sin \omega t)^2 d\omega t}$$

$$= \frac{v_m}{2} \sqrt{\frac{1}{\pi} \int_0^{\pi} (\sin^2 \omega t) d\omega t + \frac{\sin 2\alpha}{2}}$$

Full wave AC voltage converter:

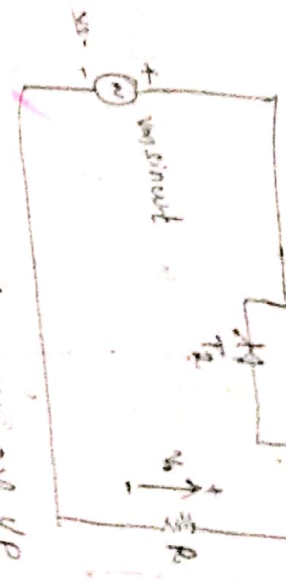2 thyristors of low inductance are connected antiparallelly, anti-parallel as 1st bidirectional converter. If, anti-parallel as 1st bidirectional converter.




For the half cycle of VP source, T1 is forward biased and T2 is reverse biased. For the half cycle of VP source, T2 is forward biased and T1 is reverse biased.

Conducting process of thyristor and load current. Load voltage $v_o = v_m \sin \omega t$. Load current $i_o = \frac{v_m \sin \omega t}{R}$.

At $\omega t = \pi$, the load voltage becomes zero. Since the thyristor is reverse biased, it gets naturally commutated. At $\omega t = (\pi + \alpha)$, forward biased thyristor is gated, hence, it conducts and connected load to the source.

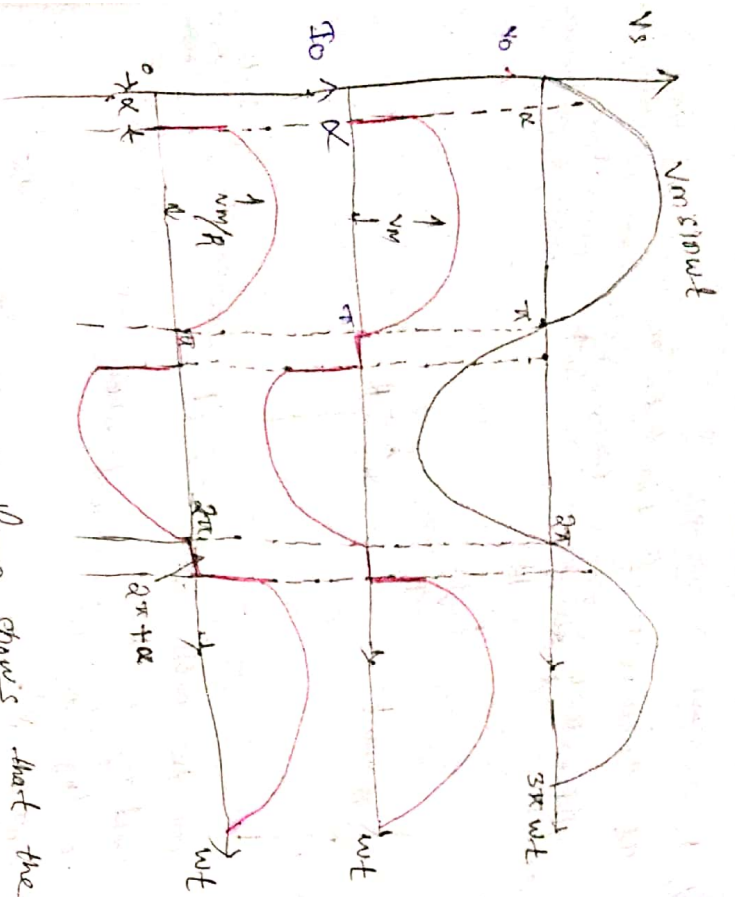Thus the rms voltage may be controlled by control of firing angle.



* The above wave form shows that the positive and negative half cycle of the load voltage & current are identical. So, $I_{avg} = 0$ / average voltage and current are zero.

$$V_{o, rms} = \sqrt{\frac{1}{T} \int_0^T v_o^2 dt}$$

$$= \sqrt{\frac{1}{\pi} \int_0^{\pi} (V_m \sin \omega t)^2 d\omega t}$$

$$= V_m \sqrt{\frac{1}{2\pi} \int_0^{\pi} (\pi - \alpha) + \frac{\sin 2\alpha}{2} d\alpha}$$

$$I_{o, rms} = \frac{V_{o, rms}}{R}$$

$$V_{avg} = 0$$

→ As a result, DC component is not introduced in the supply and load ckt. It is the big advantage of single phase full wave AC voltage controller.


→ It also overcomes the problem of dc component which is present in supply and load ckt of half wave voltage controller.

CHOPPERS :-

→ Chopper is a device which converts the constant DC to variable DC. It is equivalent to AC transformer. The two types:

- (a) AC link chopper
- (b) DC chopper

(a) AC link chopper:

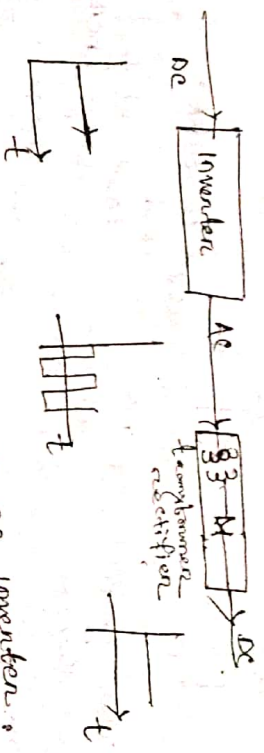

→ DC is converted into AC by an inverter.

→ AC is step up or step down by the transformer.

→ Then it is again converted into DC by rectifier.

→ As the process is two step of component are remained, the system becomes costly, bulky, less efficiency.


DC chopper :-



→ As it is a step conversion so more efficiency is required.
 → it is used in machine hoist, traction and.

Chopper are converted into two types:

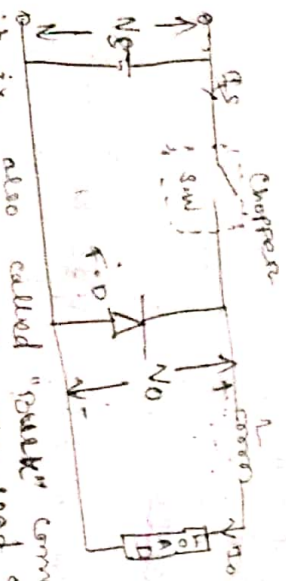- ① step up chopper (Boost)
 - ② step down chopper (Buck)
 - ③ Buck-Boost converter
- ① step down choppers



→ it is also called "Buck" converter.
 → when chopper is ON, the load current I_o flows through the inductor & load. At that time, the inductor store the charge/energy.


→ And output voltage V_o is also developed.
 $V_o < V_s$

→ when the chopper is OFF, at that time the inductor behaves as source. So the inductor release the energy through free wheeling diode.

→ So the current flows through the free wheeling diode.

→ The diode has short circuited and output is zero. ($V_o = 0$)

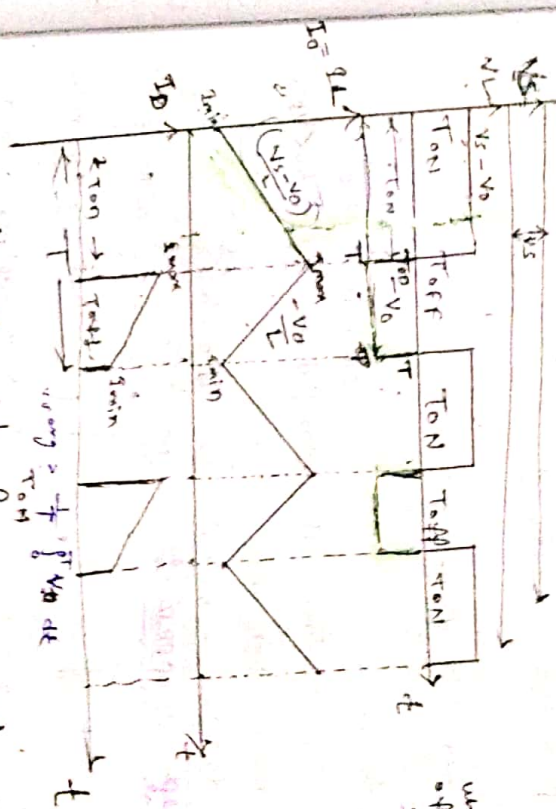when switch is ON, $V_s - V_o = L \frac{di}{dt} \Rightarrow \frac{V_s - V_o}{L} dt = di$



(∵ $V_o < V_s$)
 when in

$$V_{avg} = \frac{1}{T} \int_0^{T_{on}} V_s dt$$

$$= \frac{V_s}{T} \int_0^{T_{on}} dt$$

$$= \frac{V_s}{T} (T_{on})$$

$$V_{avg} = \frac{V_s \cdot T_{on}}{T}$$

$$V_{avg} = \left(\frac{T_{on}}{T} \right) \times V_s$$

D = duty cycle

No avg = $0 N_s$

Norm. s = $\sqrt{\frac{1}{T} \int_0^T v_s^2 dt}$

$0 = \frac{T_{on}}{T}$

$= \frac{T_{on}}{T_{on} + T_{off}}$

D value 0 to 1

$v_o \text{ avg} = D V_s$

of the D value if point 1 then the $v_o < V_s$.

$V_s \times T_s = V_o T_o$

$T_o = \left(\frac{V_o}{V_s}\right) T_s$

note

$V_s = L \frac{di}{dt}$

$\frac{V_s}{L} = \frac{di}{dt}$

$\int \frac{V_s}{L} dt = di$

$\int_0^T \frac{V_s}{L} dt = \int_0^T \frac{V_o}{L} dt$

$\int_0^T V_s dt = \int_0^T V_o dt$

$T_{on} - T_{off} = 0$


$\int_0^T V_s dt = 0$

$\int_0^T V_o dt = 0$

old see balance expression

Average voltage across inductor will be zero for 1 time period.

2) step up chopper:

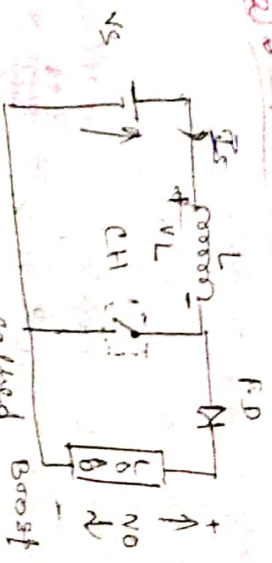

It is also called boost converter. An average of P voltage no greater than i/p voltage. V_s so it is called step up chopper.

Chopper is basically high speed turn on/off switch.

working principle: chopper CH is on, the closed switch.

when we complete through inductor current path. chopper. $V_i = 0$ during T_{on} period.

inductor stores energy during T_{on} period.

when the CH is off, the inductor does not allow to sudden change in current. So the inductor change current forced flow through

diode discharge for a time "off". The diode and the inductor current is decreasing in reverse.

when CH is on for on time

$N_s - V_L = 0$

$N_s = V_L$

$N_s > L \frac{di}{dt}$

$\frac{N_s}{L} = \frac{di}{dt}$

$\frac{N_s}{L} = \frac{di}{dt}$

$di = \frac{N_s}{L} dt$

when CH... off time 0
 such time diode will conduct.

$$\frac{V_s - V_L - V_D \Rightarrow V_L > V_s - V_D}{V_L > V_s - V_D}$$

$$-V_s - V_L + V_D = 0$$

$V_D > V_s$
 $V_L > V_s - V_D$
 in off time
 it is always -ve
 diode
 in off time
 it is always -ve
 diode

$$N_0 - V_s = L \frac{di}{dt}$$

$$\frac{N_0 - V_s}{L} = \frac{di}{dt}$$

$$\frac{N_0 - V_s}{L} \Delta t = \Delta i$$

$$\int_{t_0}^T V_L dt = 0$$

→ voltage balance expression
 always voltage of the inductor will zero.

$$\int_{T_{on}}^{T_{off}} V_L dt + \int_{T_{off}}^T V_L dt = 0$$

$$\int_{T_{on}}^{T_{off}} V_s dt + \int_{T_{off}}^T (V_s - V_0) dt = 0$$

$$V_s(T_{off} - T_{on}) + (V_s - V_0)(T - T_{on}) = 0$$

$$V_s T_{on} + V_s T - V_s T_{on} - V_0 T + V_0 T_{on} = 0$$

$$V_s T = V_0 (T - T_{on})$$

$$V_s T = V_0 (T - T_{on})$$

$$V_s T = V_0 (T - T_{on})$$

$$V_s T = V_0 T (1-D)$$

$$V_0 = \frac{V_s T}{(1-D)T}$$

$$V_0 = \frac{V_s}{1-D}$$

$$V_0 > V_s$$

Buck Boost $(\frac{D}{1-D}) V_s = V_0$
 Connection choppen

$$T_{on} + T_{off} = T$$

$$T_{off} = T - T_{on}$$


$$D = \frac{T_{on}}{T}$$

$$T_{on} = TD$$

$$T_{off} = T - TD$$

$$T_{off} = T(1-D)$$

$$0 < 1-D < 1$$

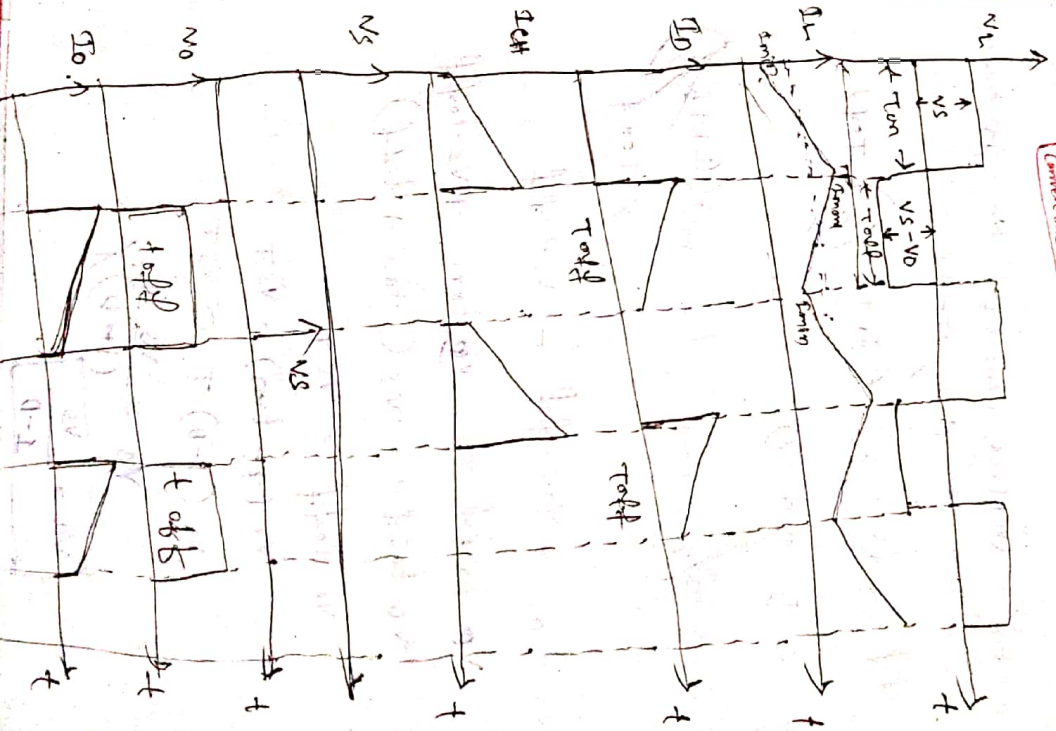

OR Avg of V_0

During ON time

$$I_{CH ON} = (\text{Voltage across } L) \text{ (average current through } L) T_{ON}$$

$$I_{CH ON} = V_S (I_1 + I_2/2) T_{ON} \quad \text{--- (1)}$$

During off time

$$I_{CH OFF} = (\text{Voltage across } L) \text{ (average current through } L) T_{OFF}$$

$$I_{CH OFF} = (V_0 - V_S) (I_1 + I_2/2) T_{OFF} \quad \text{--- (2)}$$

Equating eq 1 and 2

$$V_S (I_1 + I_2/2) T_{ON} = (V_0 - V_S) (I_1 + I_2/2) T_{OFF}$$

$$V_S T_{ON} = V_0 T_{OFF} - V_S T_{OFF}$$

$$V_0 T_{OFF} = V_S T_{ON} + V_S T_{OFF}$$

$$V_0 T_{OFF} = V_S (T_{ON} + T_{OFF})$$

$$V_0 T_{OFF} = V_S T$$

$$V_0 (1-D) T = V_S T$$

$$V_0 = \frac{V_S}{1-D}$$


$$V_0 = \frac{V_S}{1-D}$$

$$V_0 = \frac{V_S}{1-D}$$

According to quadrant rule chopper are classified

- (1) Type 'A' or 1st quadrant
- (2) Type 'B' or 2nd quadrant
- (3) Type 'C' or two quadrant type 'A'
- (4) Type 'D' or two quadrant type 'B'
- (5) Four quadrant type 'E'

(1) First quadrant or type A chopper

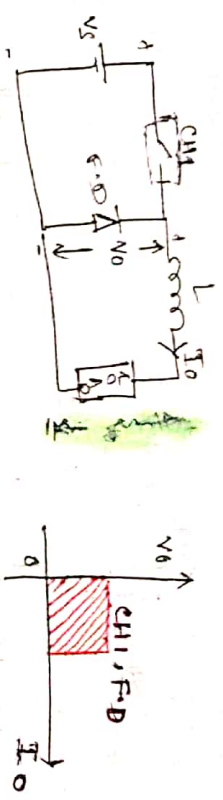


When chopper CH1 is ON, $V_0 = V_S$ and current I_{IO} flows through the load.

When CH1 is OFF, $V_0 = 0$ but i_{IO} in the load continues flowing in the same direction through free wheeling diode F.D.

It is thus seen that average values of both load voltage and current i.e. V_0 and I_{IO} are always +ve. That's why it is called 1st quadrant chopper.

The power flow in type 'A' chopper is always from source to load. This chopper is also called step down chopper as average o/p voltage V_0 is always less than the i/p dc voltage V_S .

It is called motoring mode of chopper.

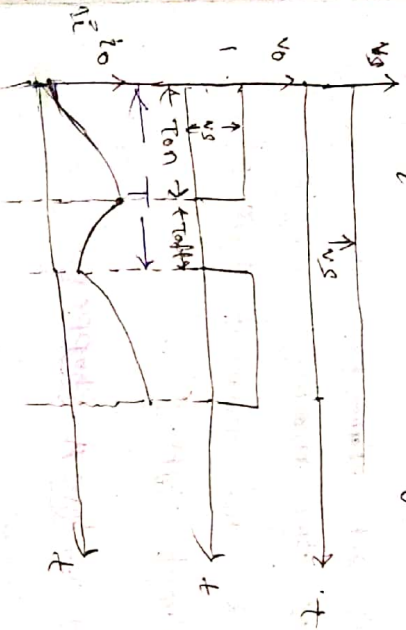

$$V_o = \frac{1}{T} \int_0^{T_{on}} V_s dt$$


$$= \frac{V_s}{T} \int_0^{T_{on}} dt$$

$$= \frac{V_s}{T} T_{on}$$

$$V_o = 0 \text{ to } V_s$$

$$0 < \frac{T_{on}}{T} < 1$$

2) Second quadrant, or type B chopper:

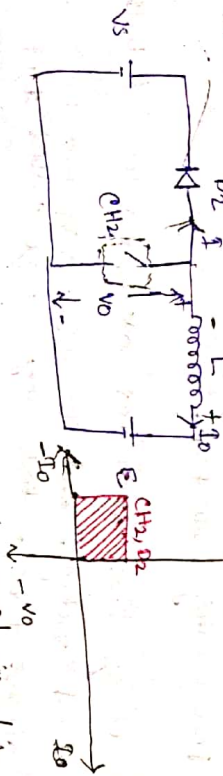

In this chopper the load must contain a dc source E, like a battery (or a dc motor) for any chopper.

voltage E


When CH2 is on, $V_o = 0$ but load drives the current through L and CH2. Inductance L stores energy during T_{on} in period of CH2. When CH2 is off, $V_o = (E + VL)$ or $(V_o = E + L \frac{di_L}{dt})$. As a result, exceeds source voltage V_s . As a result, diode D2 is forward biased and begins conduction, thus allowing power to the source.

Chopper CH2 may be on or off, current I_o flows out of the load, current I_o is treated as negative. Since V_o is always positive and I_o is negative, power flow is always from load to source. so it is operate in 2nd quadrant.

As load voltage $V_o = (E + L \frac{di_L}{dt})$ is more than source voltage V_s , type-B chopper is also called step-up chopper.

Both type A and type B chopper configuration have a common negative terminal between their 1/P and 0/P ends.

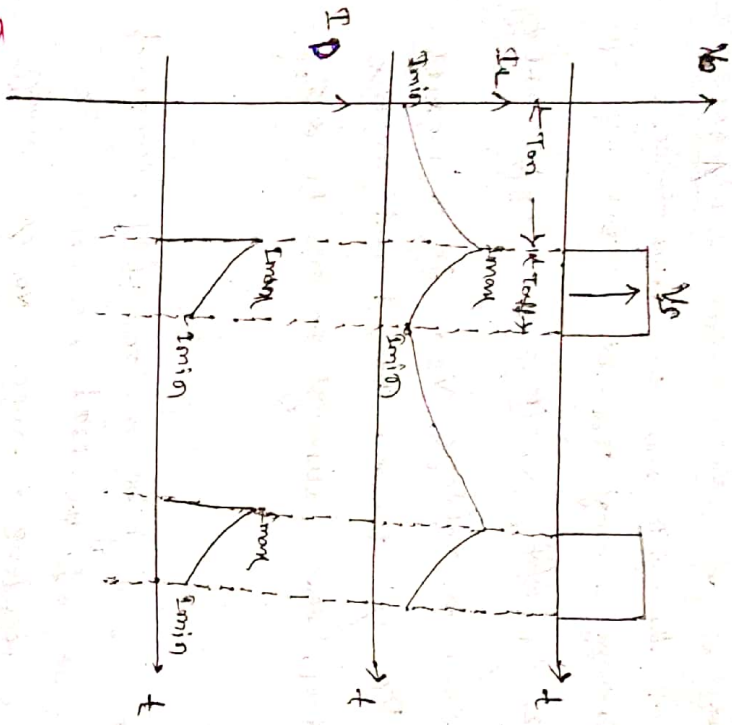In second quadrant operation of class B chopper motor is in the regenerative braking mode.





③ Two quadrant type-A chopper or type-C chopper:-

→ This type of chopper is obtained by connecting type-A and type-B chopper in parallel. The output voltage V_o is always positive because of the presence of free-wheeling diode. FWD across the load.

~~When switch is on or chopper is on~~
~~freewheeling diode~~ FWD connects

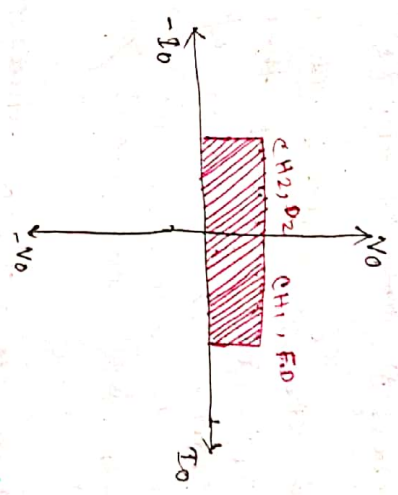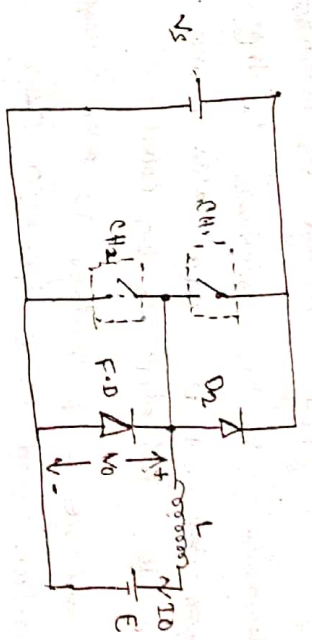To obtain first quadrant operation we should switch ON chopper CH1 and for getting second quadrant operation we should switch ON chopper CH2.



Case-1: when CH1 is switched ON/off:-

→ when chopper CH1 is switched ON, source V_s directly gets connected to the load and hence load voltage V_o is equal to source voltage. The direction of load current is from source to load as shown in the circuit diagram which is assumed positive.

→ when CH1 is switched OFF, the free-wheeling diode FWD comes in to the circuit as it gets forward biased and hence shorts the load.

→ Therefore, the output voltage V_o becomes zero. However, the " i_o " continues to the down through the F.D. and also some direction in the inductor to the load.

→ Hence the average o/p voltage V_o and current I_o are positive and hence operation of chopper is in first quadrant. In fact it is the class 'A' mode of operation.

Case - 2: when $e_a > V_o$ switched ON, load current through CH_1 is switched ON, load DC source " E " drives current through CH_2 and load. The direction of current will be opposite direction, through the load, so it is assumed negative.

→ out put voltage V_o is zero during this time.

→ when CH_2 is made off, diode D_2 gets forward biased and hence the current flows into the source from the load. The output voltage V_o is in this time as the load is connected to the source through D_2 , during off time of chopper CH_2 .


→ Thus the load current is always regenerative, the operation of chopper is with in second quadrant. In fact it is the class-B mode of operation.

→ The average load voltage is always positive but the average load current may be positive or negative.

→ Therefore power flow may be from source to load. (first quadrant operation) or load to source (second quadrant operation).

→ CHOPPERS CH_1 and CH_2 should not be ON simultaneously as this would lead to direct short circuit on the supply lines.

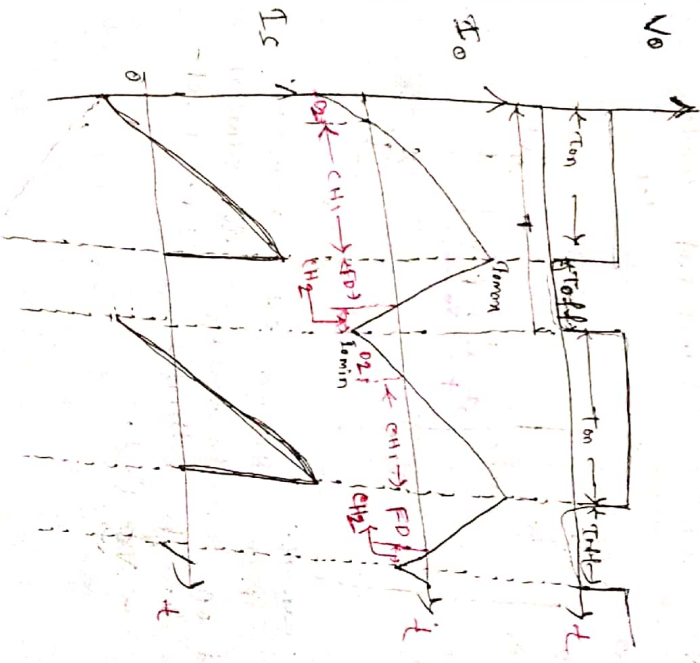→ It is used for motoring and regenerative braking of DC motors.



11) Type D chopper or two quadrant type B chopper:

This chopper works in first as well as fourth quadrant therefore the output current remain positive but output voltage may be either positive or negative.

The polarity of output voltage depends upon chopper ON time and chopper off time.

if $D > 0.5$ $T_{ON} > T_{OFF}$ \rightarrow output voltage +ve.


if $D < 0.5$ $T_{ON} < T_{OFF}$ \rightarrow output voltage negative.

if $D = 0.5$ $T_{ON} = T_{OFF}$ \rightarrow output voltage zero.



First quadrant:

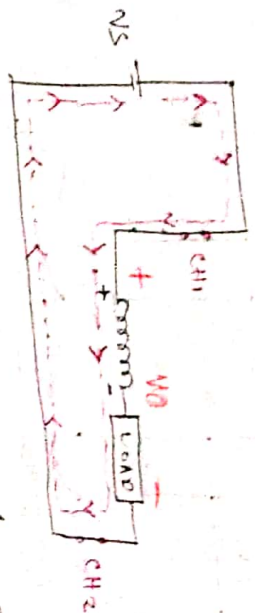
* when chopper CH1 and CH2 both are switched on simultaneously, the current flows through path (1) $V_s - CH1 - Load - CH2$ - $V_s (-)$.



The load across V_s and current increase upon efficiency because $(V_0 = V_s)$ and current flows in first quadrant because the output voltage and output current both are positive.

Fourth quadrant:

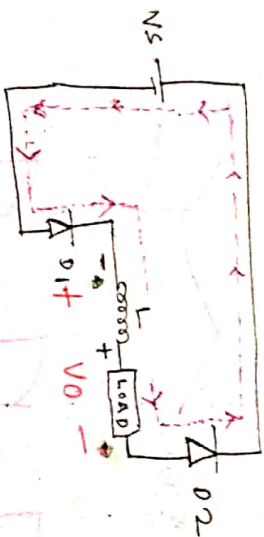When chopper CH1 and CH2 are off simultaneously, the diode D1 and D2 are forward biased and current flows through path $Load - D2 - D1 - Load$.



The chopper works on 4th quadrant because the output voltage is negative and output current is positive.

The application of type D chopper is in the forward motoring and regenerative braking of motor.

Four quadrant chopper, on type - E

chopper :-

* A four quadrant chopper is a chopper which can operated in all the 4 quadrants.

* The power can flow either from source to load or load to source in this chopper.

* In first quadrant, a class E chopper acts as a step down chopper whereas in second quadrant it behaves as a step up chopper.

* It consist of four semiconductor switches CH_1 to CH_4 and four diodes D_1 to D_4 in antiparallel.


* Numbering of choppers CH_1, \dots, CH_4 corresponds to their respective quadrant operation.

* first quadrant operation, only CH_1 is operated and second quadrant operation, only CH_2 is operated and so on.

First quadrant operation :-

For first quadrant operation, CH_1 is kept ON, CH_2 kept OFF and CH_3 & CH_4 kept OFF.

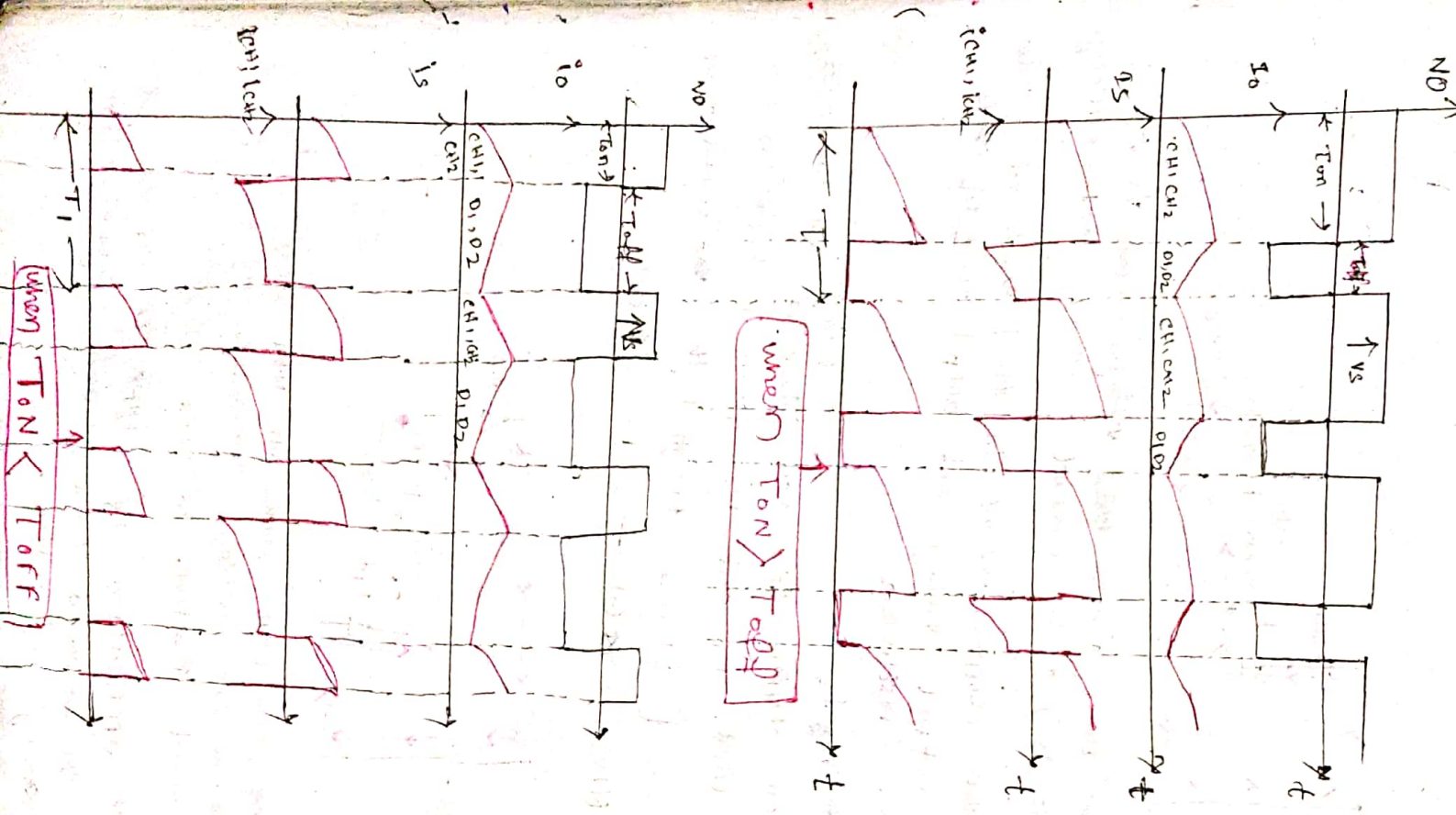When both CH_1 & CH_4 are ON simultaneously, the load gets directly connected to the source and hence the output voltage becomes equal to the source voltage ($V_o = V_s$). It may be noted that the load current flows from source to load as shown by the direction of i_o .



→ when CH_1 is switched off, the load current (free wheels) through CH_4 , D_2 .

→ During this period, the load voltage and current remains positive.

→ Thus, both the output voltage V_s and load current is positive and hence, the operation of chopper is in first quadrant.

→ It may be noted that, class-E chopper operates as a step down chopper in this case.


Second quadrant operation:

→ To obtain second quadrant operation, CH_2 is operated while keeping the CH_1 , CH_3 & CH_4 off. When CH_2 is ON, the DC source in the load drives current through CH_2 , D_4 , E and L . Inductor L stores energy during the on period of CH_2 .


→ When CH_2 is turned off, current is fed back to the source through D_1 , D_4 , E and L . This point that $(E + L \frac{di}{dt})$ should be noted as the source voltage V_s .

$(V_s < E + L \frac{di}{dt})$

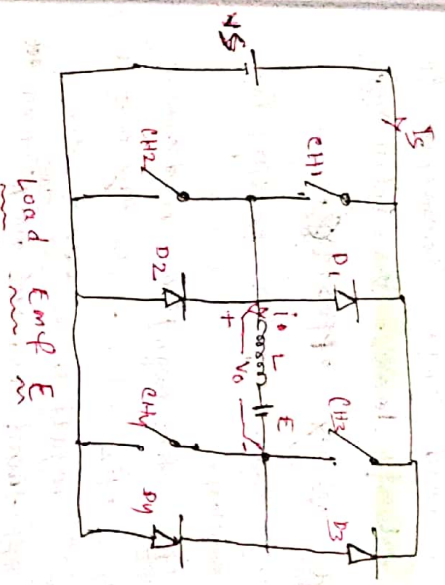→ As load voltage " V_o " is +ve and " I_o " is -ve, it is second quadrant operation of chopper. Hence load is transferring power to the source. So if it is the configuration of step up chopper.



Load EMF E

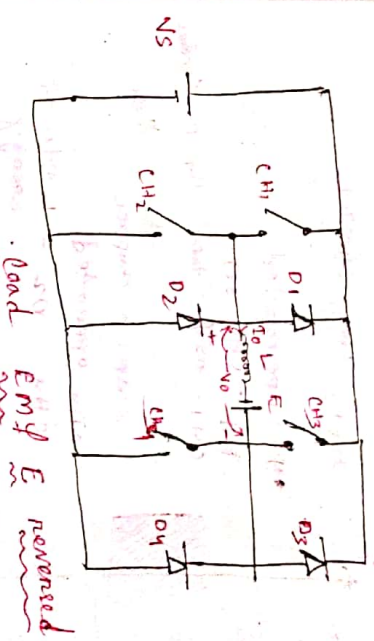

Load EMF E reversed

Third quadrant operation:


→ To obtain third quadrant operation, both the load voltage and load current should be negative. It is due to by changing the polarity of EMF " E " in load.

→ For third quadrant operation, CH_3 & CH_4 are kept off, CH_2 is operated.

Load \rightarrow CH2 \rightarrow CH3 \rightarrow Load

\rightarrow when CH3 is ON, load gets connected to source voltage "Vs". But here the polarity of load voltage is opposite. So that both are negative leading to 3rd quadrant operation.

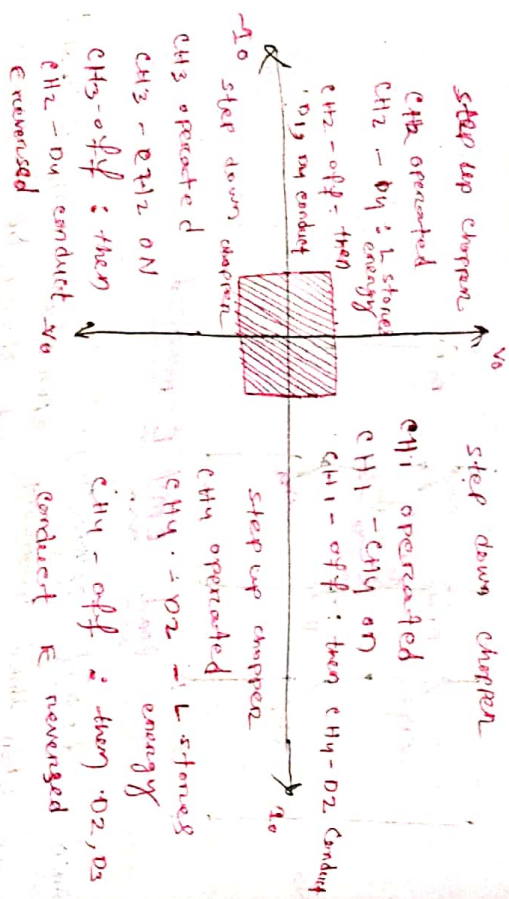\rightarrow when CH3 is off, the negative load current flows through CH2, D4. In this manner CH2 operates in third quadrant and choppen at fourth quadrant operation.



Fourth quadrant operation:

\rightarrow To obtain 4th quadrant operation, CH1, CH2 & CH3 operated while keeping CH4, CH4 & CH3 off. The polarity of load emf "eL" need to be reversed.

\rightarrow when CH4 is turned ON, positive current flows through CH4, D2, L and E.

\rightarrow inductance L stores energy during the time CH4 is ON.

\rightarrow when CH4 is off, current fed back to the source through diodes D2, D3. Here load voltage is negative but the load current is always positive.

\rightarrow This leads to choppen operation in 4th quadrant. Here, power is fed back to the source from load and choppen act as a step up choppen.

control modes of choppen:

There are two kinds of control strategies used in DC choppen namely 1) time ratio control and 2) current limit control.

1) In all situations, the average o/p voltage can be changed. The differences between these two can be discussed below.

1) Time ratio control:

In the time ratio control the value of the duty cycle D is changed. Here D is duty cycle, $D = \frac{T_{ON}}{T}$ is ratio.


→ There are two ways to achieve the time ratio control namely (a) variable frequency and (b) constant frequency operation.

(b) constant frequency operation:

→ In constant frequency operation, the ON time " T_{ON} " is changed, keeping the frequency, i.e. $f = \frac{1}{T}$, or time period " T " constant.

→ This operation is also named as PWM (Pulse width modulation control).

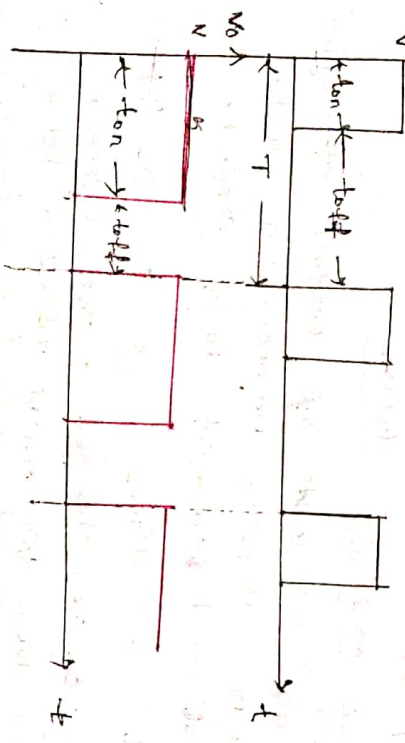
→ Hence the output voltage can be changed by changing ON time. AS the frequency is fixed the design of filter is easy. But it is why it is the widely used method.



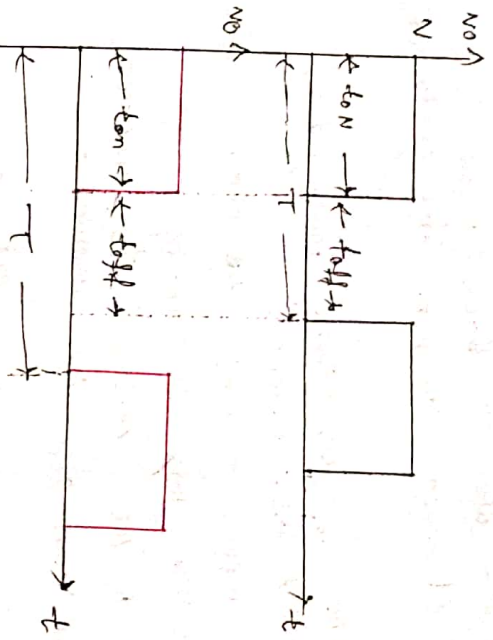(a) variable frequency operation:


In this operation, frequency ($f = \frac{1}{T}$) is changed, then the time period " T " is also changed.

→ This is also named as Imp Frequency modulation control. In both cases, the o/p voltage can be changed with the change in duty ratio.



→ So frequency keep varying, that is why it is difficult. So design filter for this control.

(2) current limit control:

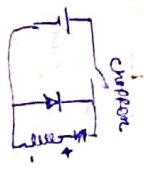

→ In a DC to DC converter, the current value varies between the minimum as well as the maximum level of constant voltage. In this method, the DC to DC converter is turned ON and OFF confining that current is preserved constantly between the upper limits and also lower limits.


→ it is called on load energy storage element.
 → The ON & OFF time of the chopper

→ The chopper adjust automatically. Beyond the upper limit the current increase, turned off.

→ The load current free wheels and starts to decrease. when it falls below the lower limit the chopper ON. It turned ON.

→ The amplitude of the ripple controlled by proper limits of current.

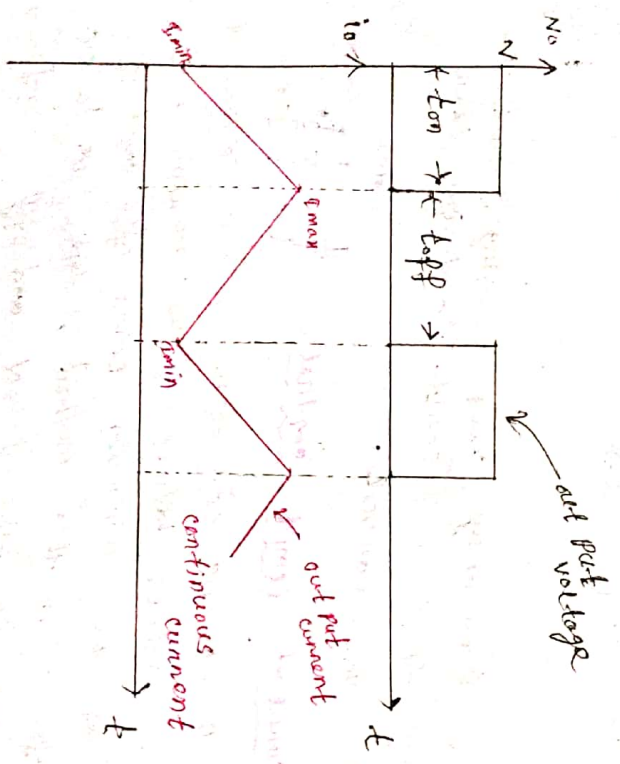→ The lower ripple current, the higher chopper frequency. By this switching losses increase. In this process discontinuous conduction can also be avoided.



Inverter:
 → Inverter is an electronic circuit which converts DC power into AC power.

Series inverter:
 → The inverter circuit in which the commutating elements L and C are under damped circuit with the load is form inverter. This circuit is called series commutated or load commutated inverter.

→ It is called load commutated inverter because the load components (L & C) are responsible to turn off the thyristor.


→ It is called self commutated inverter because in this circuit the thyristor turns off. It is operation is same like as class A commutation.

→ Series inverter operation at high frequency 200 Hz to 100 kHz.

→ Here, the value of L and C is chosen in such a way the R, L & C formation underdamped circuit.

Power circuit diagram:

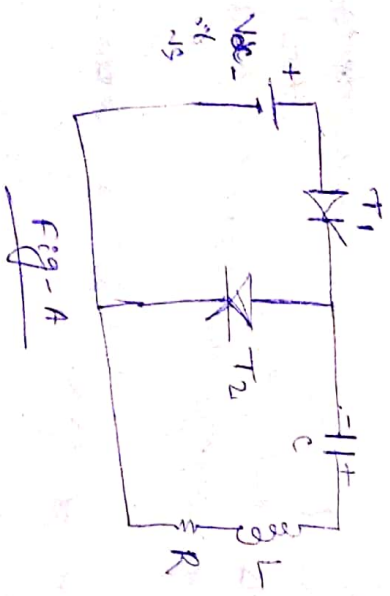- The power ckt diagram of the series inverter are shown in fig.
- The SCR T_1 & T_2 are turned on at regular interval in order to achieve desirable output voltage and frequency.
- The T_2 is kept off at starting condition. and the polarity of capacitor is shown in figure (A).
- The ckt consist of L and C connected in series with load (R).



Operation:

Mode-1

- The voltage V_B applied to RLC series ckt as soon as the SCR T_1 is turned on.
- The polarity of capacitor charging is shown in the fig B.
- T_2 is turned off.

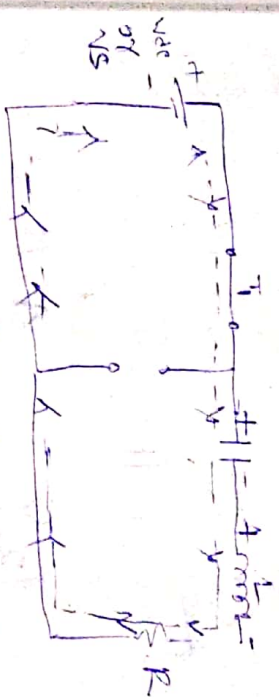


Fig-5

- So current flow from supply V_S to T_1 to load to back to V_S .
- The nature of the load current is alternating due to the inductor (L) starts charging.
- So this time the capacitor (C) starts discharging gradually from $-V_C$ to its maximum voltage.
- In this time voltage across capacitor becomes $+V_C$ at voltage across load current becomes zero.
- When the load current becomes zero the voltage across capacitor becomes $+2V_S$.
- When the load T_1 automatically turns off at point 'a'.
- When the load current becomes zero the thyristor T_1 automatically turns off at point 'a'.

Mode-2 → The load current requires zero from a to b as the SCR T_1 turns off. In this time period, the SCR T_1 and T_2 once turned off becomes equal to V_s and voltage across capacitor becomes equal to V_s .

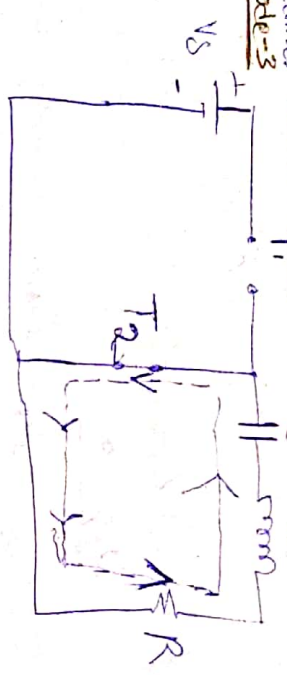


Fig-2

→ In this mode we give firing pulse to thyristor T_2 . So, T_2 get forward bias. In this time capacitor starts discharge its energy from $+V_s$ to $-V_s$ through thyristor T_2 and R-L ckt.


→ Due to capacitor discharging reverse current flows across the load. Now at point 'c' the thyristor T_2 turns off. due to the load current becomes zero.

→ The thyristor T_2 turns off during point 'c' to 'D' and thyristor T_1 again turns ON. In this way cycle repeat.

→ Now we see in the waveform the time duration ab and cd is called as dead zone.

$$v_{rms} = \sqrt{v_m^2 - \frac{v_m^2}{2}} \quad v_o = \frac{1}{\sqrt{2}}$$
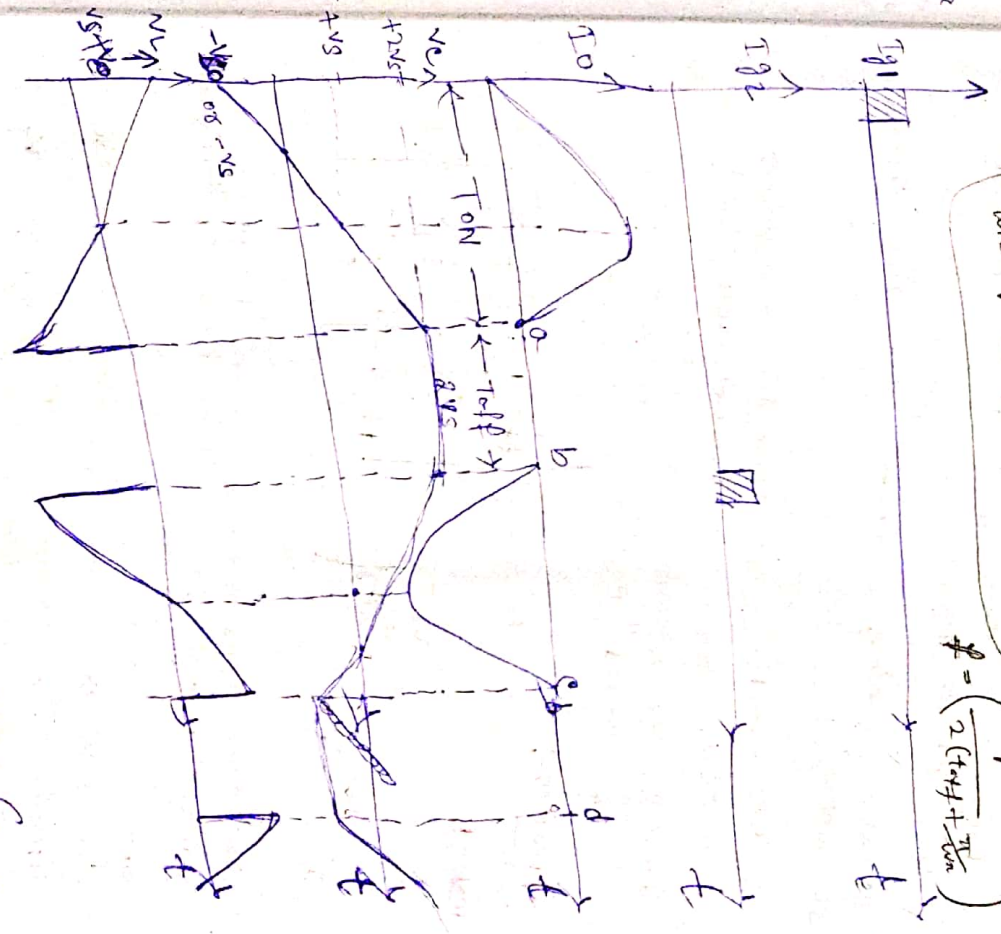
$$f = \left(\frac{1}{2(T_{off} + T_{on})} \right)$$



Application :- It is used high frequency generate high wave form.


- frequency induction heating.
- It is used for fluorescent lighting.
- For used in sonar transmitter.
- used in ultrasonic generator.

Single Phase Parallel Inverter: used to convert DC to AC.

→ It also produces a square-wave form from a DC supply.


→ In this inverter the commutating element capacitor comes in parallel with the load during the operation of inverter. it is called 'parallel operation'.

Mode-1

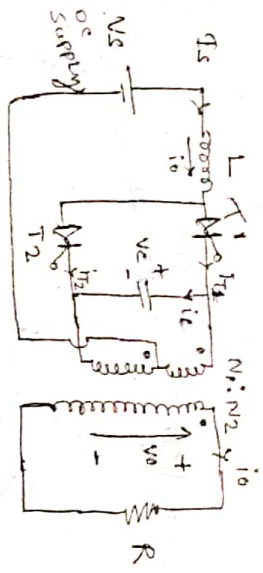

→ This mode begins when T_1 is fired and current flows through the inductor L and the thyristor T_1 .

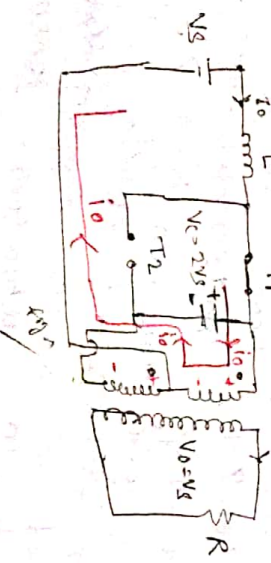
→ When SCR is turned on, a.c. voltage V_s appears across half of the transformer primary, which means the total primary voltage is $2V_s$. Hence the capacitor is charged to $2V_s$.



Mode-2

This mode begins when thyristor T_2 is fired. When T_2 is fired (reverse voltage) a cross T_1 , it will be turned off.

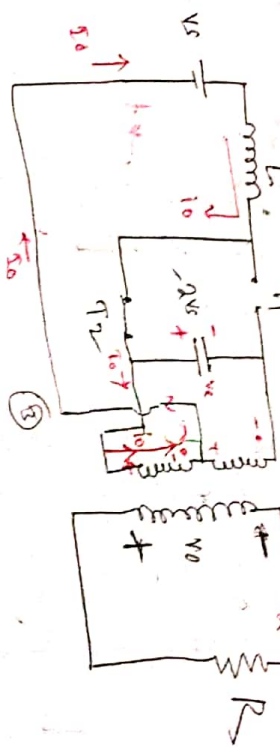
→ SCR T_2 will now be conducting and the voltage $2V_s$ will appear across the transformer primary and commutating capacitor, but with reverse polarity.




→ During mode 3, capacitor T_1 is again turned on (reverse) and capacitor applies voltage $-2V_s$ to appear across T_2 .

→ When this reverse voltage is applied for sufficient time across T_2 , it will be turned off.

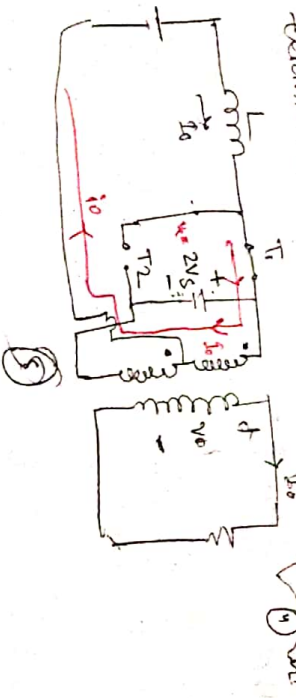→ If trigger pulse applied periodically to alternate thyristors an approximately rectangular wave form will be obtained at transformer terminals.



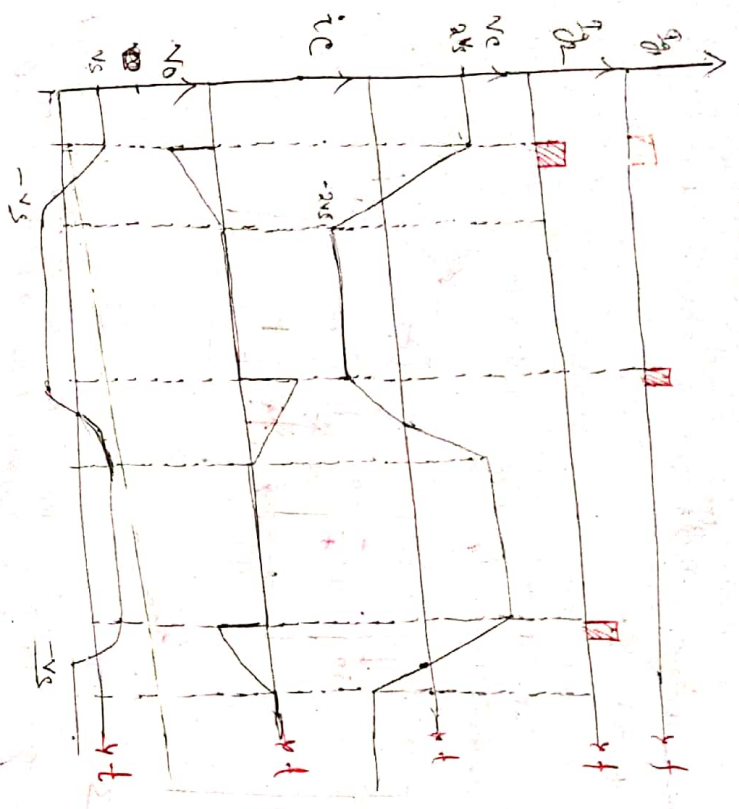



Single - Phase Bridge Inverters :-

- There are two types: (i) single phase half bridge inverter.
- (ii) single phase full bridge inverter.

In these circuits below two diagrams, the circuitry for turning on or turning off of the thyristors is not shown in the figure.

Single phase half bridge inverter :-

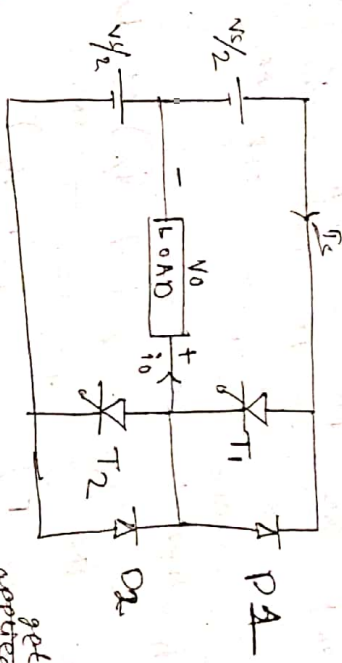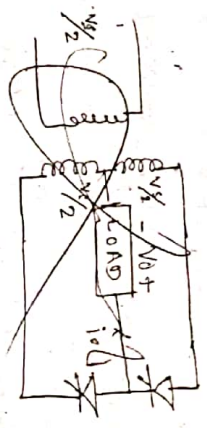Here, two thyristors T_1 & T_2 , two diodes D_1 & D_2 are used.



First of all, when we get pulse applied trigger pulse

Fig. 1: Thyristor T_1 then the thyristor T_1 starts to conducting from $0 < t < (t/2)$ or 0 to $t/2$ times

during this time T_1 conducts, load is directly connected to source " $v_s/2$ " on the upper arm.

$$V_o = \frac{V_s}{2}$$

As soon as thyristor is removed at time $t = \pi/2$, thyristor T_1 gets turned off. It may be seen from the wave form,

→ Such time t_2 is expressed and hence thyristor T_2 is turned on.

→ Thus, the load gets directly connected to the source ($V_s/2$) on the lower arm, o/p voltage

→ Note that the polarity of V_o on the source across T_1 and T_2 are opposite appearing across arm and opposite to each other.


→ During the time period $t_2 < t \leq T$ of $(T/2$ to $T)$, the T_2 thyristor is ON, the o/p voltage is $(-V_s/2)$.

Here the frequency of the o/p voltage contains by varying the time period T . No need to put θ here if there is no need to put θ .


D_1 & D_2 as o/p. Voltage and current are always in phase. Due to resistive load.

But in other load than purely resistive load i_o and v_o are not in phase to each other. For such case the diode connected in anti-parallel

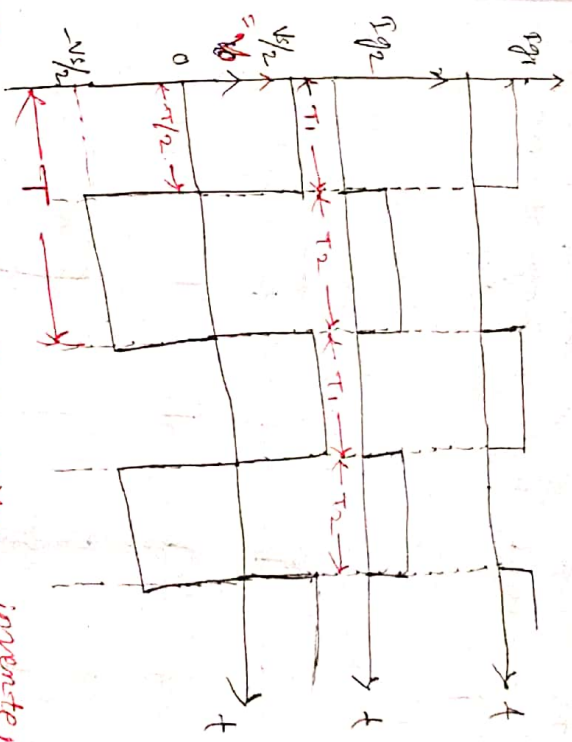with the thyristor will allow the current to flow when thyristor is turned off.




② single phase full bridge inverter:-

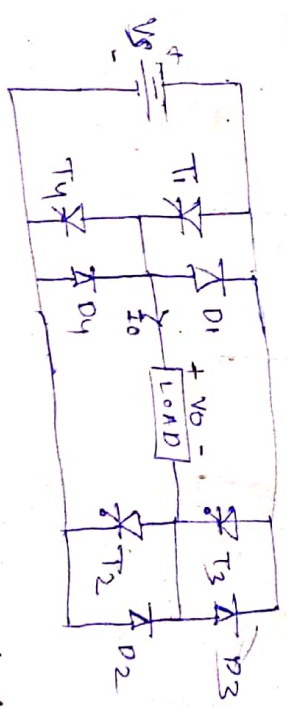

Diode D_1, D_2, D_3 and D_4 are called feedback diodes and they functions only when the load is other than resistive load.

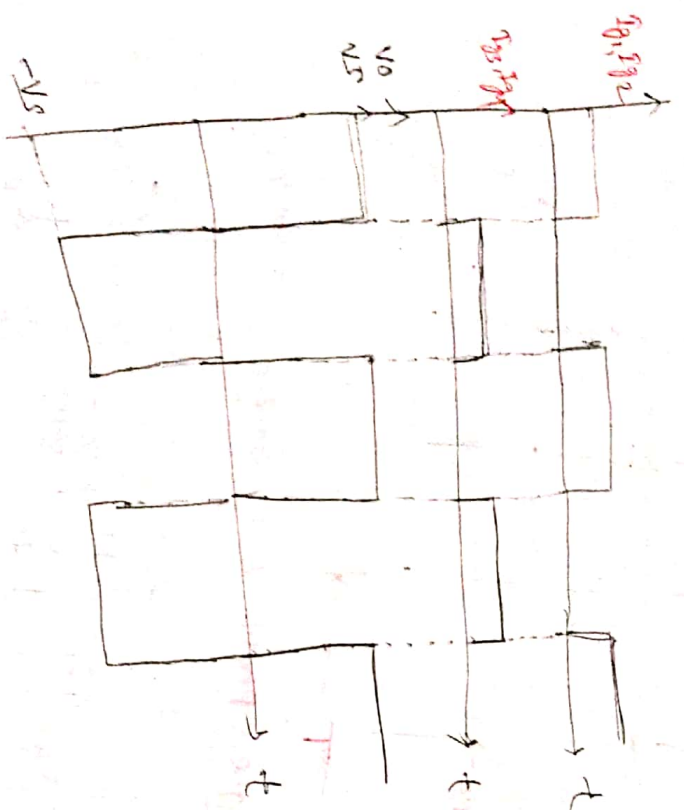For full bridge inverter, when T_1 , T_2 conduct, load voltage is V_s and when T_3 , T_4 conduct load voltage is $-V_s$. Here the frequency of the output voltage can be controlled by varying the periodic time T .



Cycle Converter:-

Cycle Converter:- It is a device which converts input power at one frequency to output power at different frequency. It also known as

cycle inverter.
 It converts from one frequency to AC power at another frequency. This process is known as AC to AC conversion.


Application:-

- speed control of high power AC drive.
 - induction heating.
 - startle of van compensator
 - For converting variable speed alternator voltage to constant frequency of AC for use as ship boards.
- Supplies in AC cycle converter
- There are two types of cycle converter

- 1) step up cycle converter ($F_o > F_s$)
- 2) step down cycle converter ($F_o < F_s$)

- 1) step up cycle converters
- ii) mid point type
- 2) bridge type

1) Mid point step up cycle converter

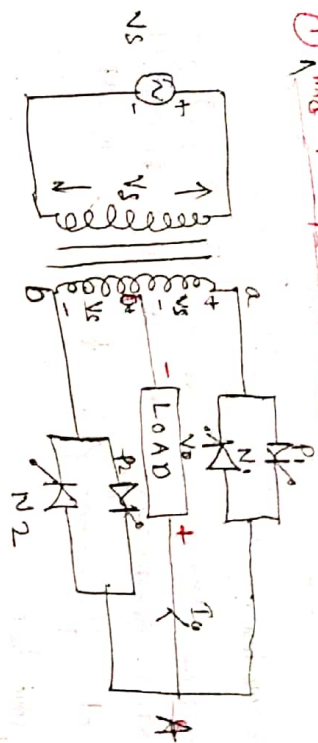



- It consists of a single phase transformer with centre tap on the secondary winding, and 4 thyristors.
- Two of these P1, P2 are for +ve group and another two of these N1, N2 are for -ve group.
- Load is connected between secondary winding mid-point '0' and terminal 'A'.
- During the half cycle terminal 'a' +ve with respect to 'b'. This time both P1 and N2 are forward biased along with '0' voltage is +ve with terminal 'A' positive and '0' negative.
- At instant wt, P1 force commutated and forward-biased thyristor N2 is turned on. So that load voltage is +ve with '0' terminal and 'A' -ve terminal.

- At wt, N2 force commutated and P1 turned on. The load voltage is now +ve with '0' and -ve with 'A' terminals.
- again at wt, N2 force commutated and P1 now force commutated. Load voltage is now -ve with 'A' and +ve with '0' terminal.
- such process continues from 0 to π .

- During -ve half cycle, terminal 'b' is +ve with respect to 'a'. Both P2 and N1 are forward biased from wt = π to 2π .
- At wt = π , N2 force commutated, they P2 is on.
- At time instant P2 force commutated and after some time N1 force commutated from thyristor P2.
- In this manner, the alternating high frequency and -ve cycle at a

- In this manner, P2, N1, in the alternating high frequency and -ve cycle at a



Bridge type step up cycle conversion:

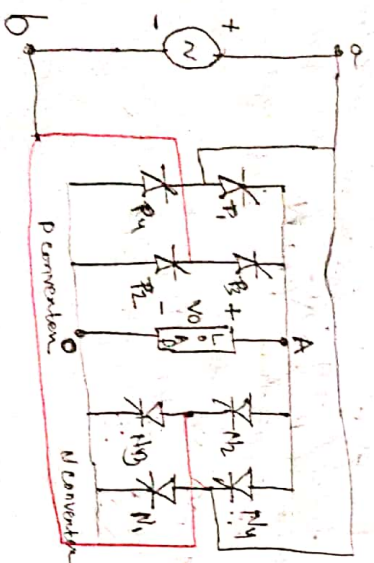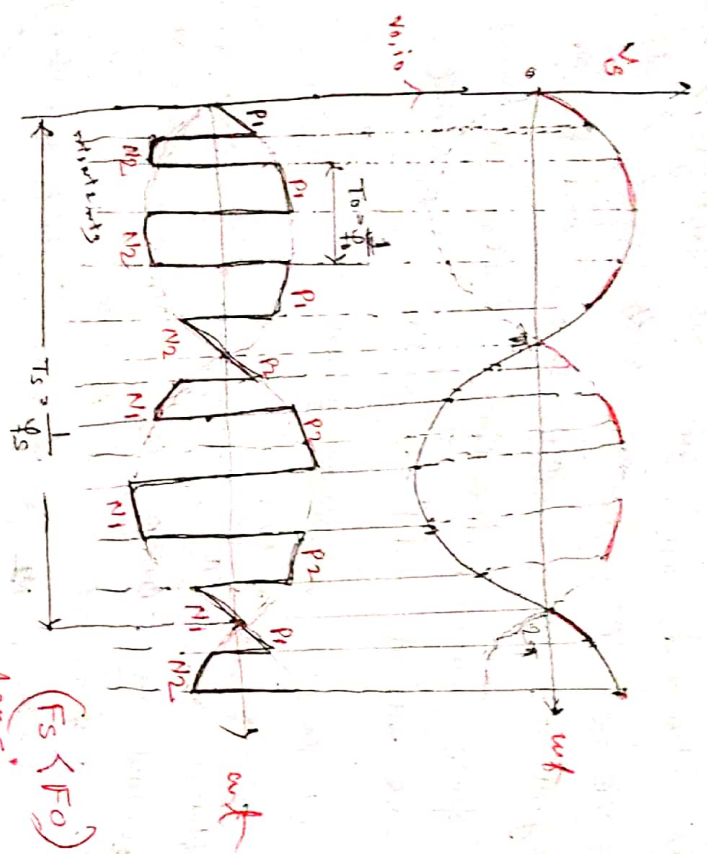

P_1, P_2 conduct
 N_1, N_2 force
 conduct
 P_1, P_2 force
 conduct
 N_1, N_2 force
 conduct

During the half cycle
 are forward biased. (a+ve & b-ve)
 During -ve half cycle
 one f.B. (a-ve & b+ve)

Step down cycle conversion

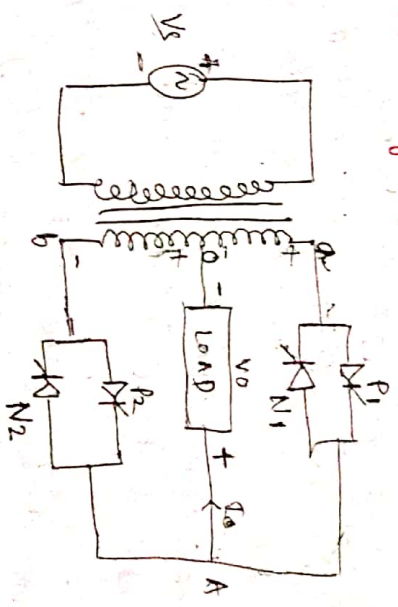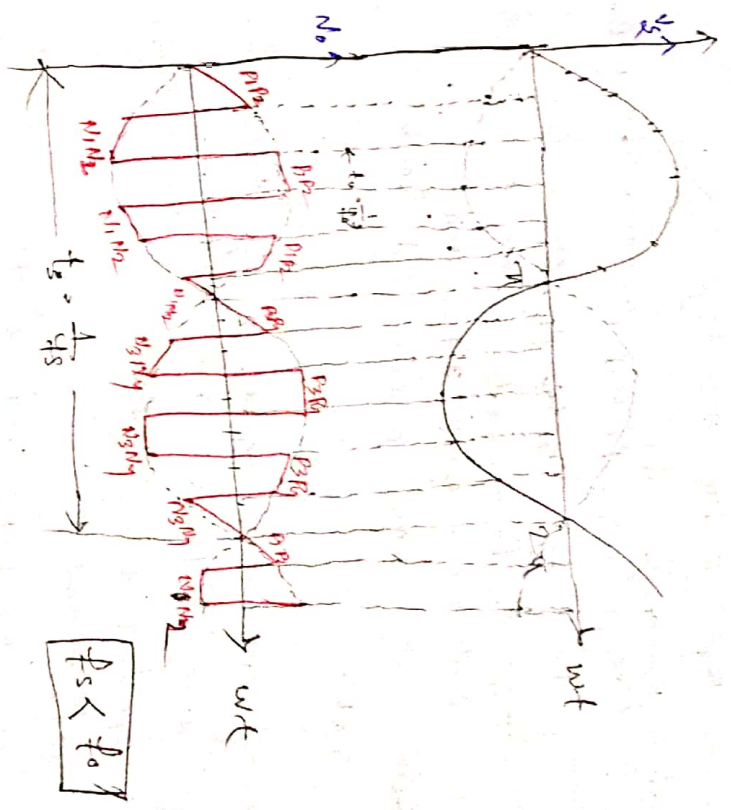

(i) solid point step down e-c
 (ii) bridge point step down e-c

Here, we use a ~~single~~ single phase 1 ϕ with centre tap on the secondary side.

and 4 thyristors used. At time $0 < t < \pi$ P1 and P2 conduct or F.B.

During the half cycle P1, P2 F.B. and triggered P1 thyristor. such time the load across voltage A(ve) and '0' -ve.

Such time a +ve and -ve terminal.


During -ve half cycle P3, P4 turned off by using natural commutation. they are applied the gate pulse to the thyristor P2 get turned on.

Such time "a" (ve) and "b" +ve terminal. The load across the voltage A +ve and '0' -ve.


after ^{instant} time from π to 2π during the half cycle when we applied a gate pulse to the N2 thyristor. we get +ve and (b) -ve and such time across voltage "0" +ve and load across voltage "0" +ve and A (-ve).

A (-ve). During -ve half cycle N1, P4 turn on, N2, P3 turn off commutation.

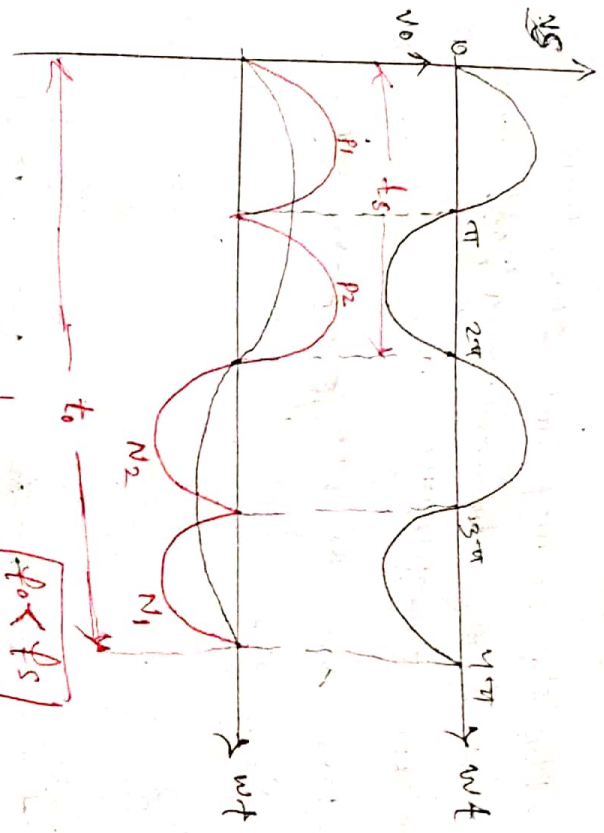Such time a +ve and b +ve terminal. Load voltage across the load "0" +ve and "a" -ve.



step down bridge cycle conversion.

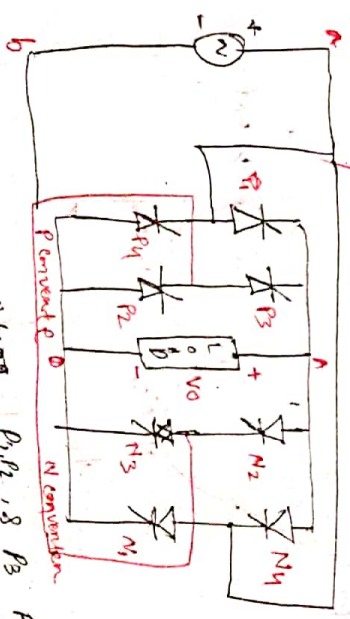

conduct.


At a time $0 < t < \pi$ P1, P2, P3, P4 one conduct.

Therefore during -ve cycle P3, P4 conduct and during +ve cycle P1, P2 conduct by natural commutation.

the load across voltage A +ve and 0 -ve after the time instant conduct.

During the half cycle N_1 & N_2 conduct and during -ve half cycle N_3 & N_4 conduct but such time N_1 & N_2 automatically kept due to natural commutation.

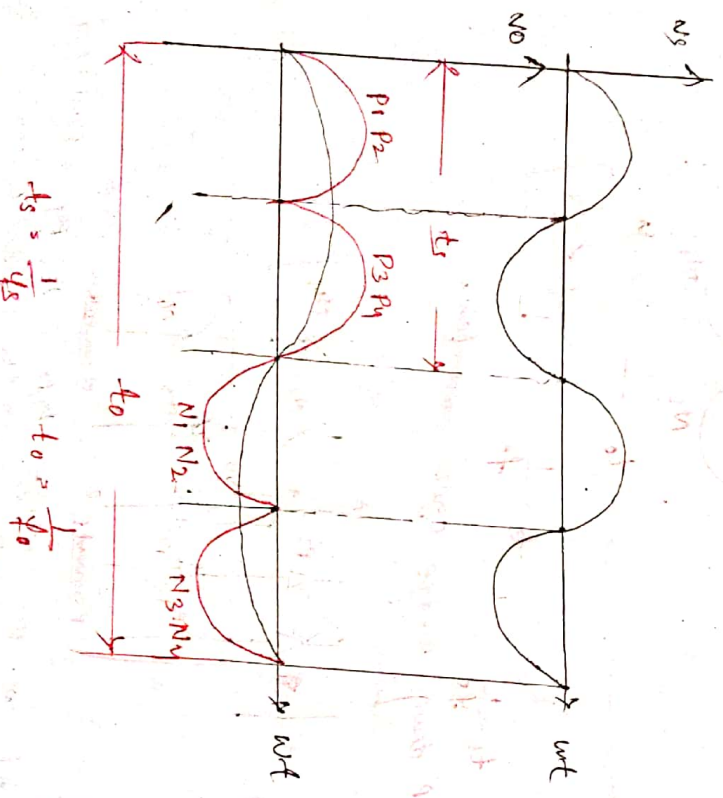Load across the voltage (A) -ve and '0', +ve.



Power electronics - (Ckt used)



it is used rolling mills, cement mills, compressors, pumps, fans, elevators etc.

Factor affecting the speed of a d.c. motor:

The flux

$\Sigma \phi$

ΣT

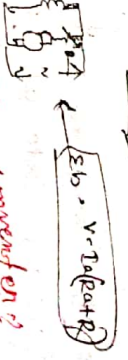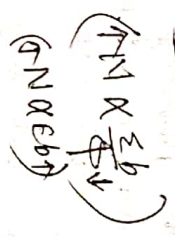


speed control of DC shunt motor using

we know the the DC shunt motor is excited separately flux motor like separately excited or

so that the speed control of DC shunt motor is similar to separately excited D.C. series motor.

we take a full wave converter for the control of speed by varying the voltage control method.

Let $V = V_{max} \sin \omega t$

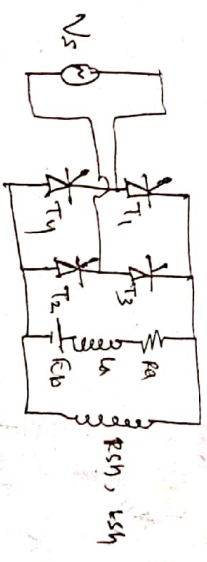

Here a thyristor are used for control the speed of dc motor.

At a typical only two thyristor are operated. mode - 1 (fire cycle)

in every half cycle if given T_1 & T_2 are conducted with providing gate pulse.


So that the current flows through armature winding as well as field winding, but the armature current is controlled by using external resistance, similarly the field current is controlled by using external resistance their own.

For this mode the current path is $V_s \rightarrow T_1 \rightarrow$ armature & field winding $\rightarrow T_2 \rightarrow V_s$

mode - 2 (we will cycle) when -ve half cycle is given the T_1 & T_2 are reversed biased and with one forward biased & give to proper gate pulse with they are operated and again the current passes through both armature and field winding, and again both current are controlled by their external resistance.

we know: $N = \frac{V_s}{\omega} = \frac{V_s}{2\pi f}$
 $N = \frac{V_s}{2\pi f} = \frac{V_s}{2\pi \cdot \frac{2\pi \cdot 60}{60}} = \frac{V_s}{4\pi \cdot 60}$

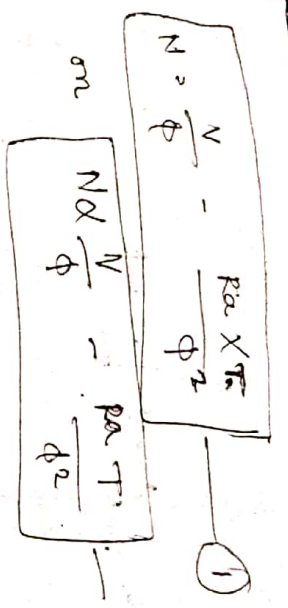$T \propto \phi I_a$
 $I_a \propto \frac{T}{\phi}$



and for continuous conduction

$V_a = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t \, d(\omega t)$

$V_a = \frac{2V_m}{\pi} \cos \alpha$ (2)


So we can get part in eqn (1)

$N = \frac{V}{\phi} - \frac{Ra T}{\phi^2}$
 $= \frac{2V_m \cos \alpha}{\pi \phi} - \frac{Ra T}{\phi^2}$
 $N = \frac{2V_m \cos \alpha}{\pi \phi} - \frac{Ra T}{\phi^2}$ (3)


So that of $0 \leq \alpha \leq \pi/2$ there the speed of dc thyristor. $N \propto \frac{V_m}{\phi}$ only.

If $0 < \pi/2 \leq \alpha \leq \pi$ then the speed of dc thyrist motor $N = \frac{V_m \sin \alpha}{\phi}$

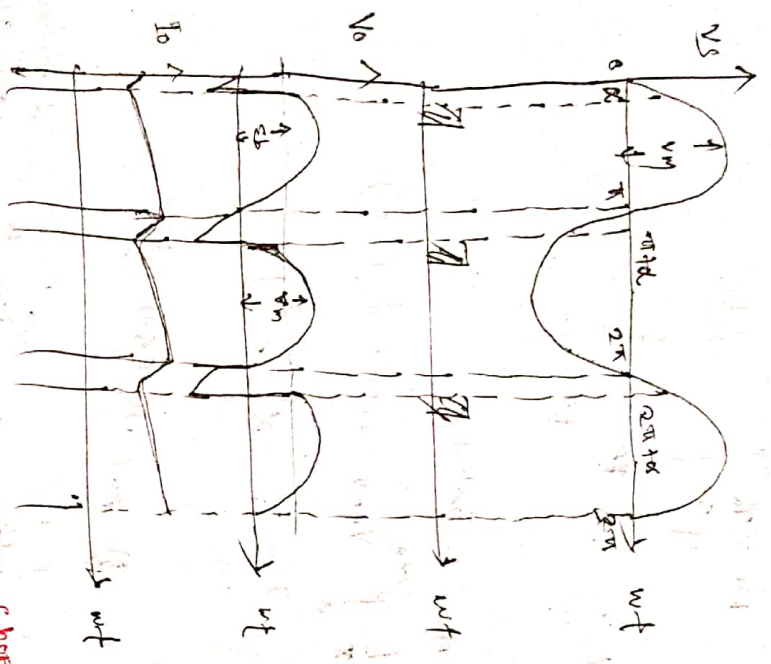Let take $\frac{2V_m}{\pi} =$ max avg of dc thyrist motor. this voltage value is equal to the rated terminal supplied voltage.




Speed Control DC motor using Choppers:

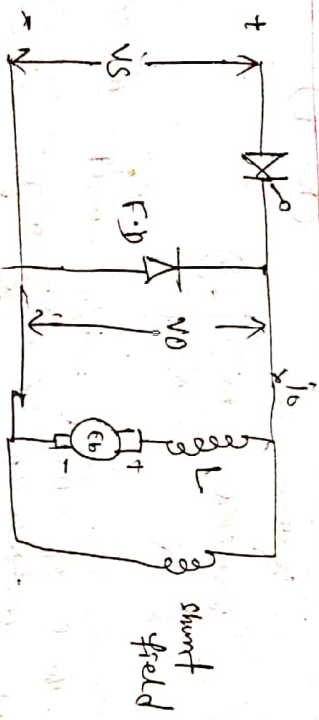

→ the firing slows the speed control of D.C. shunt motor using choppers.
 → when the chopper is on, the output is applied to the motor and the energy will be stored in the inductance, which is connected in series with the armature winding.

It is expensive than the DC series motor, because the off period of the chopper, the inductance energy will be utilized for the flow of current through the

f.o.d.

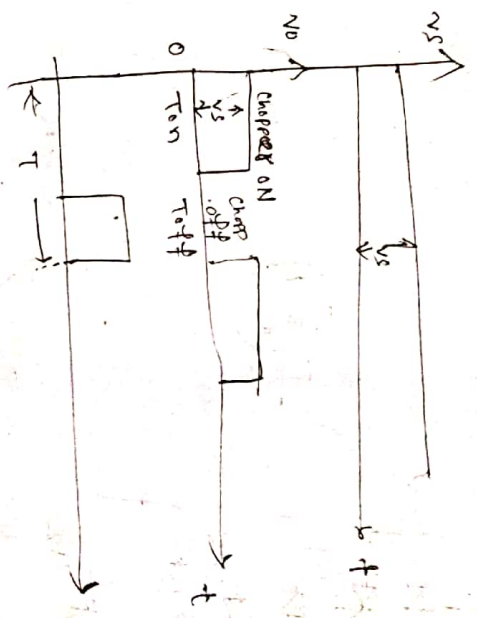

The avg motor voltage

$$V_o = V_t = \frac{T_{on}}{T} \times V_s = DV_s$$

$$V_o = 0 \text{ V}$$

$$D = \text{duty cycle}$$

$$D = \frac{T_{on}}{T}$$

$$f = \frac{1}{T}$$

$$V_o = f \times T_{on} \times V_s$$

$$T_{on} = \text{time on}$$

$$V_o = \text{avg voltage}$$


$$f = \text{frequency}$$

$$V_s = \text{source voltage}$$

List the factors affecting the speed of an motor:

- frequency and V/f
- pole changing
- Rotor resistance
- Stator resistance

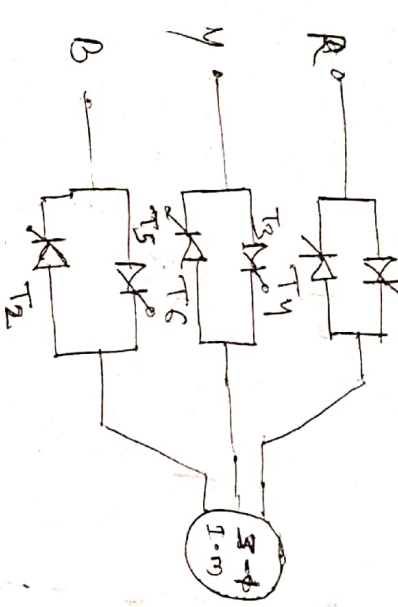→ Speed control of induction motor by using AC voltage regulation.



In 3 ϕ in the voltage is controlled by using 3 ϕ AC regulator.

$$T = \frac{3}{\omega_s} \cdot \frac{s \cdot E_2^2 \cdot R_2}{R_2^2 + (s X_{2g})^2}$$

$$T \propto E_2^2$$

→ AC voltage controlled one employed to vary the RMS value of the alternating voltage applied to a load etc by introducing thyristors between the load and the constant voltage sources.

The RMS voltage applied load etc is controlled by controlling the triggering angle of the thyristor in the ac voltage controller ckt.

→ An AC voltage controller is a type of thyristors is used to convert a fixed voltage fixed frequency ac input supply to obtain a variable voltage AC output.

→ The ac power flow to the load and the RMS voltage is controlled by varying the trigger angle ' α '.

→ The 3 ϕ load are connected in star or delta.

→ Resistance connected all 3 ϕ are equal.

→ Two thyristors are connected back to back and used per phase, Hence need six of 6 thyristors.


→ The current flow is bidirectional, with three current in one direction in positive half and other in negative half.

→ The thyristor are fired in the sequence of natural commutation time.

→ To turn the thyristors ON, the anode voltage must be higher than the cathode voltage. and also applied gate pulse to the thyristor.

→ The turning off the thyristor is its current falls to zero.

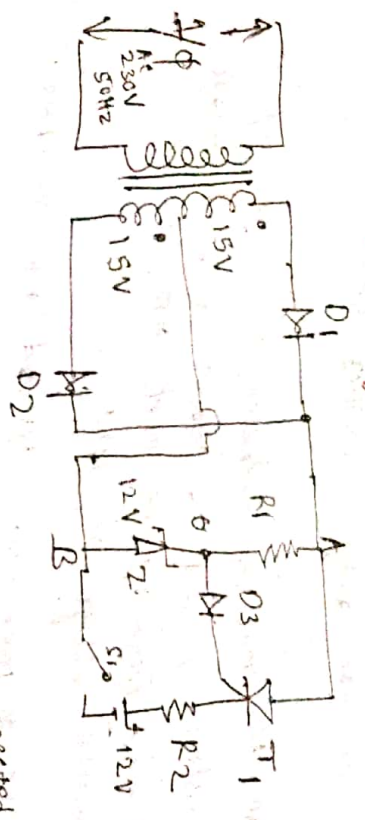Battery charger kkt using SCR with the help of diagram.



A 12V discharged battery is connected in the series SCR. when switch S1 is closed.

The single ϕ 230V supply is stepped down to (15-0-15V) by a centre tapped transformer.

Diode D1 and D2 forms full-wave rectifier. Due to this, the pulsating d.c supply appears across terminals A and B.


The maximum voltage at point "A", is 12V due to zener diode.

during each positive half cycle when the potential of point A rises to sufficient level so as forward bias diode D3 and gate - cathode junction of SCR F.B.

when the SCR is turn on, the charging current flows through battery & starts charging.

when the battery is fully charged, the cathode of SCR is held at 12V. So, diode D3 and gate - cathode junction of SCR cannot forward biased. Hence, no gate current is supplied and SCR is not triggered. In this way, after full charging function charging is automatically off.

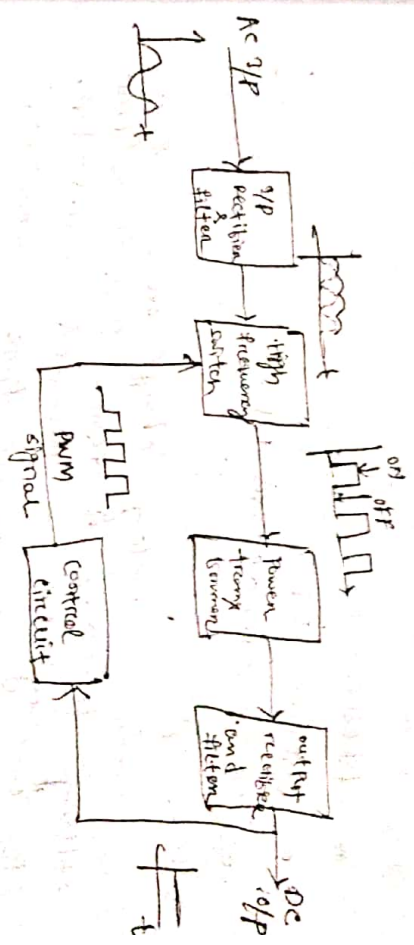what is snubber? it stands of switch mode power supply. it is a device which provides some kind of electrical load and works on high frequency switching action.




Working of UPS with block diagram.

Introduction:-

An uninterrupted power supply, is an electrical apparatus that provides emergency power to a load when the input power source fails.

Block diagram UPS:-

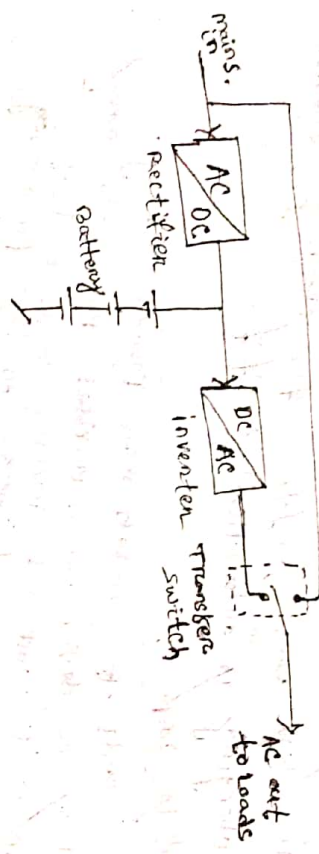

Types of UPS:-

There are three types of UPS are available:

- offline UPS.
- online UPS.
- line interactive UPS.

offline UPS:-


The mains to battery change over time in offline UPS is very low as compared to inverter. In inverters change over time is 3-8 msec. But offline UPS have of 3-8 msec. In a time when mains are present, inverter provides the output as if the input mains.

→ while, offline UPS has built automatic voltage regulation (AVR) to regulate the output voltage close to 220V ac.

→ offline UPS are normal weight used for domestic computers.

→ when the power failure occurs, the transfer switch will select the stand by system. Thus we can clearly see that any AC failure in mains. In this system, the stored voltage is first rectified and connected to the battery. rectifier.

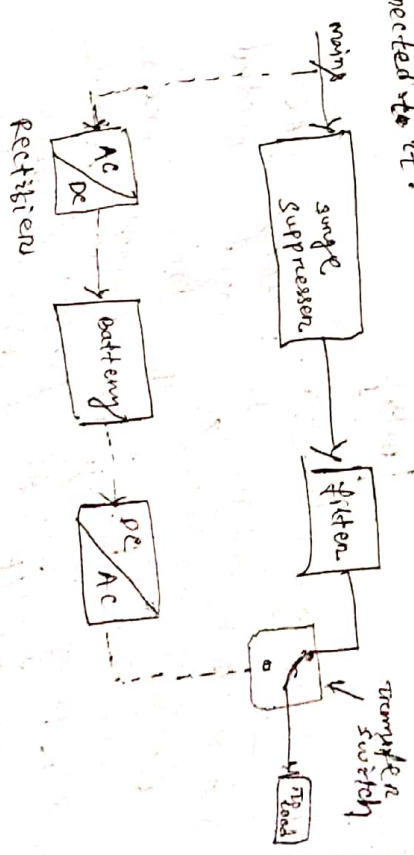→ when power breakage occurs, this DC voltage is converted to AC by transformer, and is connected to it.




ON-LINE UPS:-

→ In this system of UPS, the system always remains on battery, whether mains AC is present or not.

→ When mains AC is present, it provides power to DC supply of inverter section as well as charger of the battery simultaneously.

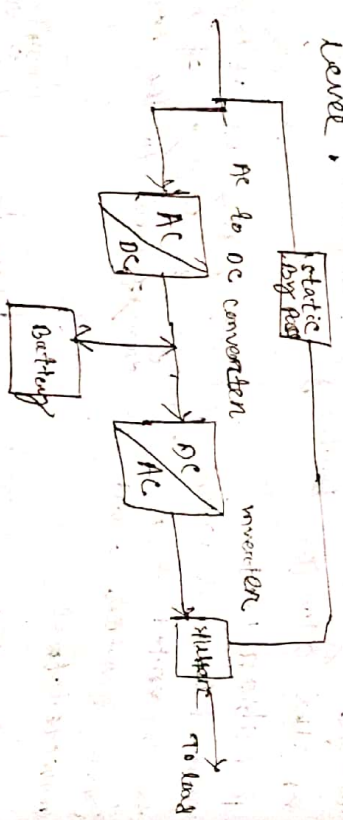→ When mains AC is not present, it will run the connected load till the battery has a recommended discharge level.




Line Interactive UPS:-

→ In this design the battery is always connected to the o/p of the UPS.

→ Battery charging is done during normal times when the UPS AC fails.

→ Battery charging is done during normal times when the UPS AC fails. The inverter switches and they

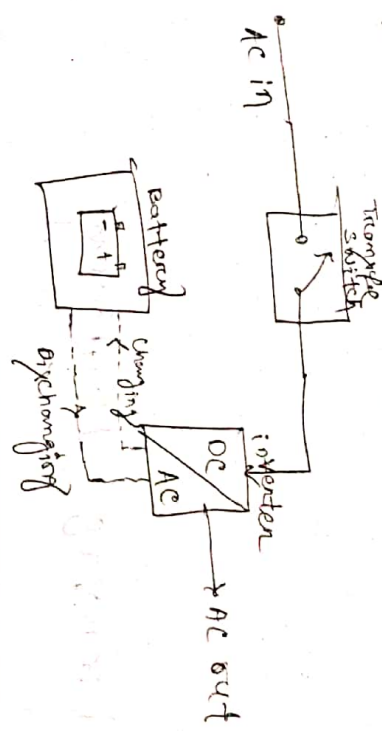automatically functioning to provide power to load immediately.



catch coil:- when the ON button is momentarily actuated, the catch coil is energized to set the relay to its latched position.


No. normally open it is a contact that does not flow current in its normal state.

Energized o/p:- energized a single bit of data if the input reading to it is true.

signaling:- adding more rungs that are associated with the same output or inputs of outputs for the same

BLOCK DIAGRAM OF PROGRAMMABLE

Logic Controller:

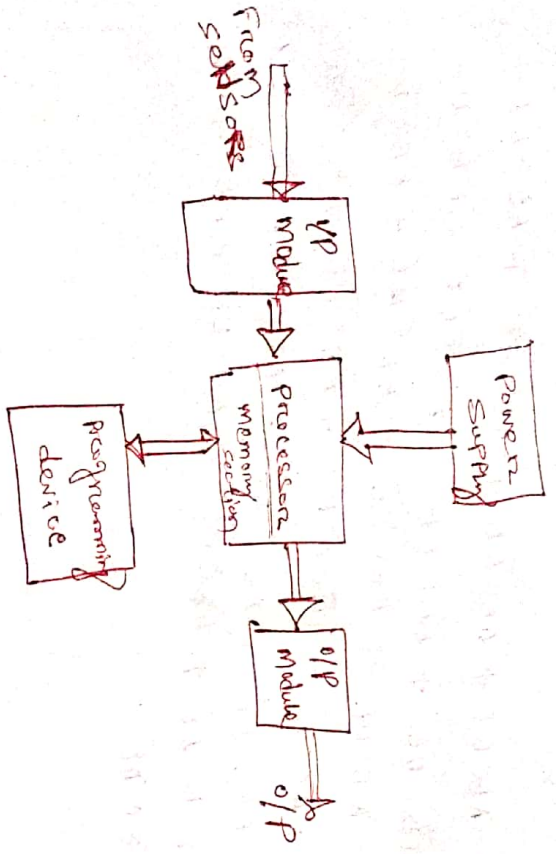

Processor section (CPU):

The processor section is 'brain' of PLC which consists of RAM, ROM, logic solver and user memory. CPU The central processing unit is heart of PLC. CPU controls monitors and supervises all operation with in PLC. The CPU makes decision and executes control instructions based on the program instruction in memory.

Program input and output module:

- The input module is a mediator between input devices and central processing unit (CPU) which is used to convert analog signal into digital signal.
- The output module is a mediator unit which is used to convert digital signal into analog signal.

Power supply:

Power supply is provided to the processor unit; power supply unit. Power supply may input and output module mounted unit. Most be integral on separately mounted unit. Most of the PLC operated on 0 volts DC and 24 volts.

Memory section:

Memory section is the area of the CPU in which the memory section is stored and retrieved. Data and information is stored numerical data required data and information to store numerical data etc. User memory is used to store calculation, bar code data etc. User memory in match calculation program.

Programming devices:

Programming devices are dedicated devices used for loading the user program into the processor memory. It is used to edit it and to monitor the execution of the program of the PLC. It is also used to troubleshoot the PLC ladder logic program. Hand held terminal computer and terminal or personal computer are commonly used in programming PLCs.