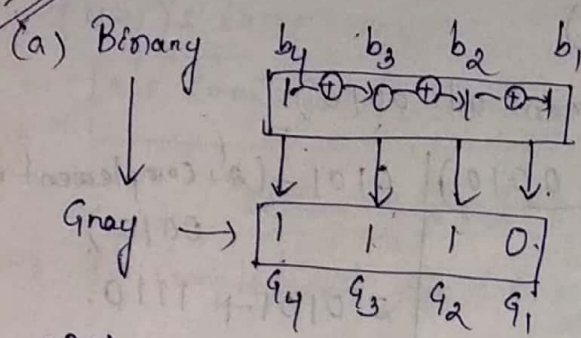


DI-23/10/22

Code conversion: Prepared By- Lopsa Pantyrahhi  
Lect. (Electrical)





$$G_4 = b_4$$

$$G_3 = b_4 \oplus b_3$$

$$G_2 = b_3 \oplus b_2$$

$$G_1 = b_2 \oplus b_1$$

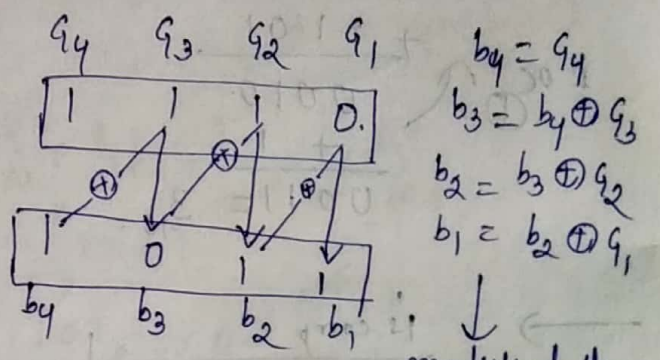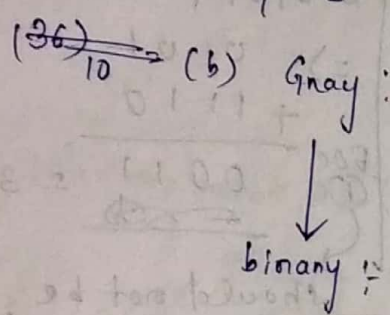

$$b_4 = G_4$$

$$b_3 = b_4 \oplus G_3$$

$$b_2 = b_3 \oplus G_2$$

$$b_1 = b_2 \oplus G_1$$

modified form

$$b_4 = G_4, b_3 = G_4 \oplus G_3$$

$$b_2 = G_4 \oplus G_3 \oplus G_2$$

$$b_1 = G_4 \oplus G_3 \oplus G_2 \oplus G_1$$

EX-OR gate also named as modulo-2 adder.


$$0+0=0$$

$$0+1=1$$

$$1+0=1$$


$$1+1=0$$

pb:- Represent (56) in gray code.

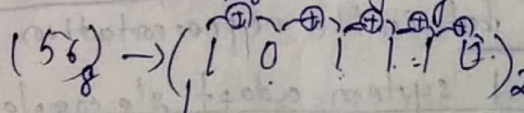

gray code = (1 1 1 0 0 1)

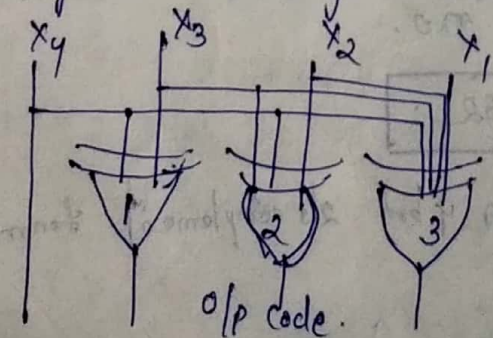pb:- Identify the following code converter.



Gray to binary code converter.

# Boolean Algebra:-

'AND' law and 'OR' law.

Identity elements.

AND

OR

1

0

$$A \cdot 0 = 0$$

$$A + 0 = A$$

$$A \cdot 1 = A$$

$$A + 1 = 1$$

① Commutative law:-

$$A + B = B + A$$

$$A \cdot B = B \cdot A$$

$$A \oplus B = B \oplus A$$

$$A \uparrow B = B \uparrow A$$

$$A \odot B = B \odot A$$

$$A \downarrow B = B \downarrow A$$

$\uparrow$  = NAND

$\downarrow$  = NOR

② Associative law:-

$$(A + B) + C = A + (B + C)$$

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$

$$(A \uparrow B) \uparrow C \neq A \uparrow (B \uparrow C)$$

\* (NAND and NOR operations are not associative)

$$(A \oplus B) \oplus C = A \oplus (B \oplus C)$$

$$(A \odot B) \odot C = A \odot (B \odot C)$$

③ Consensus law:-

$$(1) A \cdot B + \bar{A} \cdot C + B \cdot C = A \cdot B + \bar{A} \cdot C$$

$$(2) x \cdot y + \bar{y} \cdot z + x \cdot z = x \cdot y + \bar{y} \cdot z$$

Proof :-  $A \cdot B + \bar{A} \cdot C + B \cdot C (A + \bar{A})$

$$= A \cdot B + \bar{A} \cdot C + B \cdot C \cdot A + B \cdot C \cdot \bar{A} = A \cdot B (1 + C) + \bar{A} \cdot C (1 + B)$$

$$= A \cdot B + \bar{A} \cdot C \text{ (R.H.S)}$$

(4) Transposition law:-

$$A \cdot B + \bar{A} \cdot C = (A + C) \cdot (\bar{A} + B)$$

(5) Distributive law:-

$$A \cdot (B + C) = A \cdot B + A \cdot C$$

$$\text{Dual } \left\{ \begin{aligned} A + B \cdot C &= (A + B) \cdot (A + C) \end{aligned} \right.$$

$$(6) \bar{A} + A \cdot B = \bar{A} + B$$



(c)  $\overline{AB} + \overline{ABC} \Rightarrow \overline{x} + \overline{c}$   
 $= \overline{x} + \overline{c}$   
 $= \overline{AB} + \overline{C}$

⑥ DeMorgan's law: (i) NOR gate = bubbled AND gate.  
 $A + B + C + \dots = \overline{\overline{A} \cdot \overline{B} \cdot \overline{C} \dots}$

(ii) NAND gate = bubbled OR gate.  
 $\overline{A \cdot B \cdot C \dots} = \overline{A} + \overline{B} + \overline{C} + \dots$

Additional law: To find the complement of a boolean function 'F' (i) Find dual of 'F'. i.e. 'F<sub>D</sub>'

(ii) Complement all variables

eg:-  $F = \overline{A} \cdot (B + \overline{C}) (\overline{D} + E)$   
 $\overline{F} = ?$

Sol<sup>n</sup>:- (i)  $F = \overline{A} + \overline{BC} + \overline{DE}$

(ii)  $\overline{F} = \overline{\overline{A} + \overline{BC} + \overline{DE}}$

→ simplify the following boolean expressions.

(a)  $A \oplus B \oplus AB = ?$

Sol<sup>n</sup>:-  $A \oplus B \oplus AB = \overline{x} \cdot AB + x \cdot \overline{AB}$   
 $= \overline{A} \oplus B \cdot AB + (A \oplus B) \cdot \overline{AB}$   
 $= (A \oplus B) \cdot AB + \dots$   
 $= (\overline{A} \overline{B} + AB) \cdot AB + (\overline{A} B + A \overline{B}) \cdot \overline{AB}$   
 $= 0 + AB + \overline{A} B + 0 + 0 + A \overline{B}$   
 $= AB + \overline{A} B + A \overline{B}$   
 $= A + B$

(b) If  $A \oplus B \oplus C = D$  then find  $A \oplus B \oplus D = ?$

Sol<sup>n</sup>:-  $A \oplus B \oplus A \oplus B \oplus C =$

1)  $x \oplus x \oplus C = \overline{A} + B + C$

2)  $0 \oplus C = A + B + C = (A + B) + C$


3)  $C = (A + B) \cdot (A + B) = A + B$



Q11 Determine the no. of two i/p NAND gate required to implement the following functions.

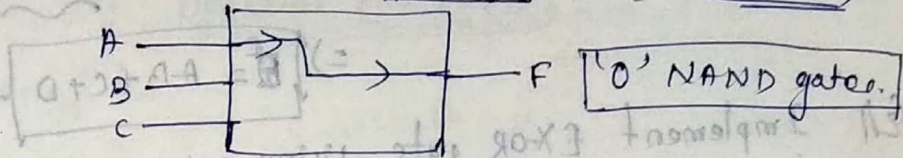(i)  $F = A + \overline{A}B + ABC$


sol<sup>n</sup>:-  $F = A + \overline{A}B + ABC$   
 $F = A + \overline{A}B + ABC$   
 $= A [1 + \overline{B} + BC]$   
 $F = A$  (as  $1+x=1$ )



(ii) How many NAND gates are required

$F = \overline{ABC} \rightarrow$  3-i/p AND gate

sol<sup>n</sup>  $F = \overline{ABC}$

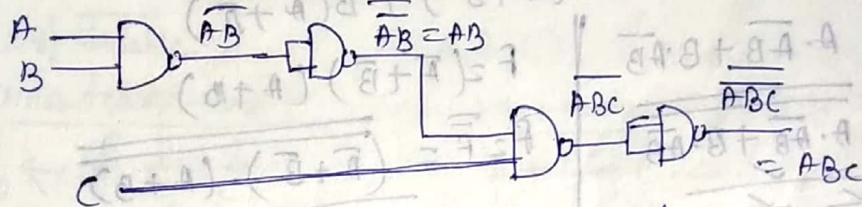

(iii) How many NAND gates are required

$F = ABCD$

sol<sup>n</sup>:-  $\overline{ABCD} \rightarrow$  4 2-i/p NAND gates

(iv)  $F = \overline{ABCD} \rightarrow$  4 i/p NAND gate

sol<sup>n</sup>:-  $F = \overline{ABCD} = \overline{AB} \cdot \overline{CD} \rightarrow$  5 NAND gates

(v) simplify  $F(A, B, C) = \overline{A}C + \overline{C}D + \overline{B}C + AB$  to 4 literals

~~$\overline{A}C = \overline{A}C(B + \overline{B}) = \overline{A}CB + \overline{A}C\overline{B}$   
 $\overline{C}D = \overline{C}D(A + \overline{A}) = \overline{C}DA + \overline{C}D\overline{A}$   
 $\overline{B}C = \overline{B}C(A + \overline{A}) = \overline{B}CA + \overline{B}C\overline{A}$~~



$$2 \quad \overline{B}CA(D+\overline{D}) + \overline{B}C\overline{A}(D+\overline{D})$$

$$2 \quad \overline{B}CAD + \overline{B}C\overline{A}D + \overline{B}CA\overline{D} + \overline{B}C\overline{A}\overline{D}$$

Sol<sup>n</sup>:  $F(A,B,C) = \overline{A}C + \overline{C}D + \overline{B}C + AB$

$$= (\overline{A} + \overline{B})C + \overline{C}D + AB$$

~~$$= \overline{A}B + C$$~~

$$= \overline{A}BC + \overline{C}D + AB = AB + C + \overline{C}D$$

~~Literal = Variable (or) complement of a variable.~~

$F(A,B) \rightarrow A, \overline{A}, B, \overline{B}$   
4 literals.

$F(A,B,C) = A, \overline{A}, B, \overline{B}, C, \overline{C}$   
6 literals.

$$\Rightarrow F = AB + C + D \rightarrow \underline{4 \text{ literals}}$$

Q11 Implement EX-OR gate using minimum no. of (a) NAND gates (b) NOR gates.

Sol<sup>n</sup>:  $F = A \oplus B = \overline{A}B + A\overline{B}$   
 $= \overline{A}B + A\overline{B} + A \cdot \overline{A} + B \cdot \overline{B}$   
 $= A(\overline{A} + \overline{B}) + B(\overline{A} + \overline{B})$

$$F = A \cdot \overline{A}B + B \cdot A\overline{B}$$

$$F = \overline{\overline{A \cdot \overline{A}B + B \cdot A\overline{B}}}$$

$$F = \overline{A \cdot \overline{A}B \cdot B \cdot A\overline{B}}$$

$$F = (\overline{A} + \overline{B})(A + B)$$

$$F = \overline{\overline{(\overline{A} + \overline{B})(A + B)}}$$

$$F = \overline{\overline{A} + \overline{B}} + \overline{A + B}$$

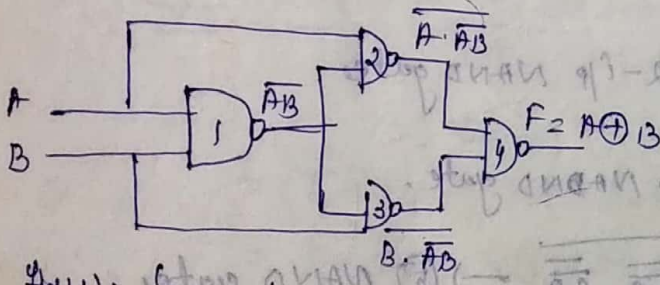


Fig (1): EX-OR using min no. of NAND gates.


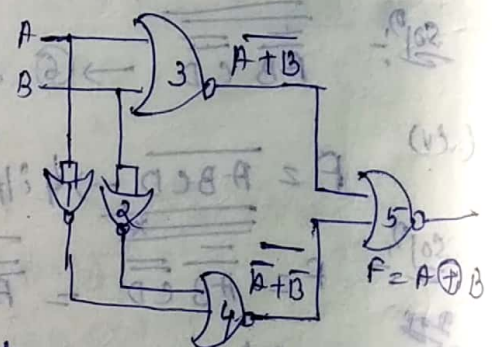


Fig (2): EX-OR using min no. of NOR gates.


The above ckt's are converted to EX-NOR gate as follows:-

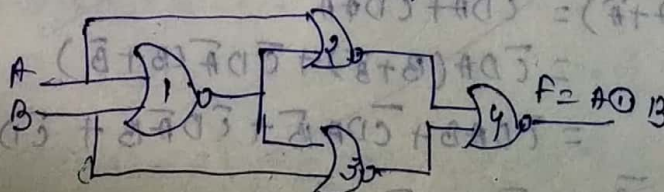(1) In Fig (1) replace all NAND gates with NOR gates as shown below:-





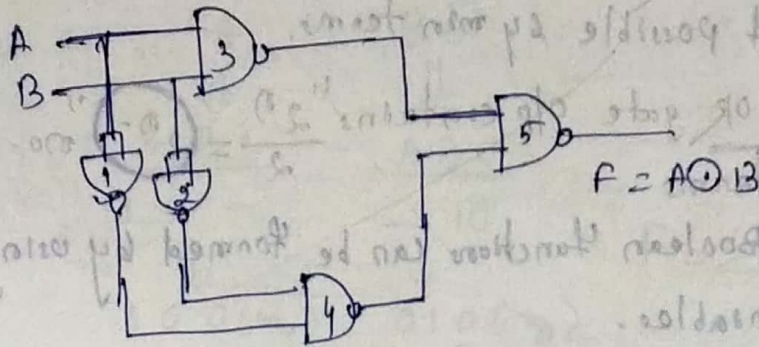(c) In Fig(a) replace all NOR gates by NAND gates



Operator precedence:

- (1) parenthesis ( )
- (2) NOT
- (3) AND
- (4) OR → least priority.

Min terms, Max terms:

Variable = 0, Variable = 1  
 (m<sub>0</sub> to m<sub>7</sub>) min terms → (8)

$m_0 \leftarrow \begin{matrix} 0 & 0 & 0 \\ \bar{A} & \bar{B} & \bar{C} \end{matrix}$   
 $m_1 \leftarrow \begin{matrix} 0 & 0 & 1 \\ \bar{A} & \bar{B} & C \end{matrix}$   
 , , ,  
 $m_6 \leftarrow \begin{matrix} 1 & 1 & 0 \\ A & B & \bar{C} \end{matrix}$   
 $m_7 \leftarrow \begin{matrix} 1 & 1 & 1 \\ A & B & C \end{matrix}$

Variable = 0, Variable = 1  
 Max terms → (8) (M<sub>0</sub> to M<sub>7</sub>)



$\bar{A} + \bar{B} + \bar{C} \rightarrow M_7$   
 $\bar{A} + \bar{B} + C \rightarrow M_6$   
 , , ,  
 $A + B + \bar{C} \rightarrow M_1$   
 $A + B + C \rightarrow M_0$

property: - (i)  $M_j = m_j$  and vice versa.

(a) sum of all min terms = 1 i.e.  $\sum_{i=0}^{2^n-1} m_i = 1$

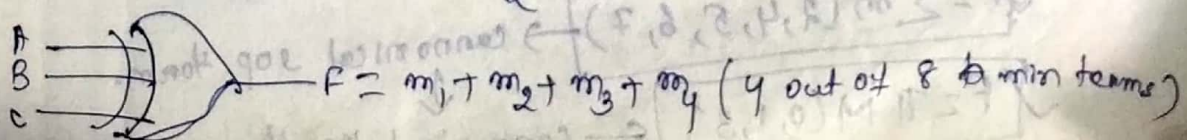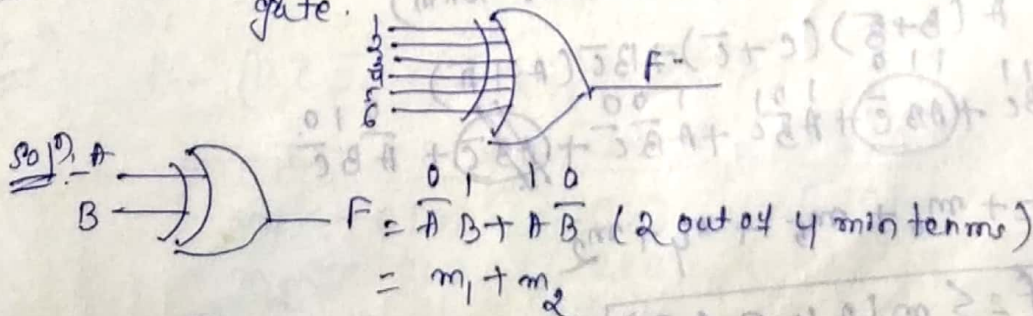(b) The product of all max terms = 0 i.e.  $\prod_{j=0}^{2^n-1} M_j = 0$

pb//: How many min terms are present at the o/p of 6 o/p EX-OR gate.






For 6 i/p. EX-OR gate the total no. of min terms are 32 out of possible 64 min terms.

→ i/p EX-OR gate o/p contains  $\frac{2^n}{2} = 2^{n-1}$  no. of min terms.

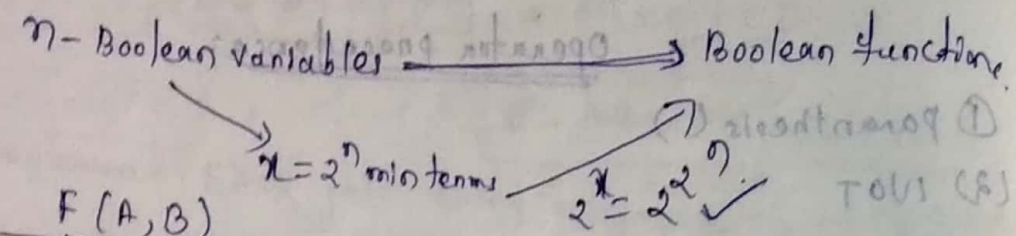→ How many Boolean functions can be formed by using 'n' boolean variables.



		F(A, B)				
		F <sub>0</sub>	F <sub>1</sub>	F <sub>2</sub>	F <sub>3</sub>	F <sub>15</sub>
m <sub>0</sub>	0 0	0	0	0	0	1
m <sub>1</sub>	0 1	0	0	0	0	1
m <sub>2</sub>	1 0	0	0	1	0	1
m <sub>3</sub>	1 1	0	1	0	1	1

$m_2 = A \cdot \bar{B}$   
 $= A/B$  (inhibition)

φ (Null), AND inhibition, Identity.

Forms of Boolean functions:

- ① SOP (sum of products) form
  - ② POS (product of sums) form
  - ③ Canonical form
    - Canonical SOP form / sum of min terms form
    - Canonical POS form / product of max terms form
- convert  $F(A, B, C) = A(B + \bar{C})$  into Canonical SOP form. (sum of min terms form)

Sol<sup>n</sup>.

$$F_2 = A(B + \bar{C})(C + \bar{C}) + A\bar{B}\bar{C}(A + \bar{A})$$

$$F_2 = \overset{111}{A\bar{B}C} + \overset{110}{A\bar{B}\bar{C}} + \overset{101}{A\bar{B}C} + \overset{100}{A\bar{B}\bar{C}} + \overset{010}{\bar{A}B\bar{C}}$$

$$= m_7 + m_6 + m_5 + m_4 + m_2$$

$F_2 \sum m(2, 4, 5, 6, 7)$  → Canonical SOP form.

$F_2 \prod M(0, 1, 3)$  ← Canonical POS form.

Method-2

1	1 0
A	B C
↓	↓
A B C	A B C
1 - -	- 1 0
↓	↓
1 0 0 (m <sub>4</sub> )	0 1 0 (m <sub>5</sub> )
1 0 1 (m <sub>5</sub> )	<del>1 0 1</del> (repetition)
1 1 0 (m <sub>6</sub> )	
1 1 1 (m <sub>7</sub> )	

$F = \sum(2, 4, 5, 6, 7)$

→ convert the following expression into canonical pos form.


$F(x, y, z) = \bar{x} \cdot (\bar{x} + y + z) (y + \bar{z})$  → canonical pos form  
(product of max terms form)

Sol:-

1	0 1
x	y + z
x + y + z	x + y + z
1 0 0	0 0 1
1 0 1	<del>1 0 1</del>
1 1 0	
1 1 1	

$F = \Pi M(\bar{0}, 1, 2, 3, 5, 7) (4, 5, 6, 7)$

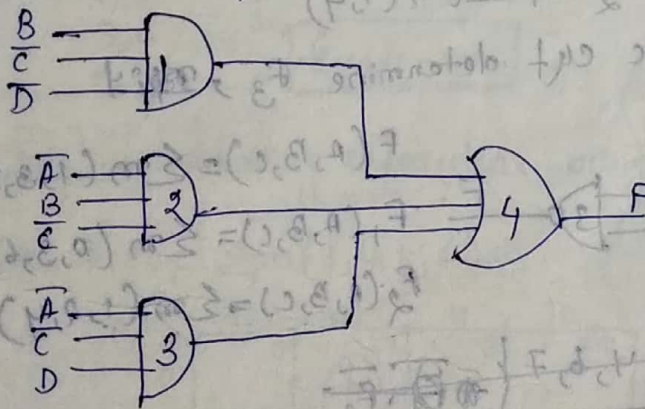→ In the following logic circuit identify the redundant gate?



Sol:-

$F = (B\bar{C}\bar{D}) + (\bar{A}B\bar{C}) + (\bar{A}\bar{C}D)$

<del>B C D</del>	A B C D	A B C D	A B C D
m <sub>4</sub> ← 0 1 0 0	0 1 0 0	0 1 0 1	0 0 0 1
m <sub>2</sub> ← 1 0 0 0			0 1 0 1
			m <sub>1</sub> m <sub>5</sub>



Gate-2 is redundant gate.




## Two-level logic

① SOP form  $\rightarrow$  **AND-OR** logic  $\equiv$  **NAND-NAND** logic

$$F = A \cdot B + C \cdot D$$

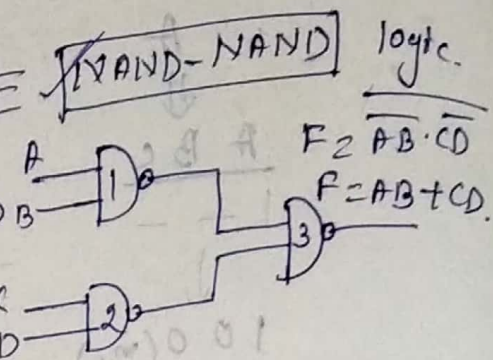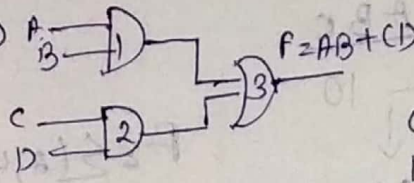

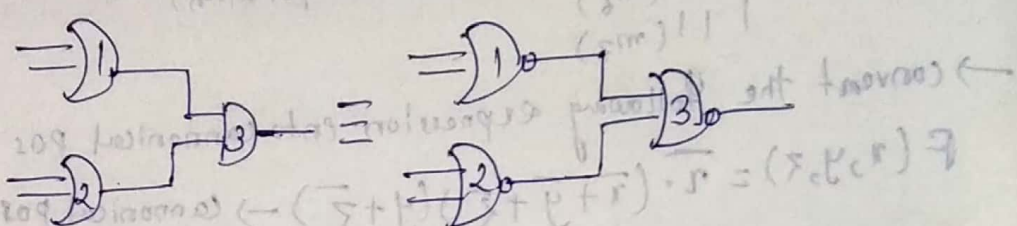② POS form  $\rightarrow$  **OR-AND** logic  $\equiv$  **NOR-NOR** logic



Q.  $F_1(A, B, C) = \sum m(0, 2, 3, 5, 6)$

$F_2(A, B, C) = \sum m(1, 2, 3, 4, 6)$


Find (a)  $F_1 \cdot F_2$  (b)  $F_1 + F_2$  (c)  $F_1 - F_2$

Sol<sup>n</sup>:  
 $\downarrow$   
 all minterms common to both  $F_1$  and  $F_2$   
 $\sum m(2, 3, 6)$

$F_1 + F_2 = \sum m(0, 1, 2, 3, 4, 5, 6)$

$F_1 - F_2 = \sum m(0, 5)$ ,  $F_2 - F_1 = \sum m(1, 4)$

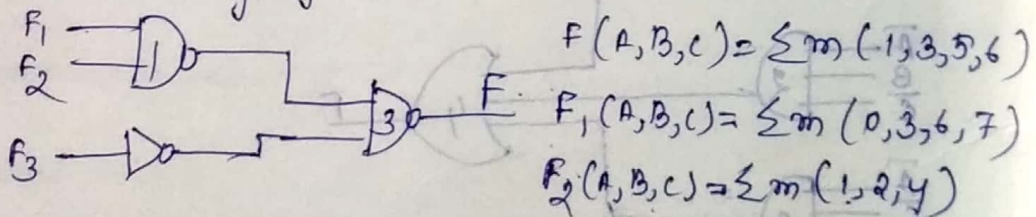Prob 11 In the following logic ckt determine  $F_3$



Sol<sup>n</sup>:  
 $F_1 \cdot F_2 = \sum m(0, 1, 2, 3, 4, 6, 7)$

$$\begin{aligned}
 F &= \overline{F_1 \cdot F_2} \cdot F_3 \\
 &= \overline{F_1 + F_2} \cdot F_3 \\
 &= \overline{F_1} \cdot \overline{F_2} \cdot F_3 + \overline{F_2} \cdot F_3 \\
 &= (\overline{F_1} \cdot \overline{F_2}) \cdot (\overline{F_2} \cdot F_3) = (F_1 + F_2)(F_2 + F_3) \\
 &= F_1 \cdot F_2
 \end{aligned}$$