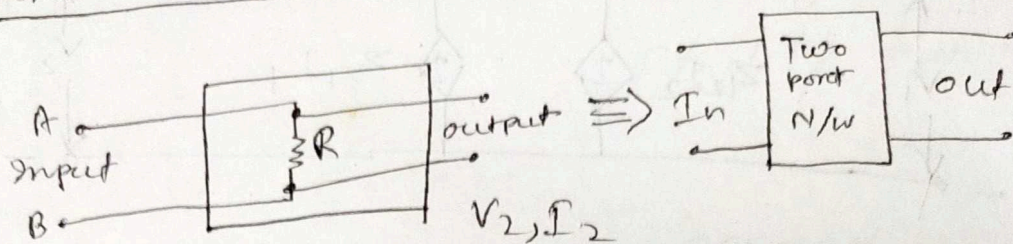


Two port network:-



A rectangular box that represents a network, consists of two pairs of terminals where one pair of terminals can be designated as input, the other pair being output, it is called a two port n/w or a four terminal n/w.

Open circuit Impedance parameters:

$$V_1 = f(I_1, I_2)$$

$$V_2 = f(I_1, I_2)$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

as $[V] = [Z][I]$

① when port ② is open circuited,

i.e., $I_2 = 0$


$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}, \quad Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

② when port ① is open circuited,

i.e., $I_1 = 0$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}, \quad Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

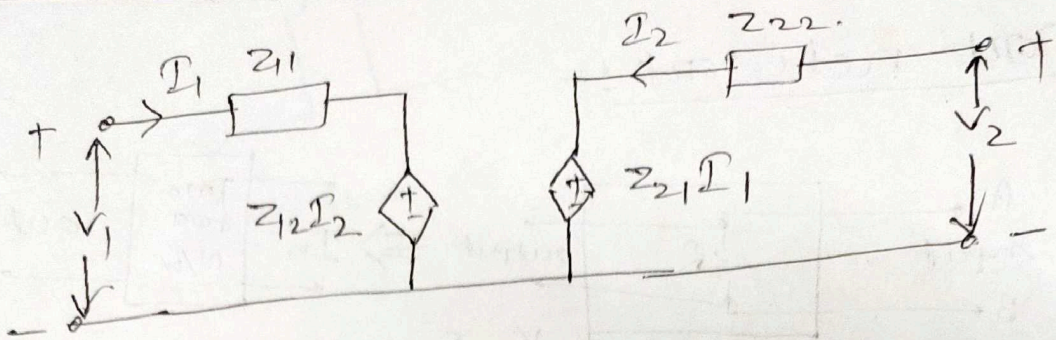Z_{11}, Z_{22} are called i/p and o/p driving point impedances respectively.
 Z_{12}, Z_{21} are called reverse and forward transfer impedances respectively.



Short circuit admittance parameter

$$I_1 = f(V_1, V_2)$$

$$I_2 = f(V_1, V_2)$$

$$I_1 = y_{11} V_1 + y_{12} V_2$$


$$I_2 = y_{21} V_1 + y_{22} V_2$$

Ⓐ port ② is short ckted i.e, $V_2 = 0$

$$y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}, \quad y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

Ⓑ port ① is short ckted i.e, $V_1 = 0$.

$$y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}, \quad y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

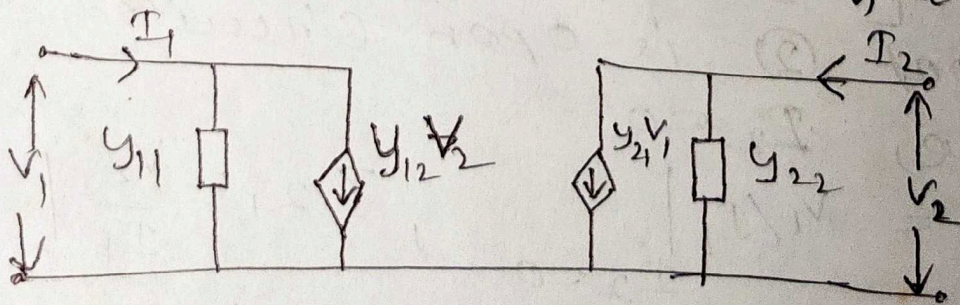

Hybrid parameters (h-parameter)

h-parameter representation is widely used in modelling of electronic components and ckt.

Here both short ckt and open ckt terminal condition are utilized.

Hence, this representation is known as hybrid parameter representation

$$V_1 = f(I_1, V_2)$$

$$I_2 = f(I_1, V_2)$$

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

when port ② is short ckted i.e.,

$$V_2 = 0.$$

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}$$

h_{11} = input impedance,

unit is Ω .

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

(forward current gain) \rightarrow unitless.


Port 1 is short circuited, i.e., $I_1 = 0$

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1 = 0}$$

(reverse voltage gain) \rightarrow unitless

$$h_{22} = \frac{I_2}{V_2} \Big|_{I_1 = 0}$$


(O/P admittance) $\rightarrow \Omega$

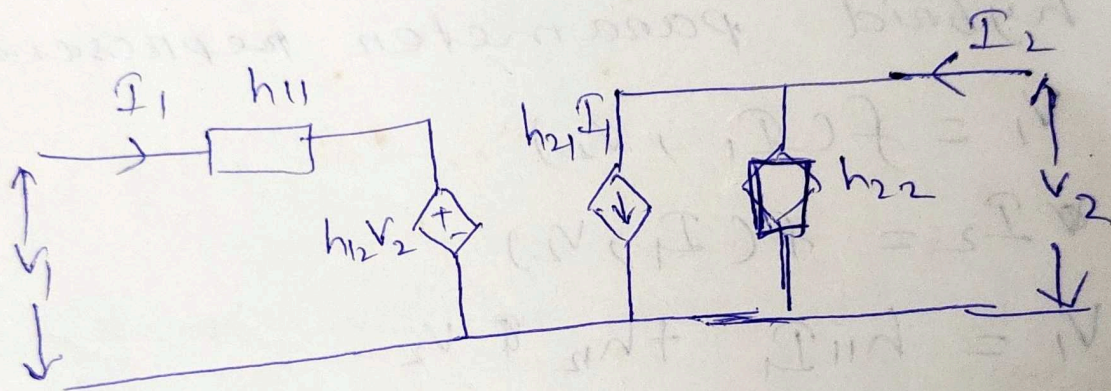

ABCD parameters

These are used in analysis of power transmission engineering.

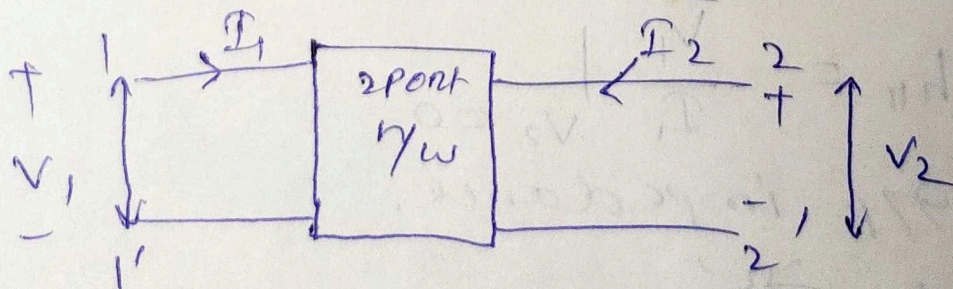These are also called transmission parameters.



$$V_1 = f(V_2, I_2)$$

$$I_1 = f(V_2, I_2)$$

Port 2 is opened, $I_2 = 0$.


$$A = \frac{V_1}{V_2} \Big|_{I_2=0} \rightarrow \text{unitless}$$

$$C = \frac{I_1}{V_2} \Big|_{I_2=0} \rightarrow \text{Admittance } (\Omega^{-1})$$

Port 2 is short ckted, $V_2 = 0$.


$$B = \frac{V_1}{(-I_2)} \Big|_{V_2=0} \rightarrow \text{Impedance } (\Omega)$$

$$D = \frac{I_1}{(-I_2)} \Big|_{V_2=0} \rightarrow \text{unitless}$$

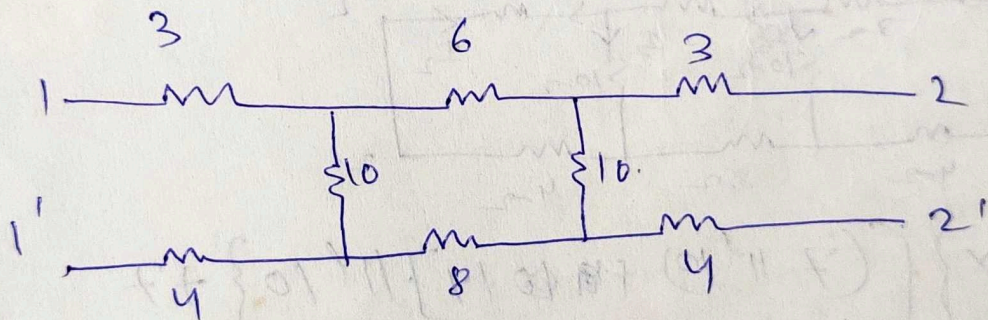

Find A, B, C, D parameters.

(a) port (2) is opened, $I_2 = 0$.

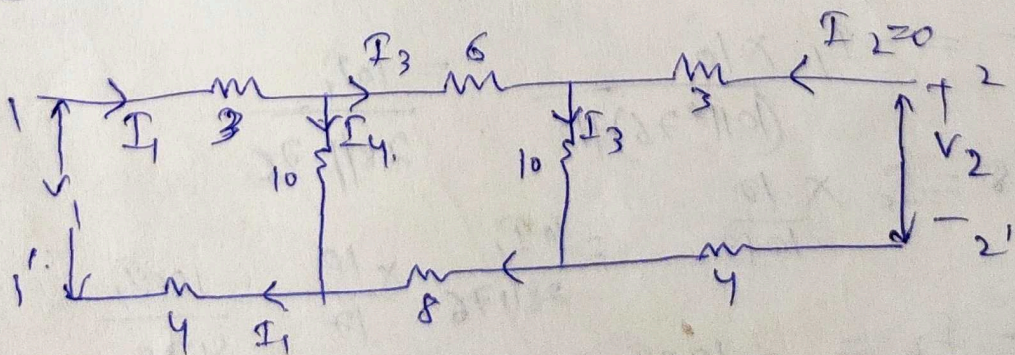

$$V_1 = I_1 \times [3 + 4 + (10 \parallel 26j)]$$

$$\Rightarrow \frac{V_1}{I_1} = 14.06$$

$$V_2 = I_3 \times 10 \Omega$$

$$I_3 = \frac{I_1 \times 10}{10 + 24} = \frac{10 I_1}{34}$$


$$V_2 = \frac{10 I_1}{34} \times 10 = \frac{100}{34} I_1$$

$$\Rightarrow \frac{V_2}{I_1} = \frac{100}{34}$$

$$\Rightarrow \frac{I_1}{V_2} = \frac{34}{100} = 0.34 \Omega^{-1}$$

$$\frac{V_1}{V_2} = A = \frac{14.04 I_1}{\frac{100}{34} I_1} = \frac{14.04}{100} \times 34 = 4.7804$$

When $V_2 = 0$

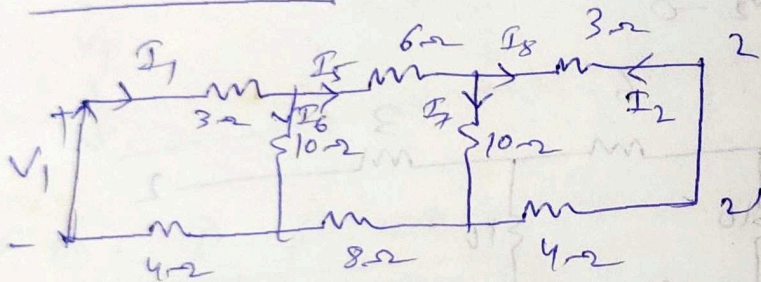

$$V_1 = I_1 \times \left\{ \left[(7 \parallel 10) + 14 \right] \parallel 10 \right\} + 7$$

$$V_1 = 13.4435 I_1$$

$$I_2 = -I_8$$

$$I_5 = -I_1 \times \frac{10}{(10 \parallel 76) + 10} = \frac{10 I_1}{28 \parallel 76}$$

$$I_8 = I_5 \times \frac{10}{10 + 7} = \frac{10 I_1}{28 \parallel 76} \times \frac{10}{17} = \frac{100 I_1}{478}$$

$$-I_2 = \frac{100 I_1}{478}$$

$$\Rightarrow \frac{I_1}{(-I_2)} = D = \frac{478}{100} = 4.78$$

$$\frac{V_1}{(-I_2)} = B = \frac{13.44 \times 478}{100} = 64.26 \Omega$$

Inter relationship between parameters of 2-port Network,

Y in terms of Z

$$[V] = [Z][I]$$

$$\Rightarrow [I] = [Z]^{-1}[V]$$

$$= [Y][V]$$

$$\therefore [Y] = [Z]^{-1}$$

$$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix}^{-1}$$

Similarly,

$$[Z] = [Y]^{-1}$$

$$\Rightarrow \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}^{-1}$$

ABCD in terms of Z

$$\begin{aligned} V_1 &= z_{11} I_1 + z_{12} I_2 \quad \text{--- (1)} & V_1 &= AV_2 - BI_2 \quad \text{--- (3)} \\ V_2 &= z_{21} I_1 + z_{22} I_2 \quad \text{--- (2)} & I_1 &= CV_2 - DI_2 \quad \text{--- (4)} \end{aligned}$$

from eqn (2),

$$z_{21} I_1 = V_2 - z_{22} I_2$$

$$\Rightarrow I_1 = \frac{1}{z_{21}} V_2 - \frac{z_{22}}{z_{21}} I_2 \quad \text{--- (5)}$$

Comparing eqn (4) and (5),

$$C = \frac{1}{z_{21}}, \quad D = \frac{z_{22}}{z_{21}}$$

from eqn (1),

$$V_1 = z_{11} I_1 + z_{12} I_2$$

putting the value of I_1 from eqn (5),

in eqn (1),

$$V_1 = z_{11} \left[\frac{1}{z_{21}} V_2 - \frac{z_{22}}{z_{21}} I_2 \right] + z_{12} I_2$$

$$= \frac{z_{11}}{z_{21}} V_2 - \frac{z_{11} z_{22}}{z_{21}} I_2 + z_{12} I_2$$

$$\Rightarrow \frac{z_{11}}{z_{21}} V_2 - I_2 \left(\frac{z_{11} z_{22}}{z_{21}} - z_{12} \right)$$

$$\text{so, } A = \frac{z_{11}}{z_{21}}, \quad B = -z_{12} + \frac{z_{11} z_{22}}{z_{21}}$$

h' in terms of Z

$$V_1 = z_{11} I_1 + z_{12} I_2 \quad \text{--- (1)}$$

$$V_2 = z_{21} I_1 + z_{22} I_2 \quad \text{--- (2)}$$

$$V_1 = h_{11} I_1 + h_{12} V_2 \quad \text{--- (3)}$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad \text{--- (4)}$$

$$z_{22} I_2 = V_2 - z_{21} I_1$$

$$\Rightarrow I_2 = \frac{V_2}{z_{22}} - \frac{z_{21}}{z_{22}} I_1 \quad \text{--- (5)}$$

comparing eqⁿ (4) and (5),

$$h_{21} = -\frac{z_{21}}{z_{22}}, \quad h_{22} = \frac{1}{z_{22}}$$

$$V_1 = z_{11} I_1 + z_{12} I_2$$

$$= z_{11} I_1 + z_{12} \left(\frac{V_2}{z_{22}} - \frac{z_{21}}{z_{22}} I_1 \right)$$

$$= z_{11} I_1 + \frac{z_{12}}{z_{22}} V_2 - \frac{z_{12} z_{21}}{z_{22}} I_1$$

$$= I_1 \left[z_{11} - \frac{z_{12} z_{21}}{z_{22}} \right] + \frac{z_{12}}{z_{22}} V_2$$

$$\boxed{h_{11} = z_{11} - \frac{z_{12} z_{21}}{z_{22}}}, \quad \boxed{h_{12} = \frac{z_{12}}{z_{22}}}$$

ABCD in terms of Y

$$I_1 = y_{11} V_1 + y_{12} V_2$$

$$I_2 = y_{21} V_1 + y_{22} V_2$$

$$V_1 = A V_2 - B I_2$$

$$I_1 = C V_2 - D I_2$$

$$y_{21} V_1 = -y_{22} V_2 + I_2$$

$$\Rightarrow V_1 = \frac{-y_{22}}{y_{21}} V_2 + \frac{1}{y_{21}} I_2$$

$$V_1 = A V_2 - B I_2$$

$$A = \frac{-y_{22}}{y_{21}}, \quad B = \frac{1}{y_{21}}$$

$$I_1 = y_{11} \left[\frac{-y_{22}}{y_{21}} V_2 + \frac{1}{y_{21}} I_2 \right] + y_{12} V_2$$

$$= y_{12} \left(y_{12} - y_{11} \frac{y_{22}}{y_{21}} \right) + \frac{y_{11}}{y_{21}} I_2$$

$$= V_2 \left(y_{12} - y_{11} \frac{y_{22}}{y_{21}} \right) + \frac{y_{11}}{y_{21}} I_2$$

$$I_1 = C V_2 - D I_2$$

$$C = y_{12} - \frac{y_{11} y_{22}}{y_{21}}$$

$$D = \frac{-y_{11}}{y_{21}}$$

h in terms of y!

$$I_1 = y_{11} V_1 + y_{12} V_2$$

$$I_2 = y_{21} V_1 + y_{22} V_2$$

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

$$y_{11} V_1 = -y_{12} V_2 + I_1$$

$$\Rightarrow V_1 = \frac{-y_{12}}{y_{11}} V_2 + \frac{1}{y_{11}} I_1$$

$$\Rightarrow \boxed{h_{11} = \frac{1}{y_{11}}}, \quad \boxed{h_{12} = \frac{-y_{12}}{y_{11}}}$$

$$\begin{aligned}
 I_2 &= y_{21} \left[-\frac{y_{12}}{y_{11}} V_2 + \frac{1}{y_{11}} I_1 \right] + y_{22} V_2 \\
 &= -\frac{y_{21} y_{12}}{y_{11}} V_2 + \frac{y_{21}}{y_{11}} I_1 + y_{22} V_2 \\
 &= V_2 \left[y_{22} - \frac{y_{21} y_{12}}{y_{11}} \right] + \frac{y_{21}}{y_{11}} I_1
 \end{aligned}$$

$$h_{22} = \left[y_{22} - \frac{y_{21} y_{12}}{y_{11}} \right]$$

$$h_{21} = \frac{y_{21}}{y_{11}}$$

(d) $A = 2, B = 1, C = 3, D = -2$

Find z-parameters.

Soln

$$V_1 = 2V_2 + I_2$$

$$I_1 = 3V_2 + 2I_2$$

$$V_1 = z_{11} I_1 + z_{12} I_2$$

$$V_2 = z_{21} I_1 + z_{22} I_2$$

$$I_1 = 3V_2 + 2I_2 \Rightarrow 3V_2 = I_1 - 2I_2$$

$$\Rightarrow V_2 = \frac{I_1}{3} - \frac{2}{3} I_2$$

$$\boxed{z_{21} = \frac{1}{3}, z_{22} = -\frac{2}{3}}$$

$$V_1 = 2V_2 + I_2$$

$$= 2 \left[\frac{I_1}{3} - \frac{2}{3} I_2 \right] + I_2 = \frac{2}{3} I_1 - \frac{4}{3} I_2 + I_2$$

$$V_1 = \frac{2}{3} I_1 - \frac{1}{3} I_2$$

$$\boxed{z_{11} = \frac{2}{3}, z_{12} = -\frac{1}{3}}$$

$$(Q) \quad h_{11} = 1, h_{12} = -2, h_{21} = -3, h_{22} = 2$$

find z-parameters.

$$V_1 = h_{11} I_1 + h_{12} I_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

$$V_1 = I_1 - 2V_2$$

$$I_2 = -3I_1 + 2V_2$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$I_2 = -3I_1 + 2V_2$$

$$\Rightarrow 2V_2 = 3I_1 + I_2$$

$$\Rightarrow V_2 = \frac{3}{2} I_1 + \frac{I_2}{2}$$

$$\boxed{Z_{21} = 3/2 \Omega, Z_{22} = 1/2 \Omega}$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_1 = I_1 - 2V_2$$

$$= I_1 - 2 \left(\frac{3}{2} I_1 + \frac{I_2}{2} \right)$$

$$= I_1 - 3I_1 - I_2$$

$$V_1 = -2I_1 - I_2$$

$$\therefore Z_{11} = -2 \Omega, Z_{12} = -1 \Omega$$